

Homework #4

Due: 10/7

- Use separate sheets for your answers.
- Draw a box around each answer.
- You *must* show your work by attaching your worksheets.
- Drawings and tables should be clear and unambiguous. The use of quad-ruled paper is recommended.
- When writing logic equations, remember that “ \overline{AB} ” is not equivalent to “ $\overline{A} \overline{B}$ ”.

1. [25 points] Write a Boolean equation in sum-of-products canonical form for each of these truth tables:

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

	A	B	C	D	Y
	0	0	0	0	1
	0	0	0	1	0
	0	0	1	0	1
	0	0	1	1	1
	0	1	0	0	0
	0	1	0	1	0
	0	1	1	0	1
d)	0	1	1	1	1
	1	0	0	0	1
	1	0	0	1	0
	1	0	1	0	1
	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	0
	1	1	1	1	0
	A	B	C	D	Y
	0	0	0	0	0
	0	0	0	1	0
	0	0	1	0	0
	0	0	1	1	1
	0	1	0	0	0
	0	1	0	1	0
	0	1	1	0	1
e)	0	1	1	1	1
	1	0	0	0	1
	1	0	0	1	1
	1	0	1	0	1
	1	0	1	1	1
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	0
	1	1	1	1	0

2. [15 points]

Simplify the following Boolean equations using a series of Boolean theorems. Show the result of each theorem in order and give its name. (You can check for correctness with a truth table or Karnaugh map, but you don't need to submit them.)

a) $Y = \overline{A}CB + \overline{A}B\overline{C}$

b) $Y = \overline{ABC} + A\overline{B}$

c) $Y = ABC\overline{D} + A\overline{BCD} + (\overline{A+B+C+D})$


3. [15 points] Simplify each of the following Boolean equations. Sketch a reasonably simple combinational circuit implementing the simplified equation.

(a) $Y = \overline{A}BC + \overline{B}\overline{C} + BC$

(b) $Y = (\overline{A+B+C})D + AD + B$

(c) $Y = ABCD + \overline{A}B\overline{C}D + (\overline{B+D})E$

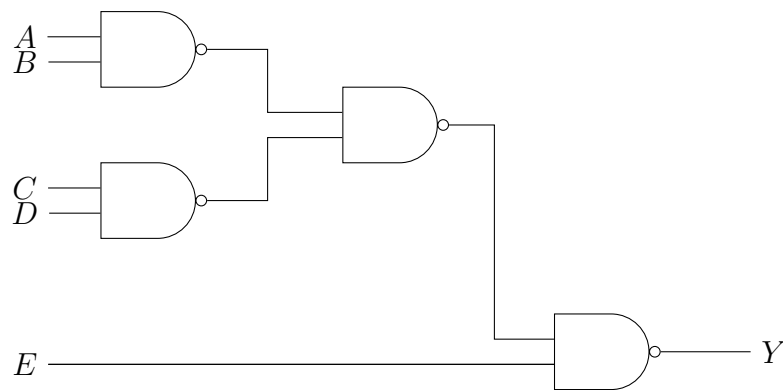4. [10 points] Using De Morgan equivalent gates and bubble pushing methods, redraw the circuit below so that you can find the Boolean expression by inspection. Show that circuit and its expression.




5. [35 points]

An M -bit *thermometer code* for the number k consists of k 1's in the least significant bit positions and $M - k$ 0's in all the more significant bit positions.

An $N : M$ *binary-to-thermometer code converter* has N bits input and $M = 2^N - 1$ outputs.

Design a 3:7 binary-to-thermometer code converter. The inputs are A_2 to A_0 , with A_2 being the high-order bit. The outputs are Y_0 to Y_6 , with Y_6 being lit only on the maximum input ($A_0 = A_1 = A_2 = 1$).

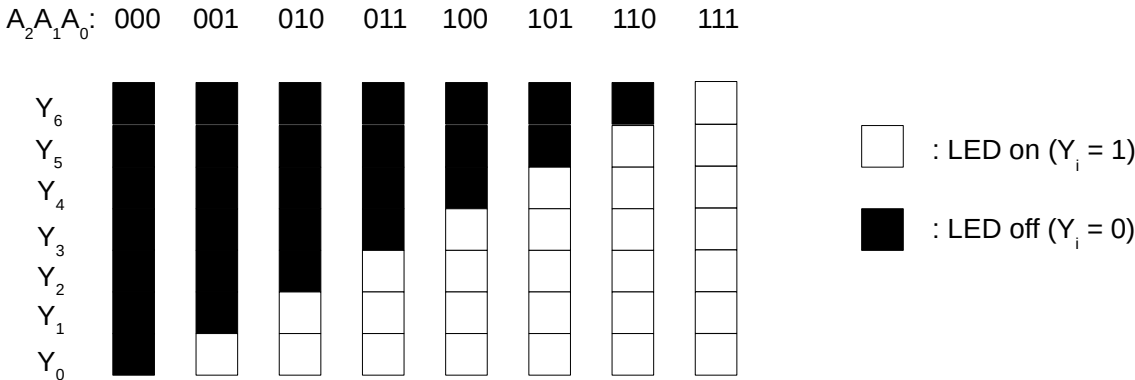If we were to connect the outputs to an array of seven LED's, here's how they would respond to different values of the three input bits:



These are often used to display digital sound levels.

Submit a (single) truth table with 3 inputs and 7 outputs. Give simplified Boolean equations for each output and sketch schematics for them using only AND and OR gates.