

Chapter 5

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 5 :: Topics

- **Introduction**
- **Arithmetic Circuits**
- **Number Systems (no)**
- **Sequential Building Blocks (later)**
- **Memory Arrays (later)**
- **Logic Arrays (maybe)**


Introduction

- **Digital building blocks:**
 - Gates, multiplexers, decoders, registers, arithmetic circuits, counters, memory arrays, logic arrays
- **Building blocks demonstrate hierarchy, modularity, and regularity:**
 - Hierarchy of simpler components
 - Well-defined interfaces and functions
 - Regular structure easily extends to different sizes
- **Will use these building blocks in**

Chapter 7 to build microprocessor

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + C_{in} \cdot (A \oplus B)$$

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + C_{in} \cdot (A \oplus B)$$

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Adders (CPAs)


- Types of carry propagate adders (CPAs):
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware

Symbol

 

Ripple-Carry Adder

 - Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a full adder

Carry-Lookahead Adder

- Compute carry out (C_{out}) for k -bit blocks using *generate* and *propagate* signals
- **Some definitions:**
 - Column i produces a carry out by either *generating* a carry out or *propagating* a carry in to the carry out
 - Generate (G_i) and propagate (P_i) signals for each column:
 - Column i will generate a carry out if A_i AND B_i are both 1.

$$G_i = A_i B_i$$

- Column i will propagate a carry in to the carry out if A_i OR B_i is 1.

$$P_i = A_i + B_i$$

- The carry out of column i (C_i) is:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

Carry-Lookahead Addition

- **Step 1:** Compute G_i and P_i for all columns
- **Step 2:** Compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate block

Carry-Lookahead Adder

- **Example:** 4-bit blocks ($G_{3:0}$ and $P_{3:0}$) :

$$G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0))$$

$$P_{3:0} = P_3 P_2 P_1 P_0$$



- **Generally,**

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} G_j))$$

$$P_{i:j} = P_i P_{i-1} P_{i-2} P_j$$

$$C_i = G_{i:j} + P_{i:j} C_{i-1}$$

32-bit CLA with 4-bit Blocks

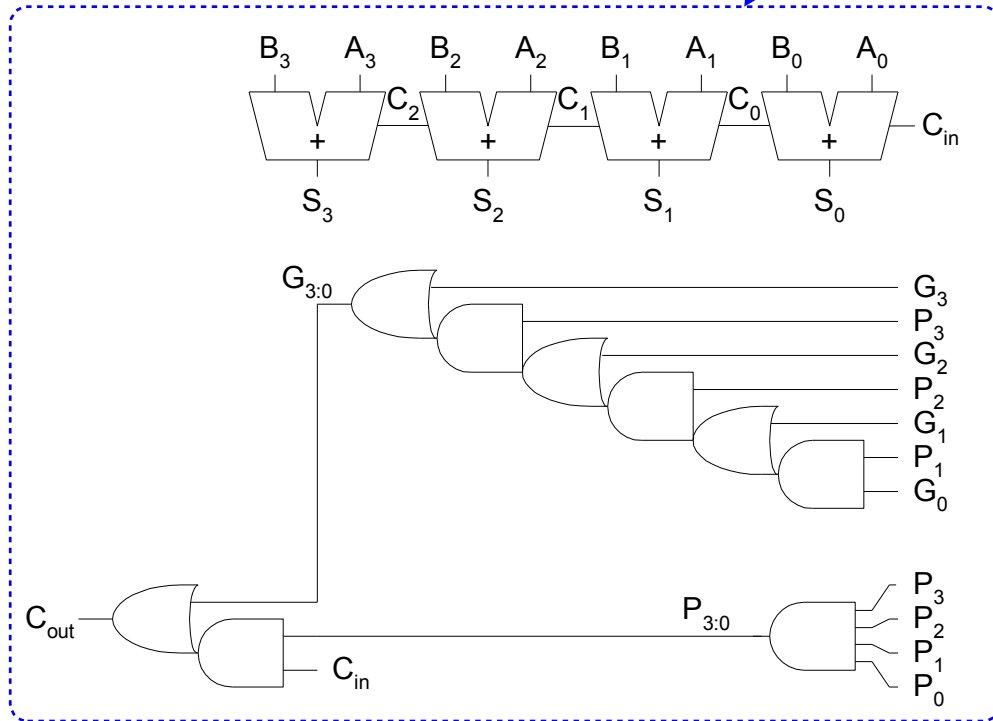 

Carry-Lookahead Adder Delay

For N -bit CLA with k -bit blocks:

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA}$$

- t_{pg} : delay to generate all P_i, G_i
- t_{pg_block} : delay to generate all P_{ij}, G_{ij}
- t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k -bit CLA block

An N -bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_i$$

- Computes G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages

Prefix Adder

- Carry in either *generated* in a column or *propagated* from a previous column.

- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}, P_{-1} = 0$$

- Carry in to column i = carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}$, $G_{1:-1}$, $G_{2:-1}$, $G_{3:-1}$, $G_{4:-1}$, $G_{5:-1}$, ... (called *prefixes*)

Prefix Adder


- Generate and propagate signals for a block spanning bits $i:j$:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$




$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry

Prefix Adder Schematic

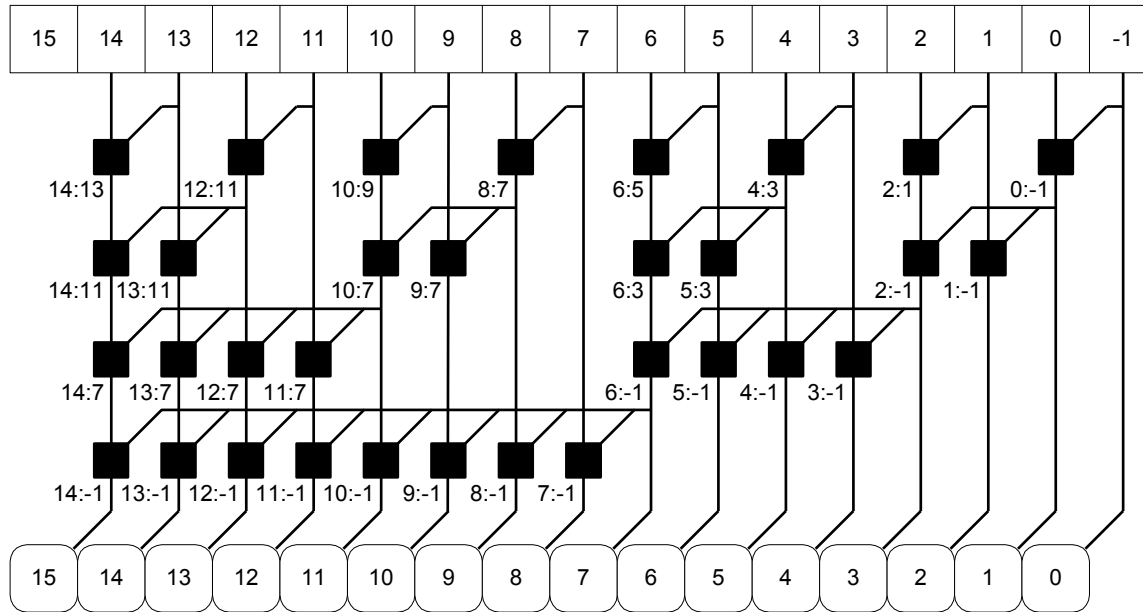

Legend

   

Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N (t_{pg_prefix}) + t_{XOR}$$

- t_{pg} : delay to produce $P_i G_i$ (AND or OR gate)
- t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

Adder Delay Comparisons

Compare delay of: 32-bit ripple-carry, carry-lookahead, and prefix adders

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps

Adder Delay Comparisons

Compare delay of: 32-bit ripple-carry, carry-lookahead, and prefix adders

- CLA has 4-bit blocks
- 2-input gate delay = 100 ps; full adder delay = 300 ps


$$\begin{aligned} t_{\text{ripple}} &= Nt_{FA} = 32(300 \text{ ps}) \\ &= \mathbf{9.6 \text{ ns}} \end{aligned}$$

$$\begin{aligned} t_{CLA} &= t_{pg} + t_{pg_block} + (N/k - 1)t_{AND_OR} + kt_{FA} \\ &= [100 + 600 + (7)200 + 4(300)] \text{ ps} \\ &= \mathbf{3.3 \text{ ns}} \end{aligned}$$


$$\begin{aligned} t_{PA} &= t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR} \\ &= [100 + \log_2 32(200) + 100] \text{ ps} \\ &= \mathbf{1.2 \text{ ns}} \end{aligned}$$

Subtractor

Symbol

 


Implementation

 


Comparator: Equality


Symbol

 


Implementation

 

Comparator: Less Than

 


Arithmetic Logic Unit (ALU)

 


$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

ALU Design

 


F _{2:0}	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & ~B
101	A ~B
110	A - B
111	SLT

Set Less Than (SLT) Example

 

- Configure 32-bit ALU for SLT operation: $A = 25$ and $B = 32$

Set Less Than (SLT) Example

 

- Configure 32-bit ALU for SLT operation: $A = 25$ and $B = 32$
 - $A < B$, so Y should be 32-bit representation of 1 (0x00000001)
 - $F_{2:0} = 111$
 - $F_2 = 1$ (adder acts as subtracter), so $25 - 32 = -7$
 - -7 has 1 in the most significant bit ($S_{31} = 1$)
 - $F_{1:0} = 11$ multiplexer selects $Y = S_{31}$ (zero extended) = 0x00000001.



Shifters

- **Logical shifter:** shifts value to left or right and fills empty spaces with 0's
 - Ex: 11001 >> 2 =
 - Ex: 11001 << 2 =
- **Arithmetic shifter:** same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (msb).
 - Ex: 11001 >>> 2 =
 - Ex: 11001 <<< 2 =
- **Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - Ex: 11001 ROR 2 =
 - Ex: 11001 ROL 2 =

Shifters

- **Logical shifter:**
 - Ex: 11001 >> 2 = 00110
 - Ex: 11001 << 2 = 00100
- **Arithmetic shifter:**
 - Ex: 11001 >>> 2 = 11110
 - Ex: 11001 <<< 2 = 00100
- **Rotator:**
 - Ex: 11001 ROR 2 = 01110
 - Ex: 11001 ROL 2 = 00111

Shifter Design

  

Shifters as Multipliers, Dividers

- $A \ll N = A \times 2^N$
 - **Example:** $00001 \ll 2 = 00100$ ($1 \times 2^2 = 4$)
 - **Example:** $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)
- $A \gg N = A \div 2^N$
 - **Example:** $01000 \gg 2 = 00010$ ($8 \div 2^2 = 2$)
 - **Example:** $10000 \gg 2 = 11100$ ($-16 \div 2^2 = -4$)

Multipliers

- **Partial products** formed by multiplying a single digit of the multiplier with multiplicand
- **Shifted** partial products **summed** to form Mlt

Decimal

$$\begin{array}{r}
 230 \\
 \times 42 \\
 \hline
 460 \\
 + 920 \\
 \hline
 9660
 \end{array}$$

$$230 \times 42 = 9660$$

multiplicand
 multiplier
 partial
 products


result

Binary


$$\begin{array}{r}
 0101 \\
 \times 0111 \\
 \hline
 0101 \\
 0101 \\
 0101 \\
 + 0000 \\
 \hline
 0100011
 \end{array}$$

$$5 \times 7 = 35$$


4 x 4 Multiplier

 


 
$$\begin{array}{r}
 \\
 \\
 \\
 \\
 + \\
 \hline
 P_7
 \end{array}$$



4 x 4 Divider

 

Legend

  

$$A/B = Q + R/B$$

Algorithm:

$$R' = 0$$

for $i = N-1$ to 0

$$R = \{R' \ll 1, A_i\}$$

$$D = R - B$$

if $D < 0$, $Q_i = 0$, $R' = R$

else $Q_i = 1$, $R' = D$

$$R' = R$$

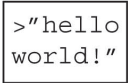


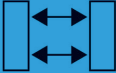
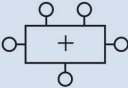
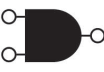
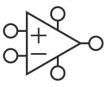


Chapter 7

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 7 :: Topics

- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Exceptions
- Advanced Microarchitecture

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- **Processor:**
 - **Datapath:** functional blocks
 - **Control:** control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor Performance

- Program execution time

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- Definitions:
 - CPI: Cycles/instruction
 - clock period: seconds/cycle
 - IPC: instructions/cycle = IPC
- Challenge is to satisfy constraints of:
 - Cost
 - Power
 - Performance


MIPS Processor

- Consider subset of MIPS instructions:
 - R-type instructions: `and`, `or`, `add`, `sub`, `slt`
 - Memory instructions: `lw`, `sw`
 - Branch instructions: `beq`

Architectural State

- Determines everything about a processor:
 - PC
 - 32 registers (and a few extra ones we'll ignore here)
 - Memory

MIPS State Elements

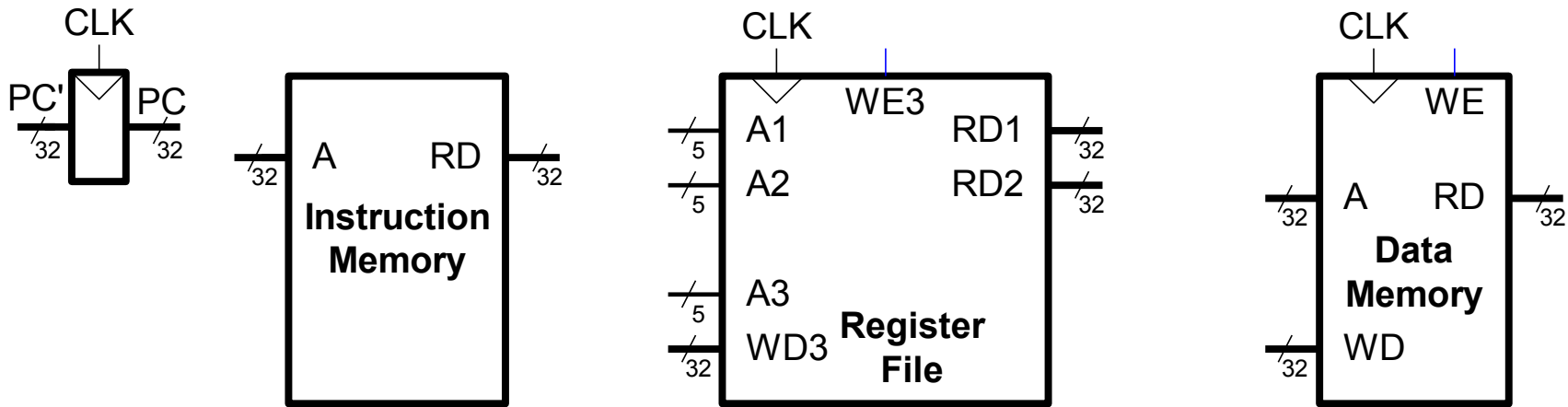



Single-Cycle MIPS Processor

- Datapath
- Control

Single-Cycle Datapath: 1_w fetch


STEP 1: Fetch instruction

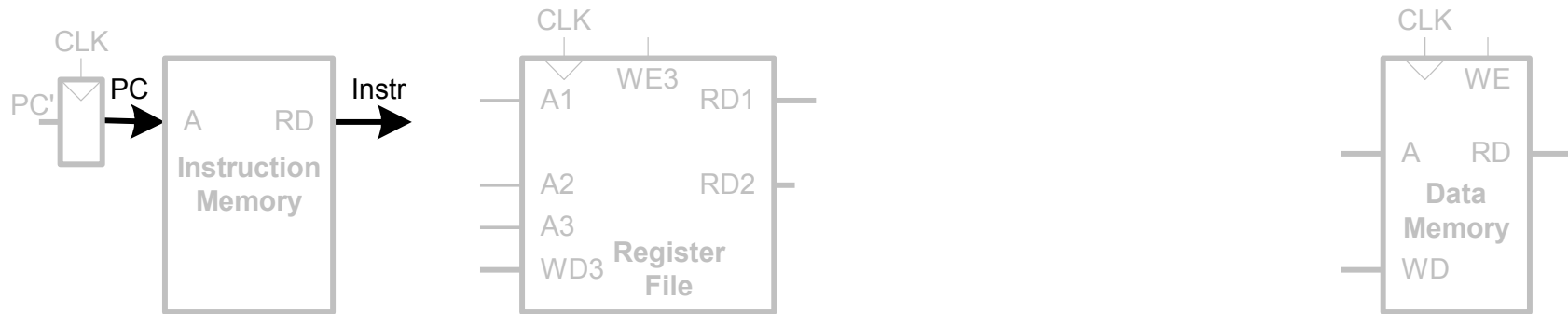

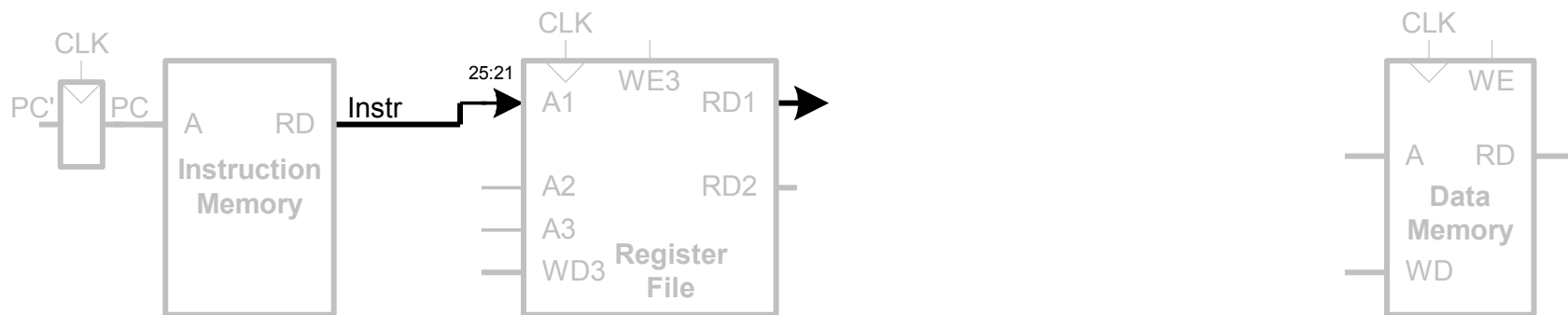Single-Cycle Datapath: \perp_w Register Read**STEP 2:** Read source operands from RF


Single-Cycle Datapath: 1_W Immediate

STEP 3: Sign-extend the immediate

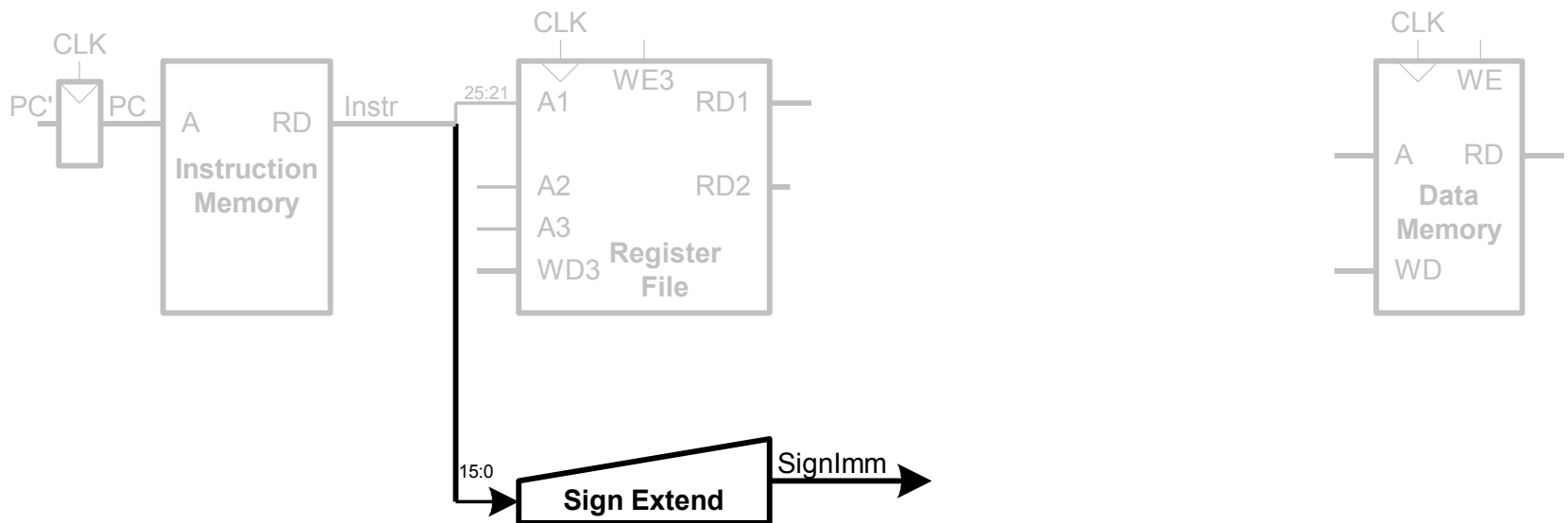


Single-Cycle Datapath: \perp_w address

STEP 4: Compute the memory address

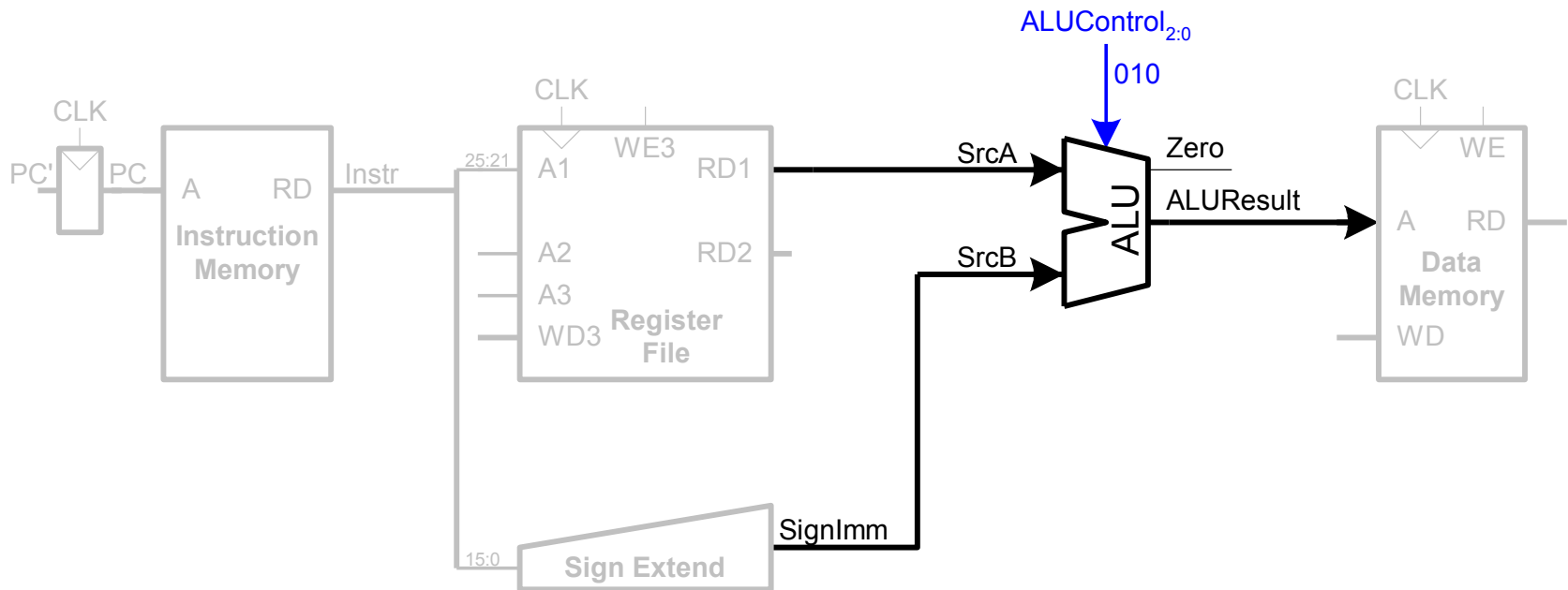


Single-Cycle Datapath: 1_W Memory Read

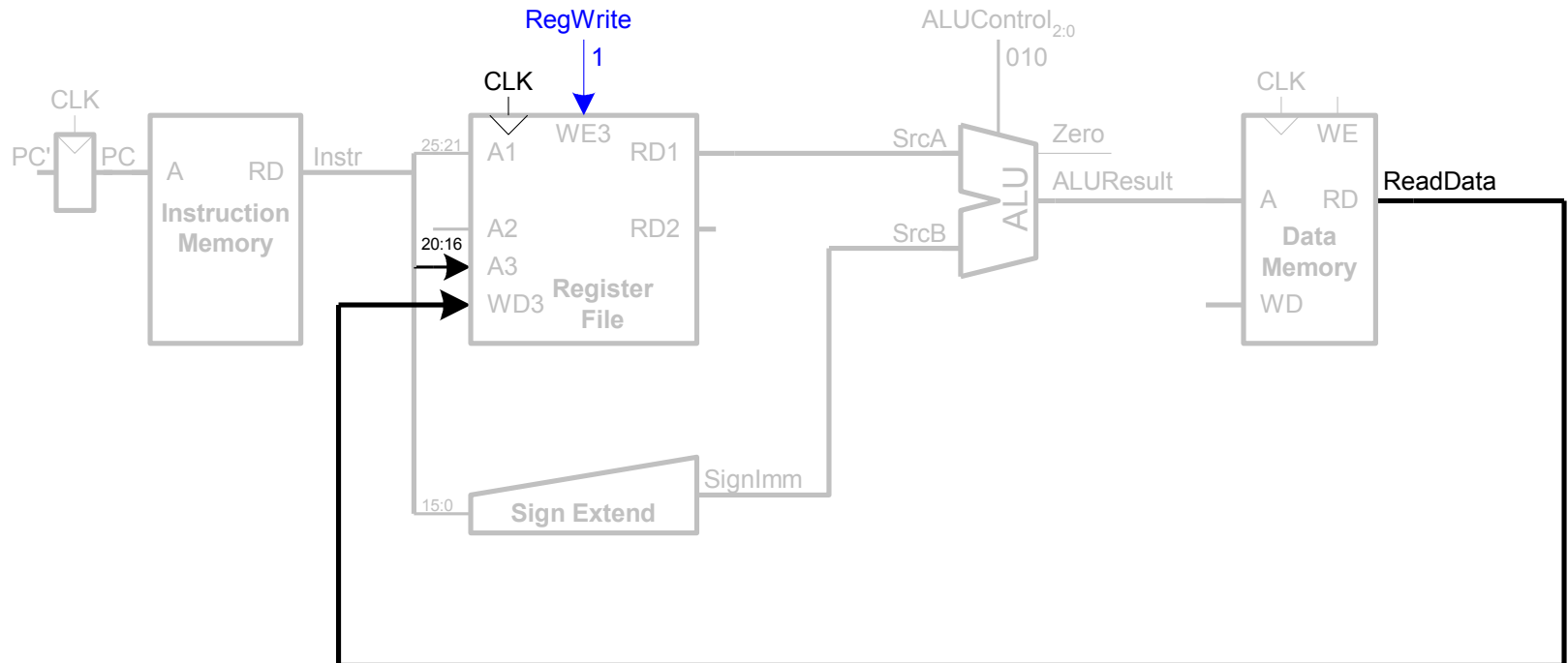- **STEP 5:** Read data from memory and write it back to register file




Single-Cycle Datapath: 1_W PC Increment

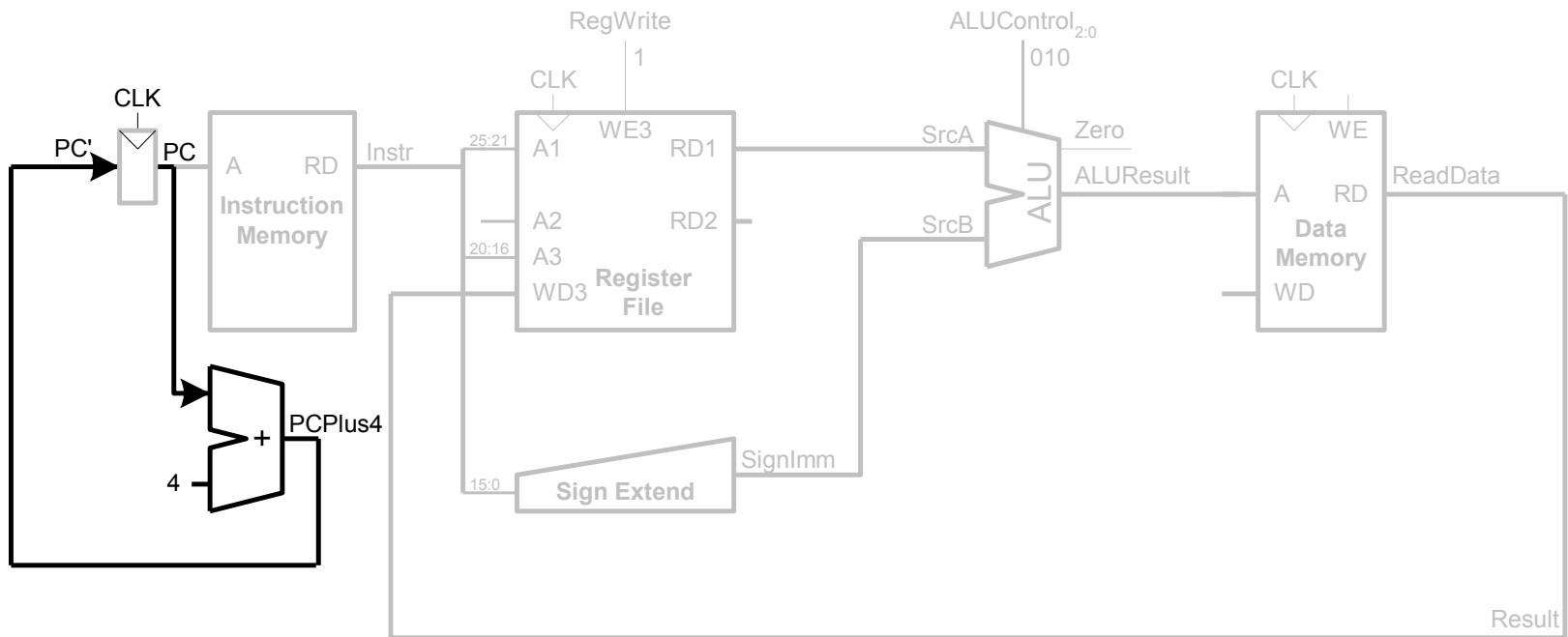STEP 6: Determine address of next instruction




Single-Cycle Datapath: sw

Write data in rt to memory

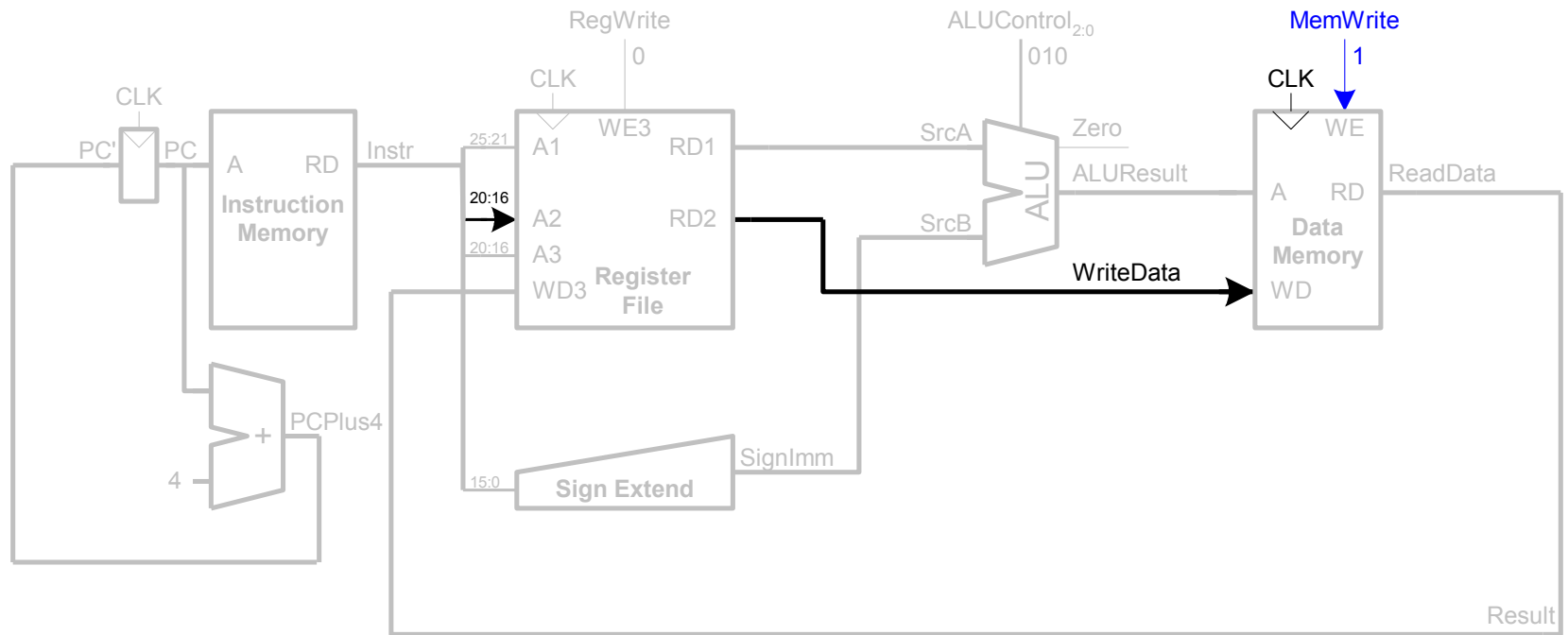

Single-Cycle Datapath: R-Type

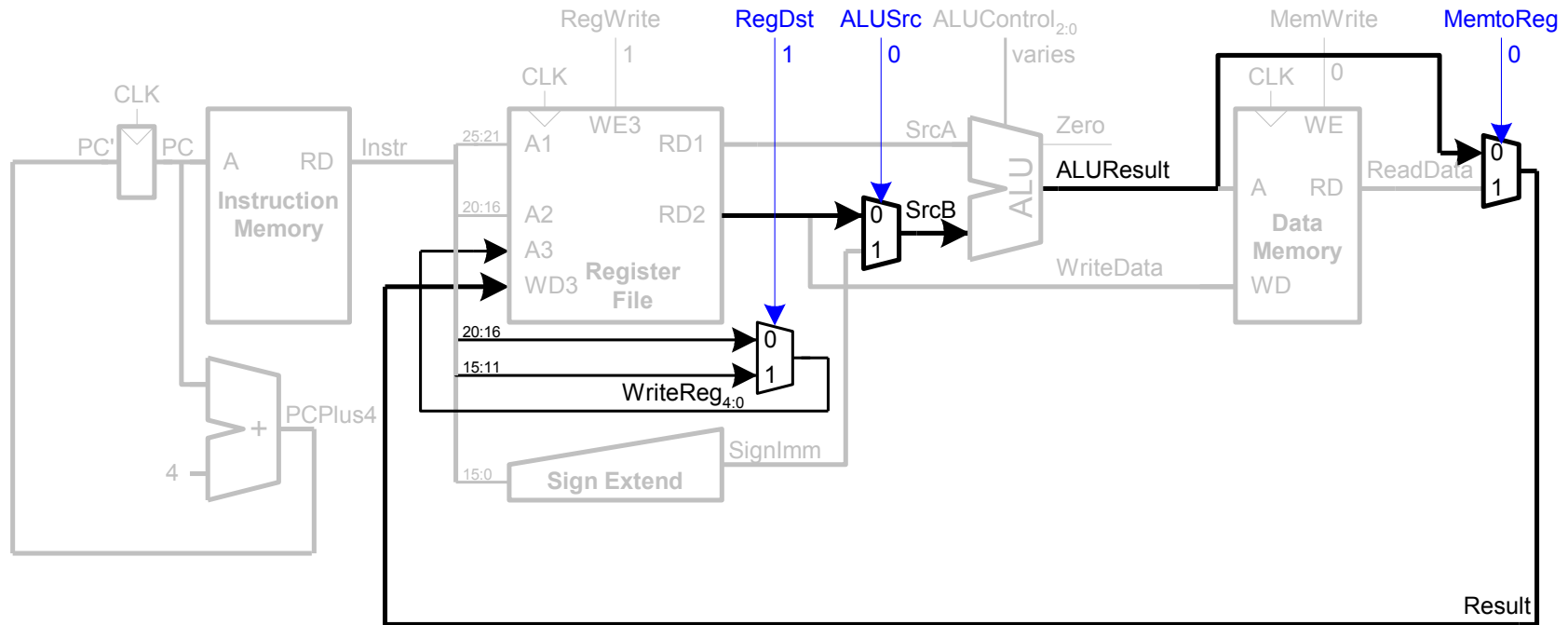
- Read from *rs* and *rt*
- Write *ALUResult* to register file
- Write to *rd* (instead of *rt*)




Single-Cycle Datapath: beq

- Determine whether values in `rs` and `rt` are equal
- Calculate branch target address:

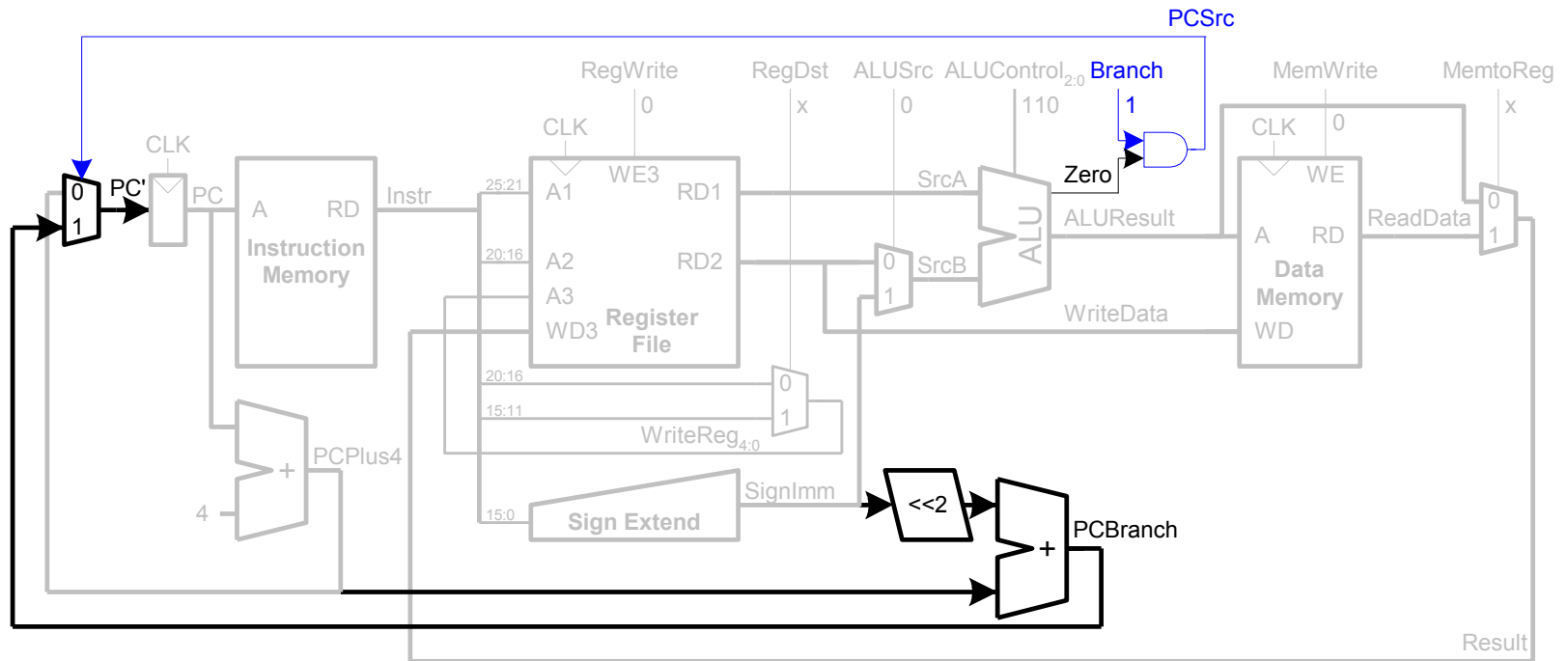
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$




Single-Cycle Processor

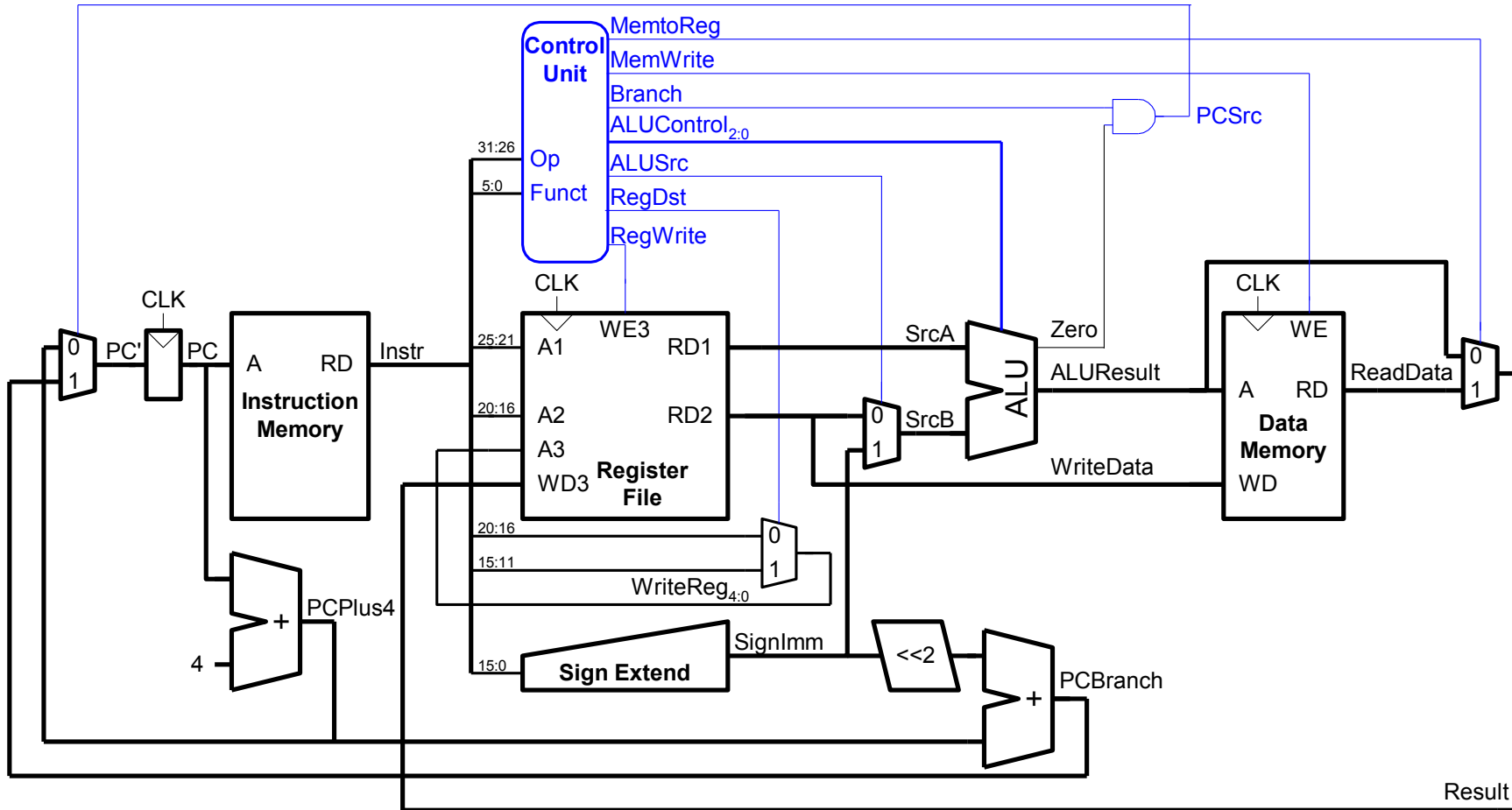

Single-Cycle Control

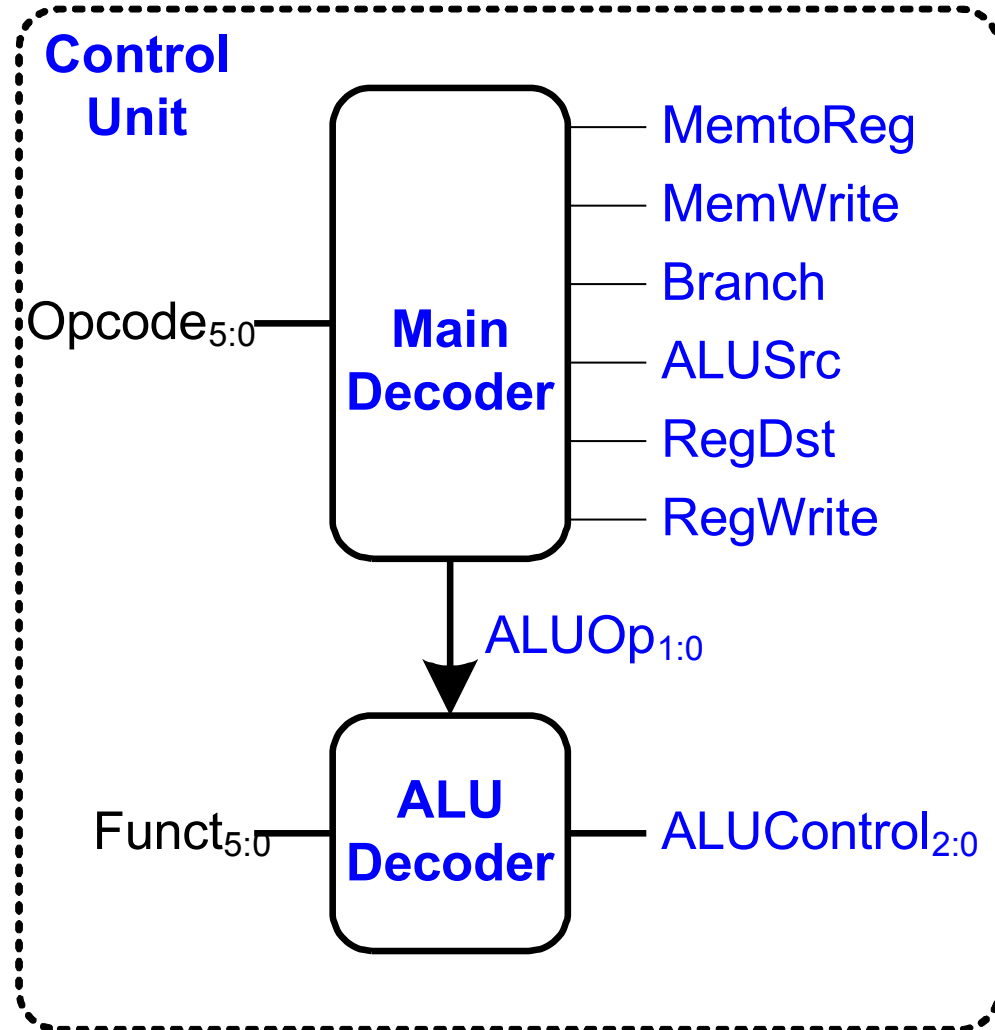


Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Review: ALU

 


Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Control Unit Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

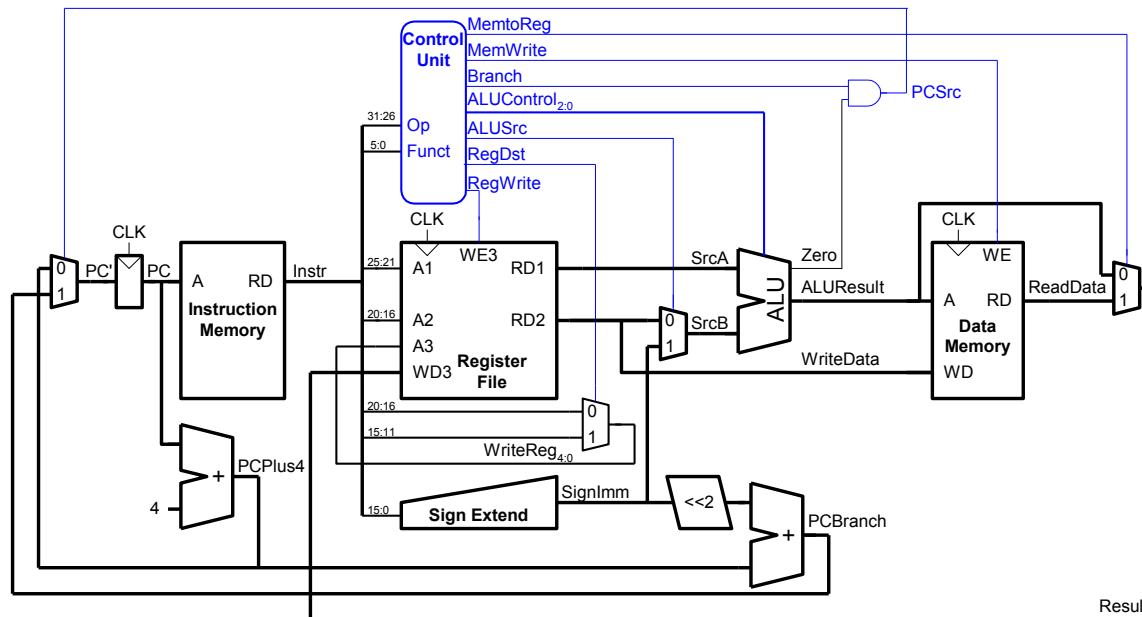


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Single-Cycle Datapath: or

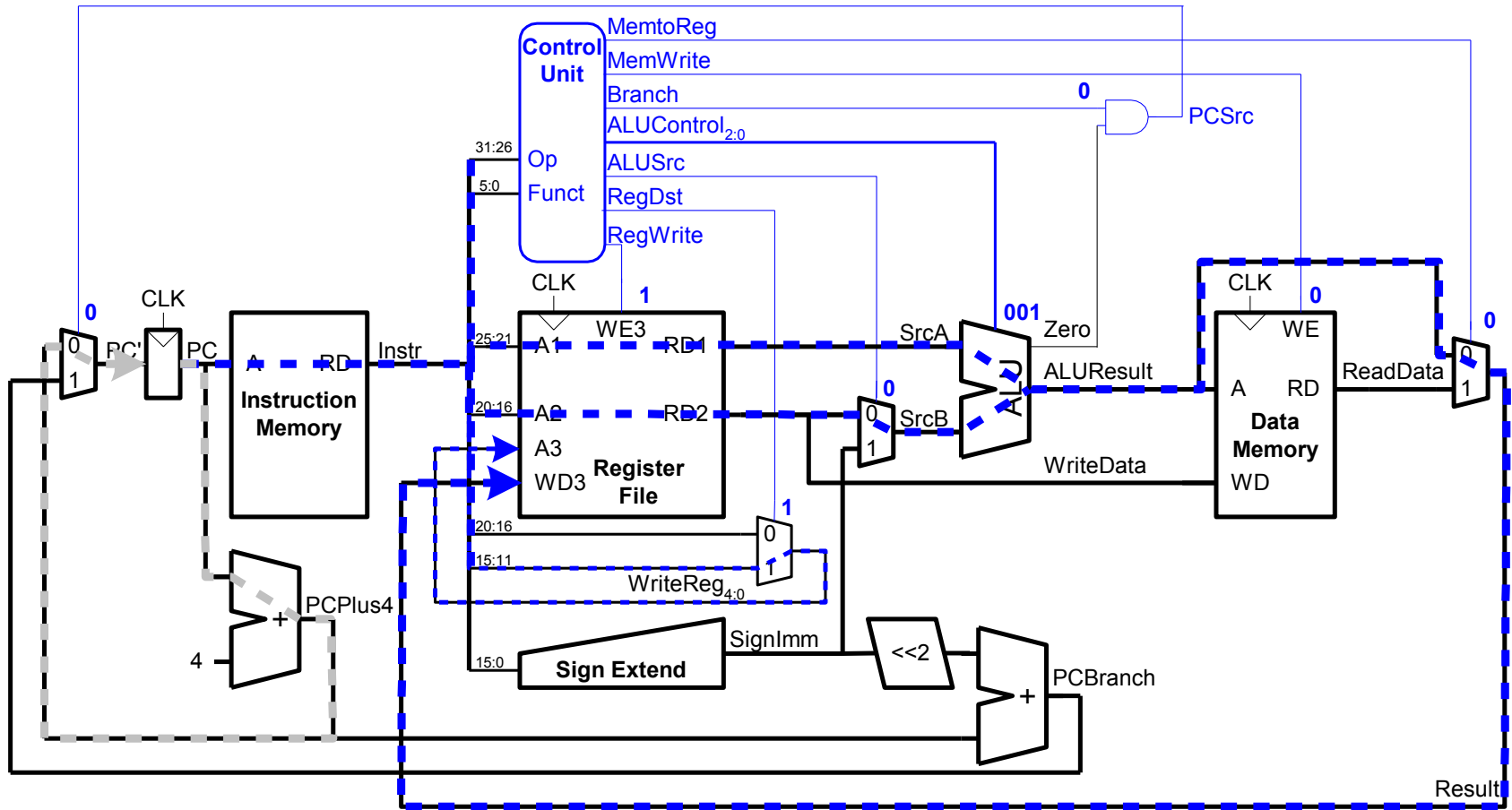

Extended Functionality: addi

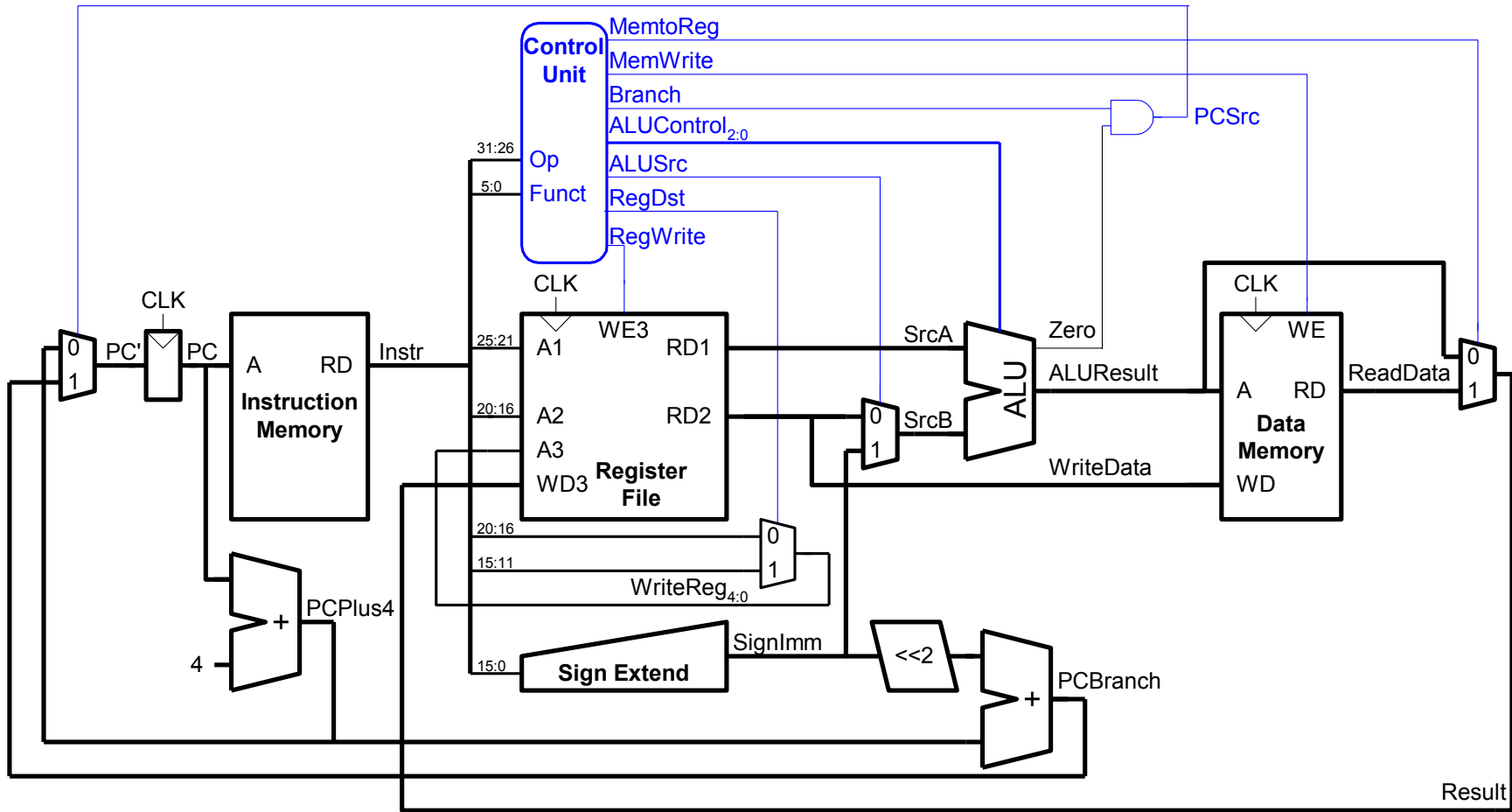

No change to datapath


Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000							

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Extended Functionality: j

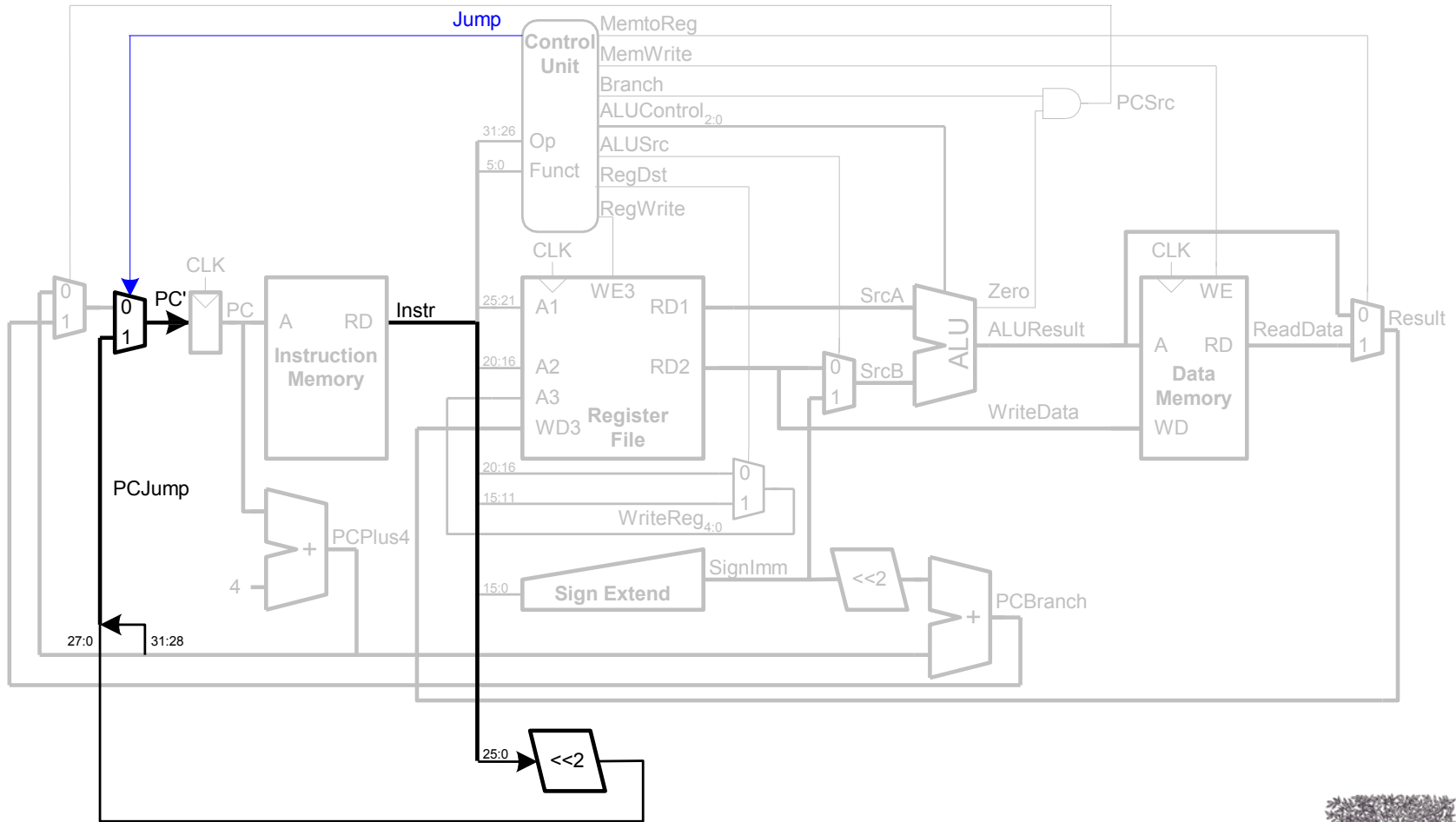

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100	0	X	X	X	0	X	XX	1


Review: Processor Performance

Program Execution Time

$$= (\# \text{instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_c$$

Single-Cycle Performance

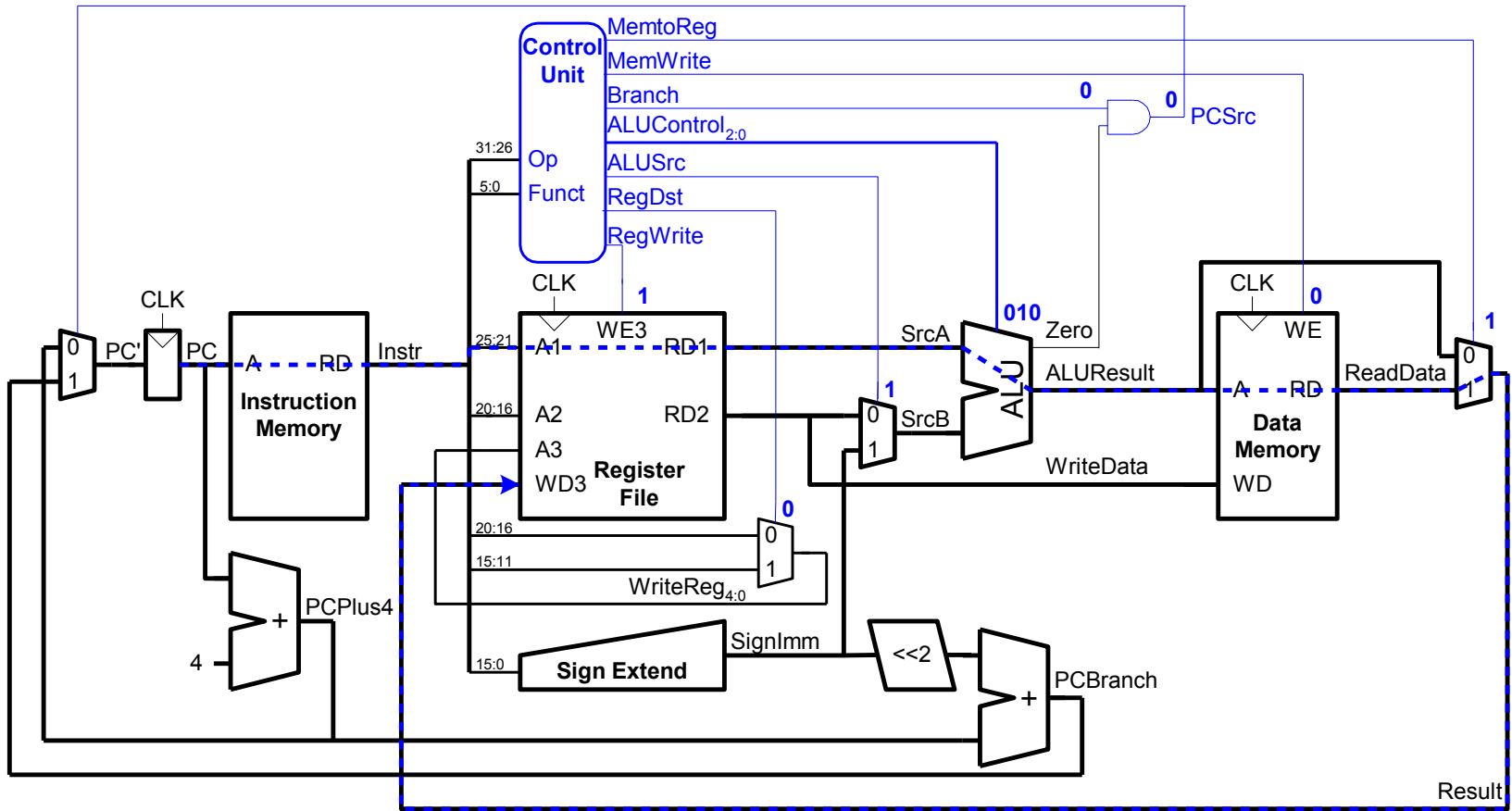

T_C limited by critical path (1w)



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file

- $T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c = ?$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}
 T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\
 &= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\
 &= 925 \text{ ps}
 \end{aligned}$$

Single-Cycle Performance Example

Program with 100 billion instructions:


$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= \mathbf{92.5 \text{ seconds}}\end{aligned}$$

Multicycle MIPS Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (1_w)
 - 2 adders/ALUs & 2 memories
- **Multicycle:**
 - + higher clock speed
 - + simpler instructions run faster
 - + reuse expensive hardware on multiple cycles
 - sequencing overhead paid many times
- **Same design steps: datapath & control**


Multicycle State Elements

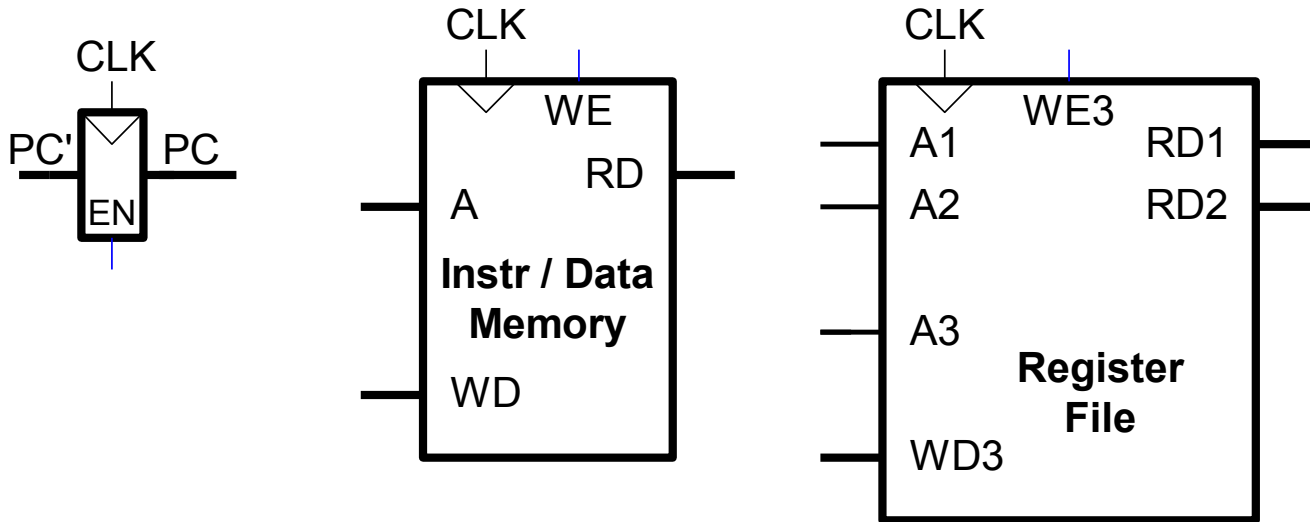- Replace Instruction and Data memories with a single unified memory – more realistic




Multicycle Datapath: Instruction Fetch

STEP 1: Fetch instruction

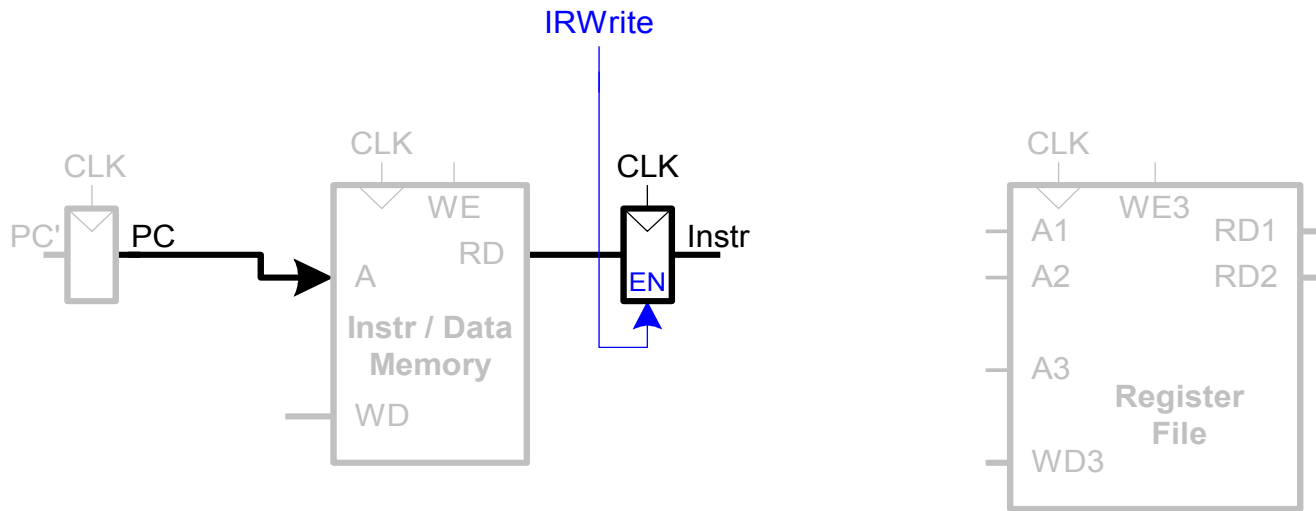


Multicycle Datapath: 1_w Register

STEP 2a: Read source operands from RF

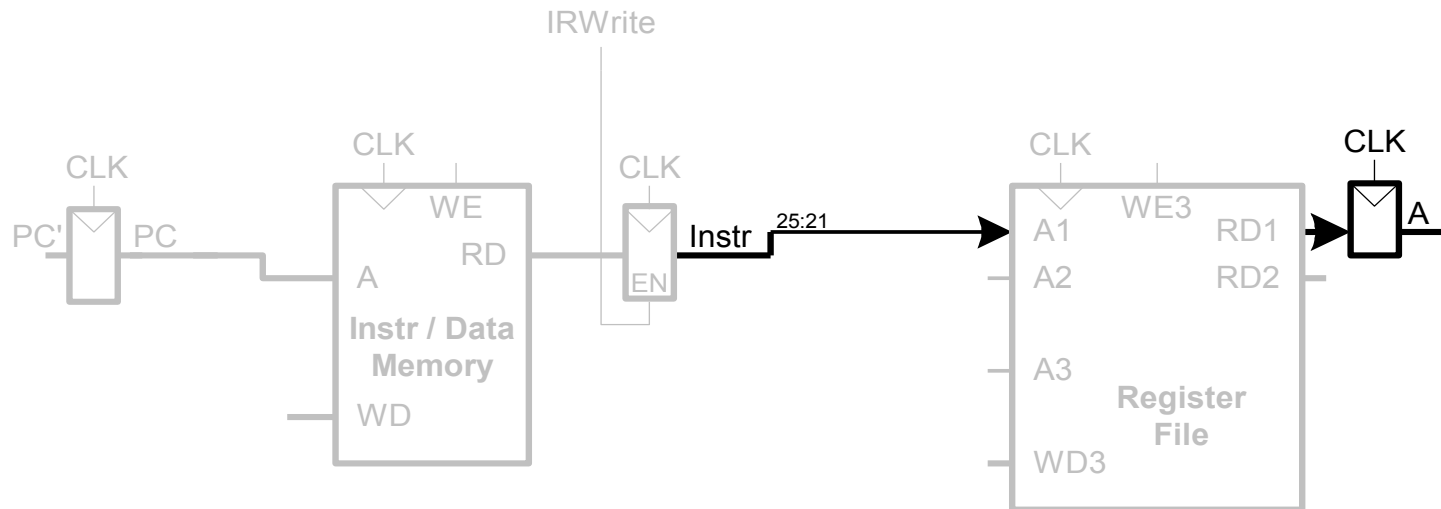


Multicycle Datapath: 1_w Immediate

STEP 2b: Sign-extend the immediate

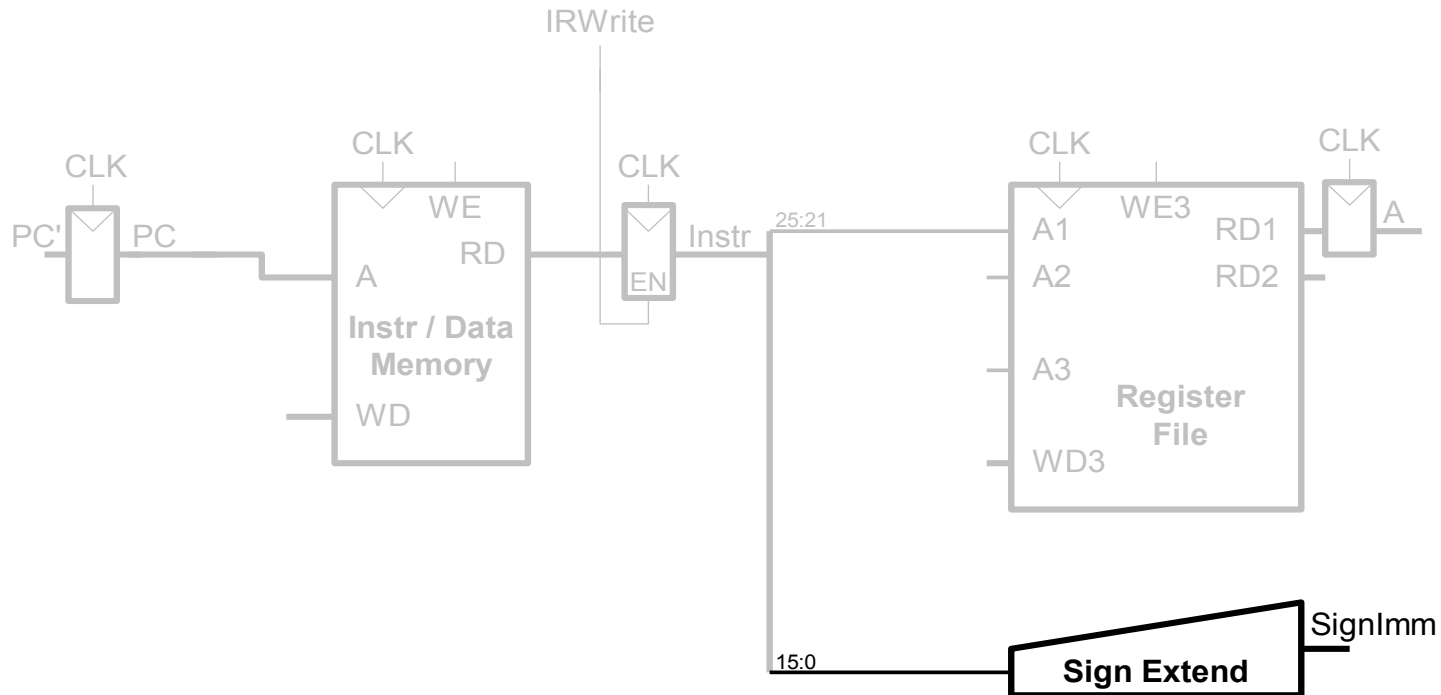


Multicycle Datapath: 1_w Address

STEP 3: Compute the memory address

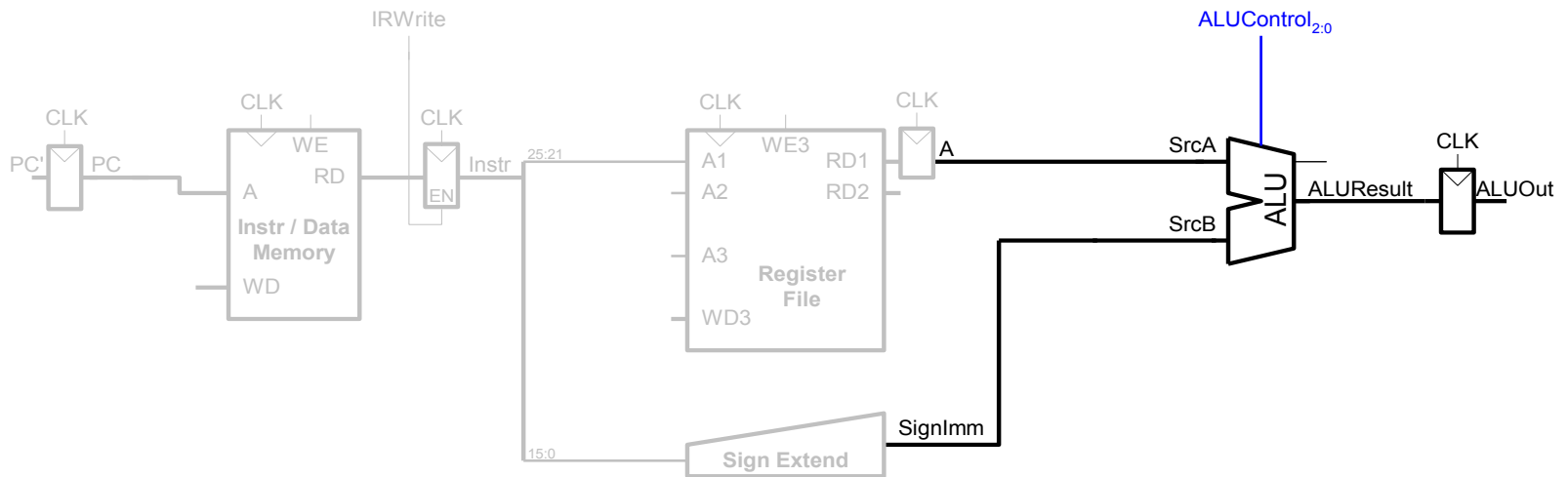


Multicycle Datapath: 1_W Memory Read

STEP 4: Read data from memory

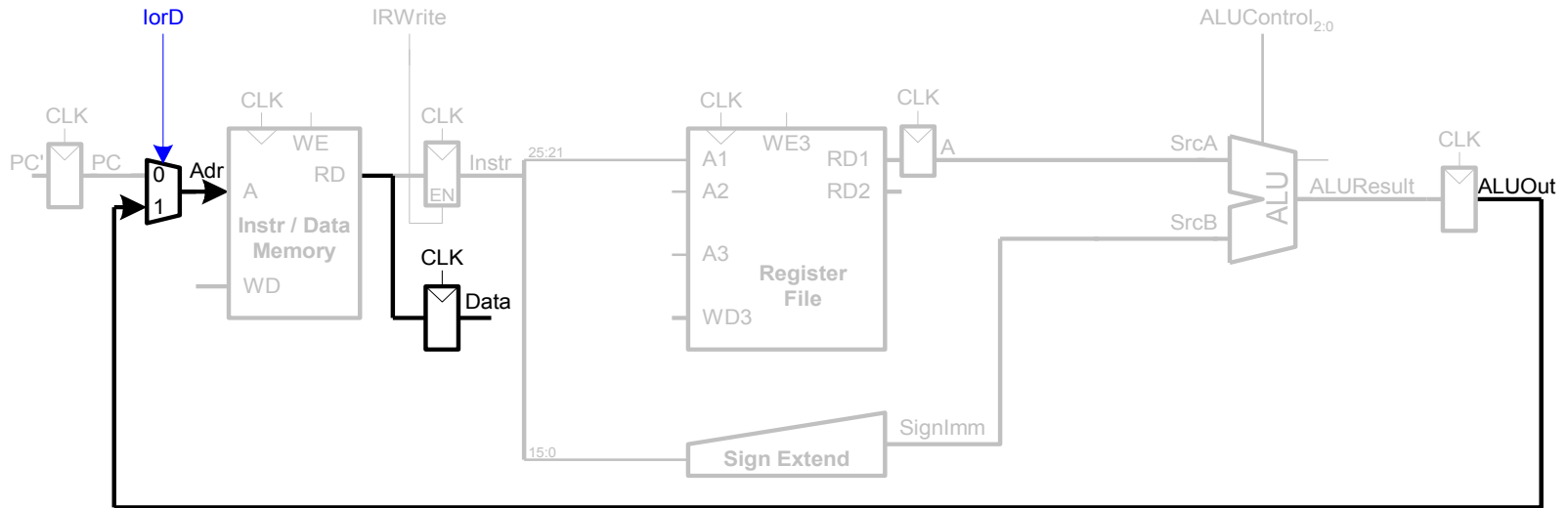


Multicycle Datapath: 1_W Write Register

STEP 5: Write data back to register file

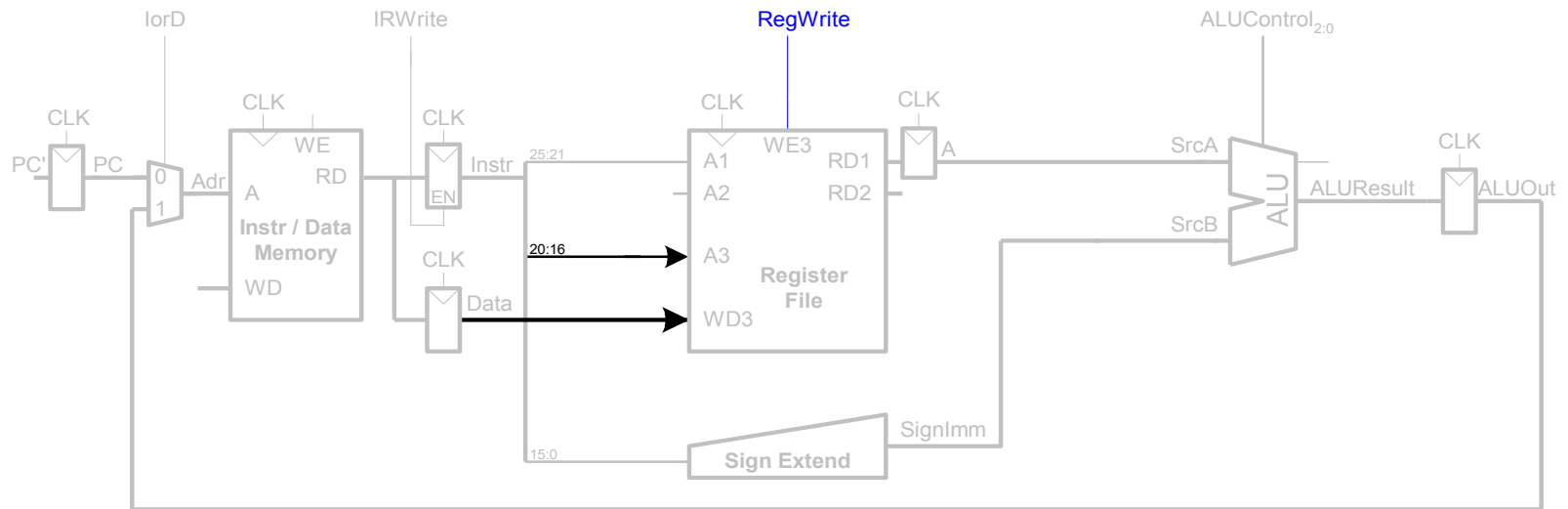


Multicycle Datapath: Increment PC

STEP 6: Increment PC

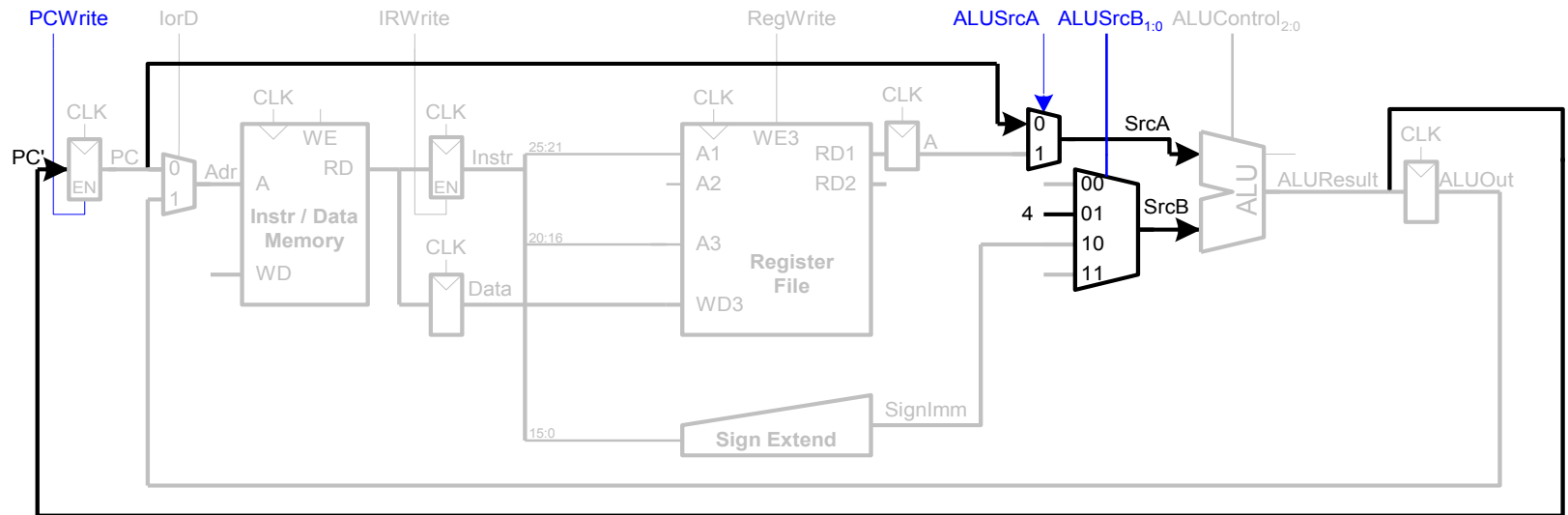


Multicycle Datapath: sw

Write data in `rt` to memory

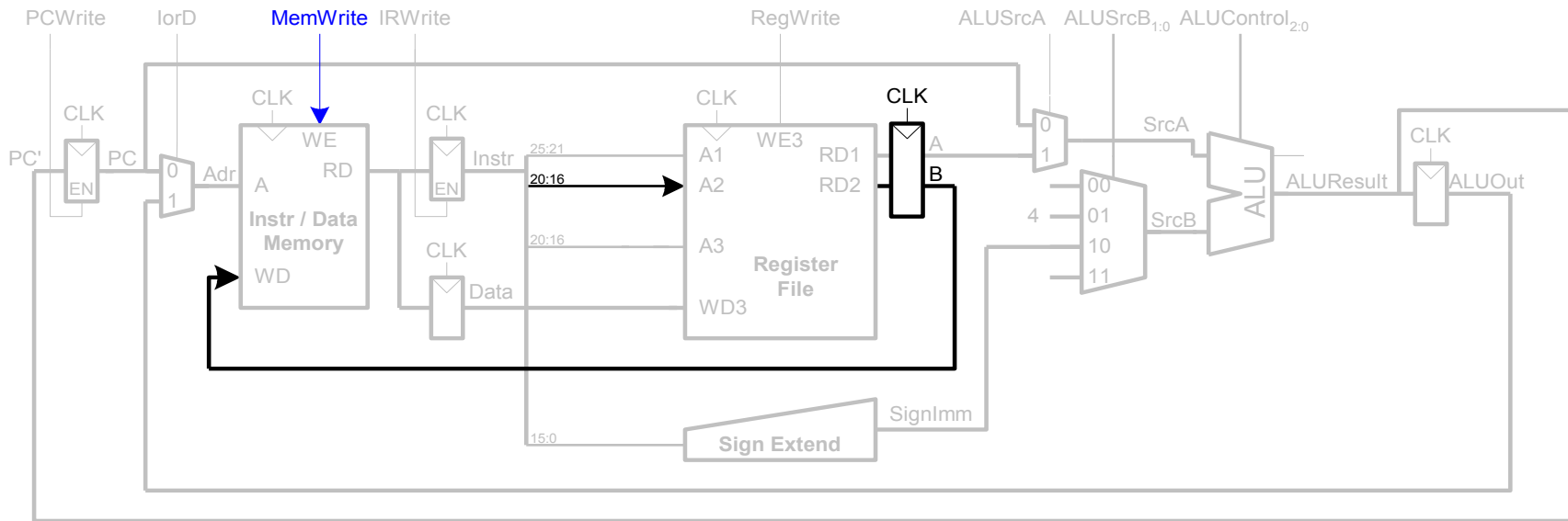


Multicycle Datapath: R-Type

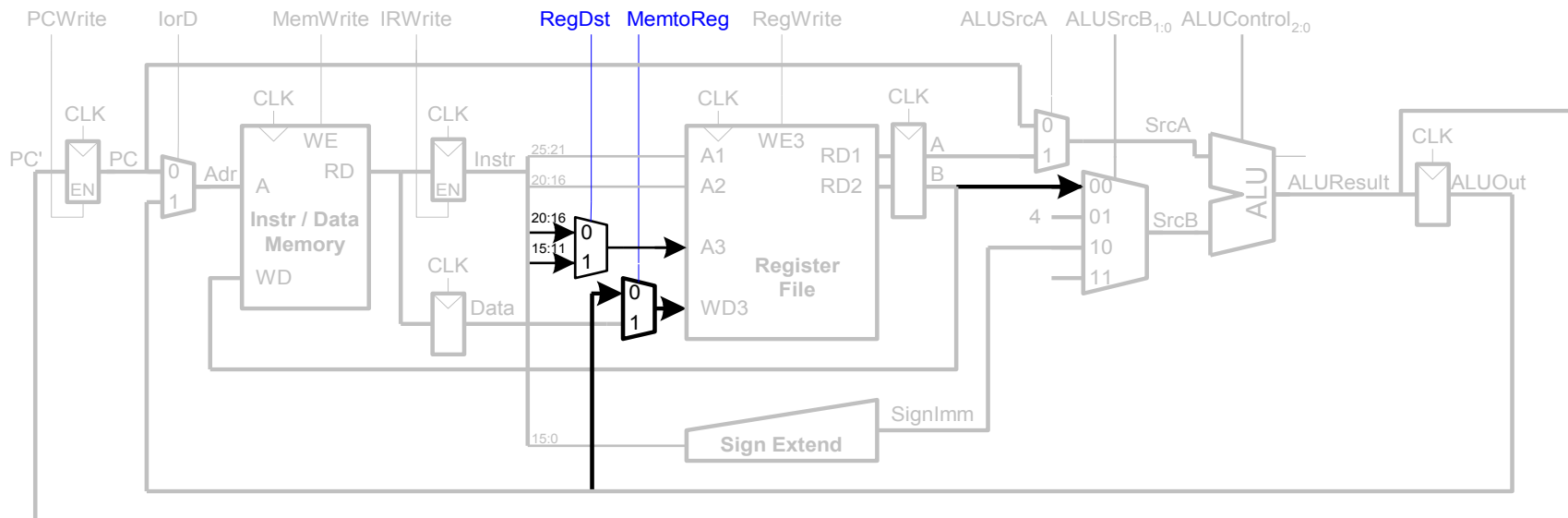
- Read from rs and rt
- Write $ALUResult$ to register file
- Write to rd (instead of rt)





Multicycle Processor

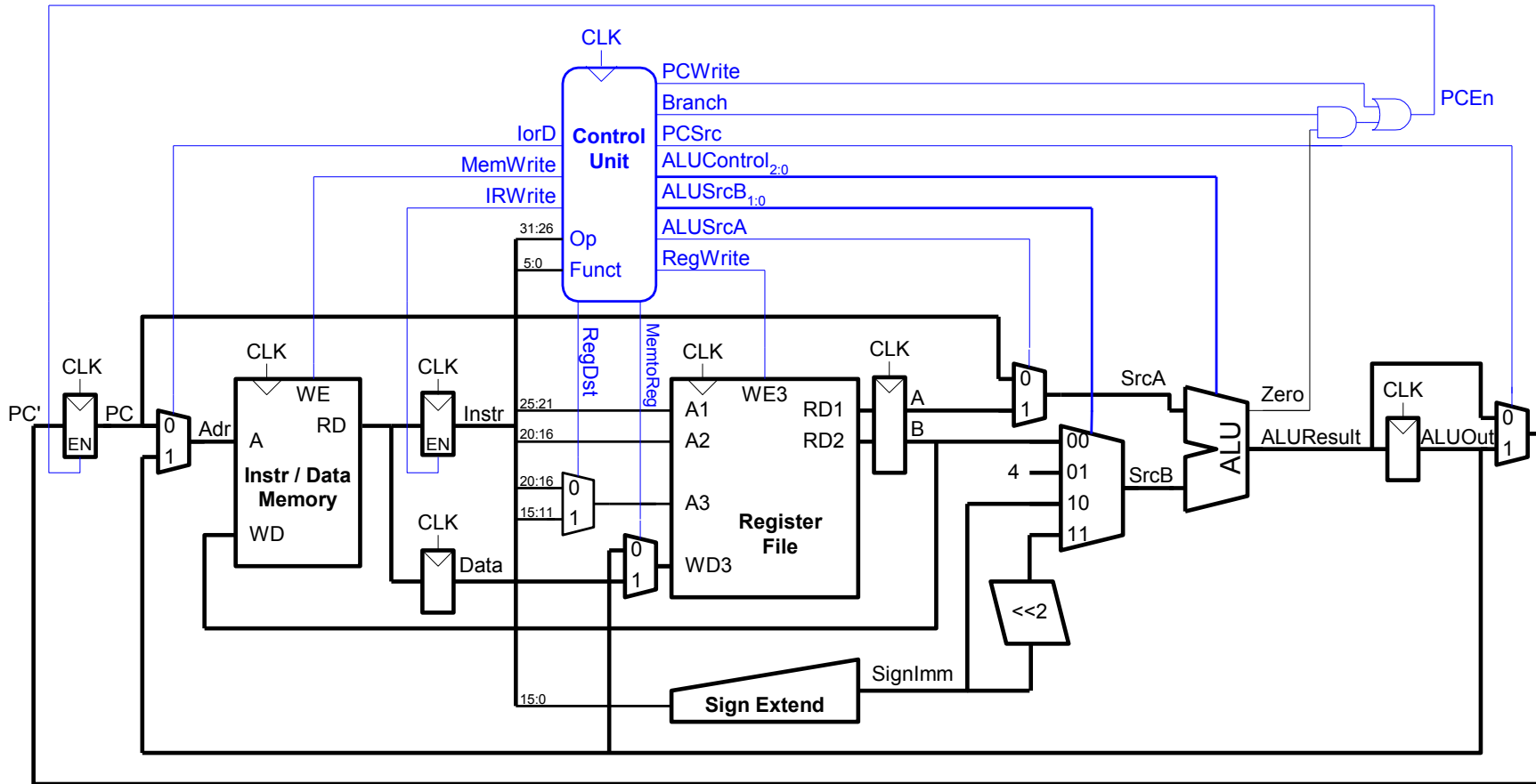

Multicycle Control

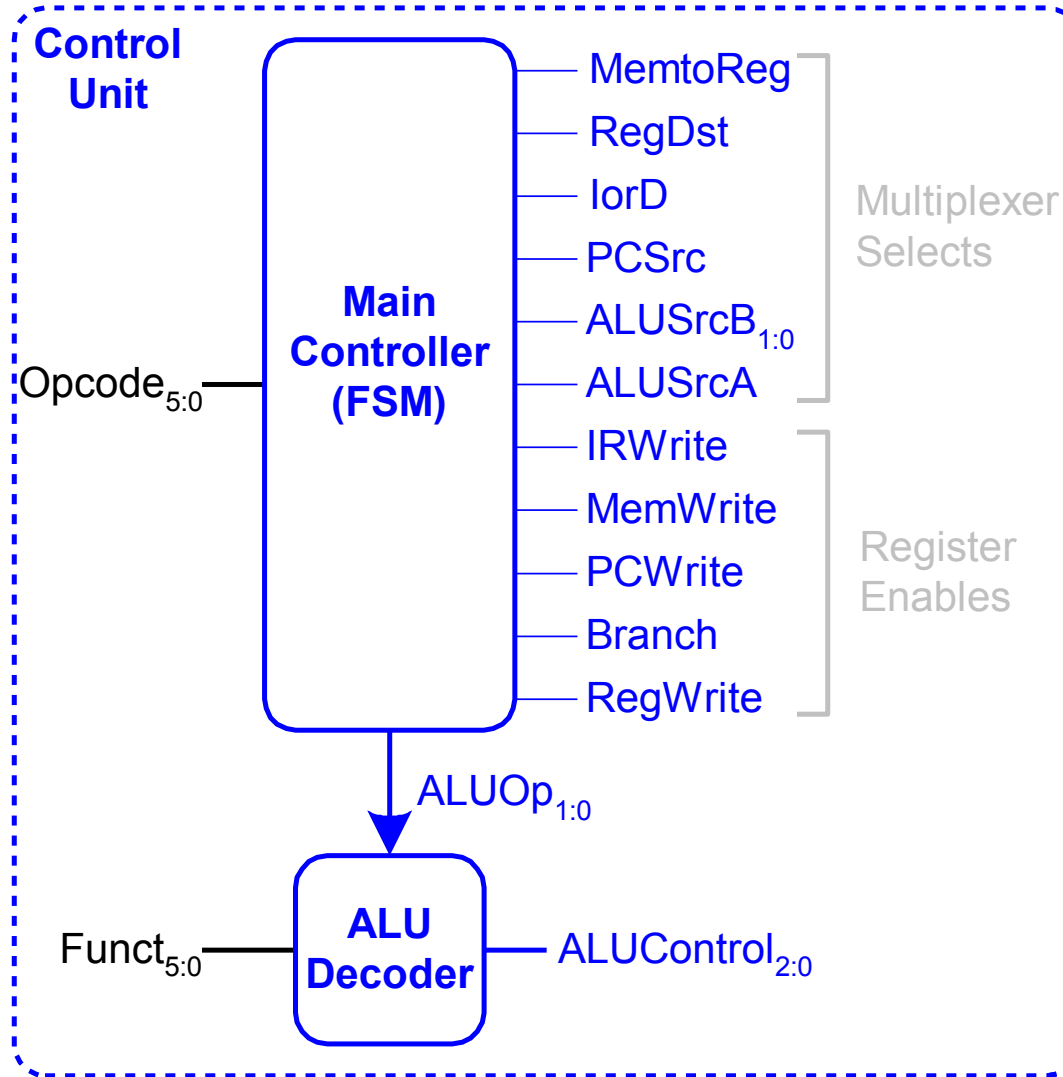

Main Controller FSM: Fetch

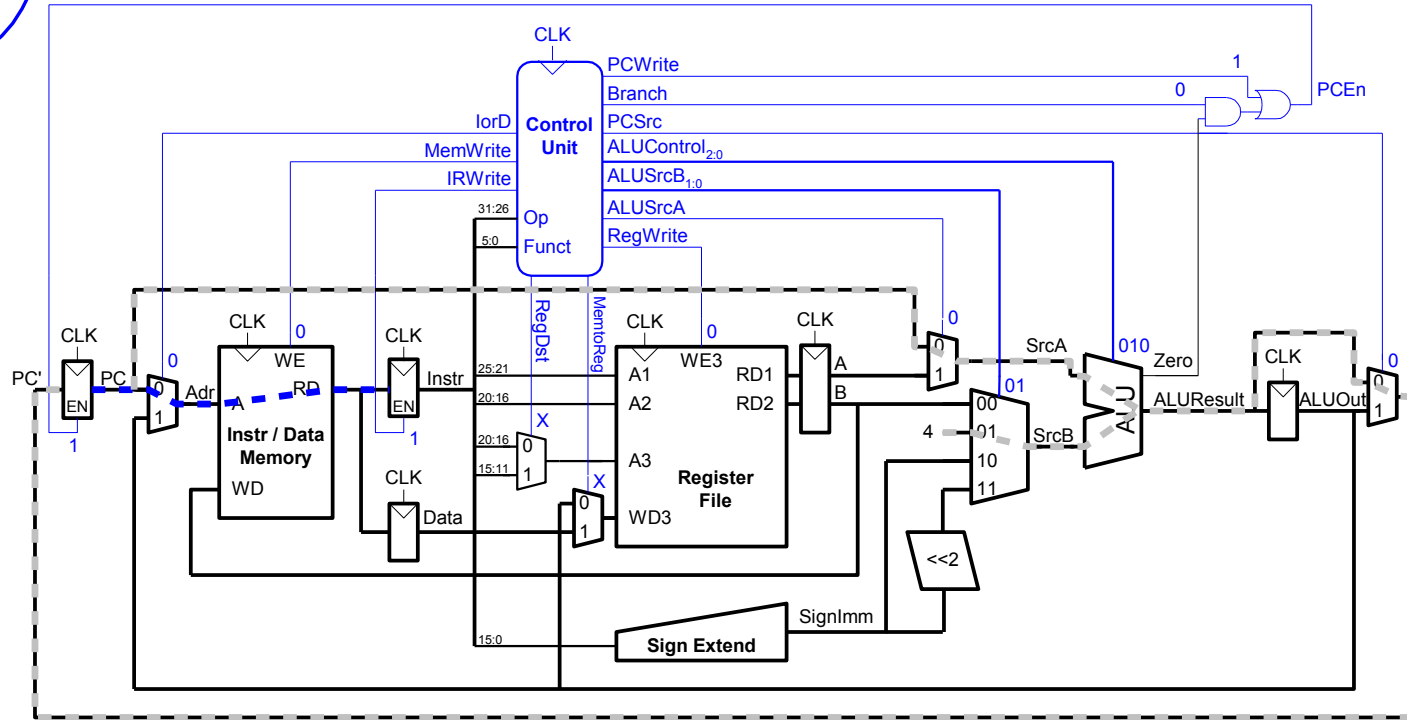 


Main Controller FSM: Fetch



S0: Fetch

Reset

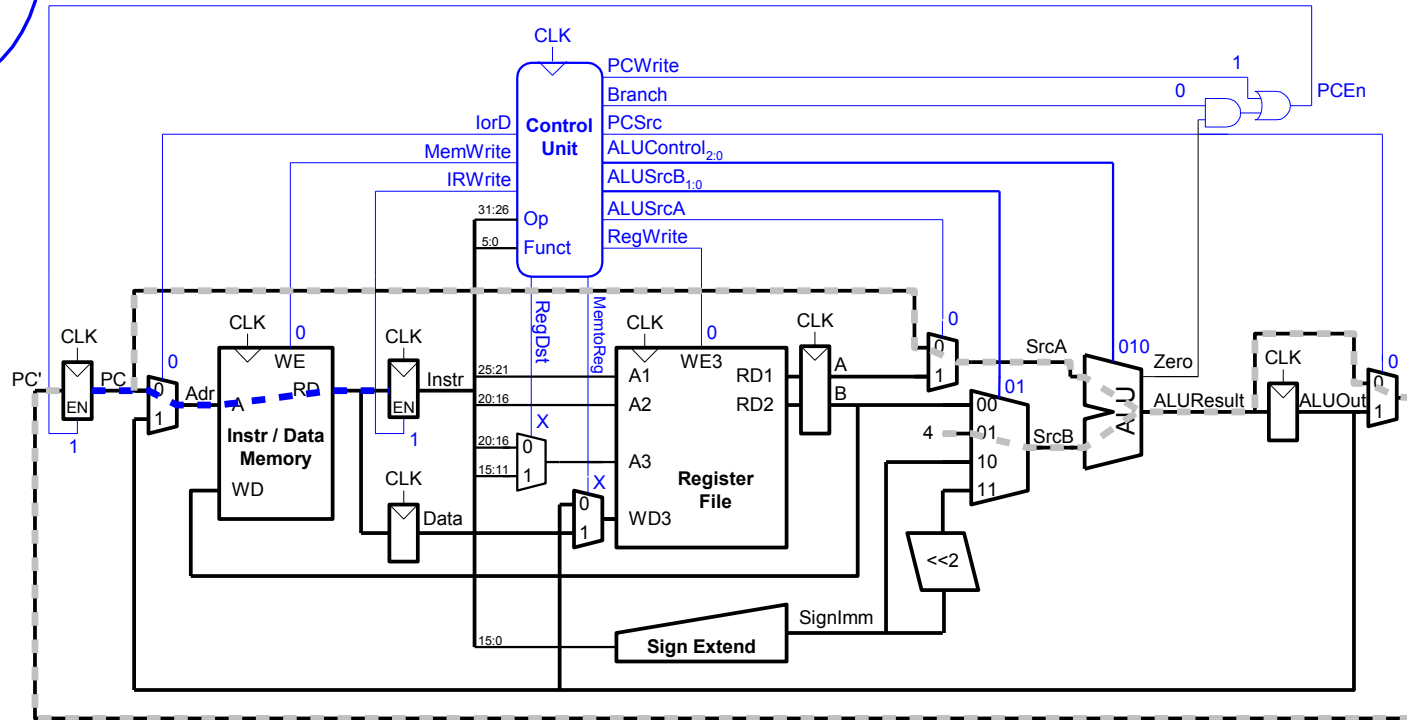
- lrd = 0
- AluSrcA = 0
- ALUSrcB = 01
- ALUOp = 00
- PCSrc = 0
- IRWrite
- PCWrite




Main Controller FSM: Decode

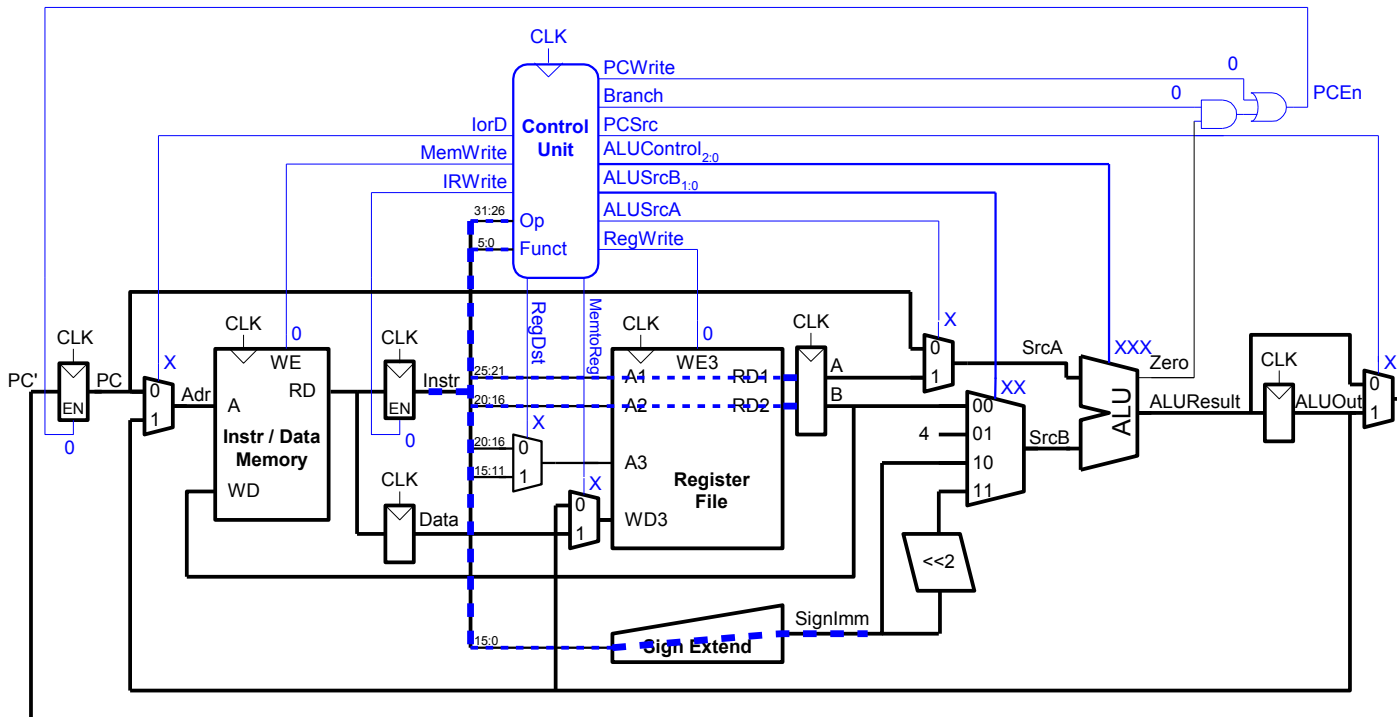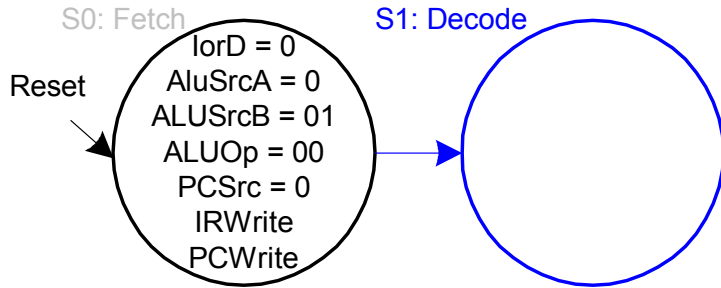


Main Controller FSM: Address

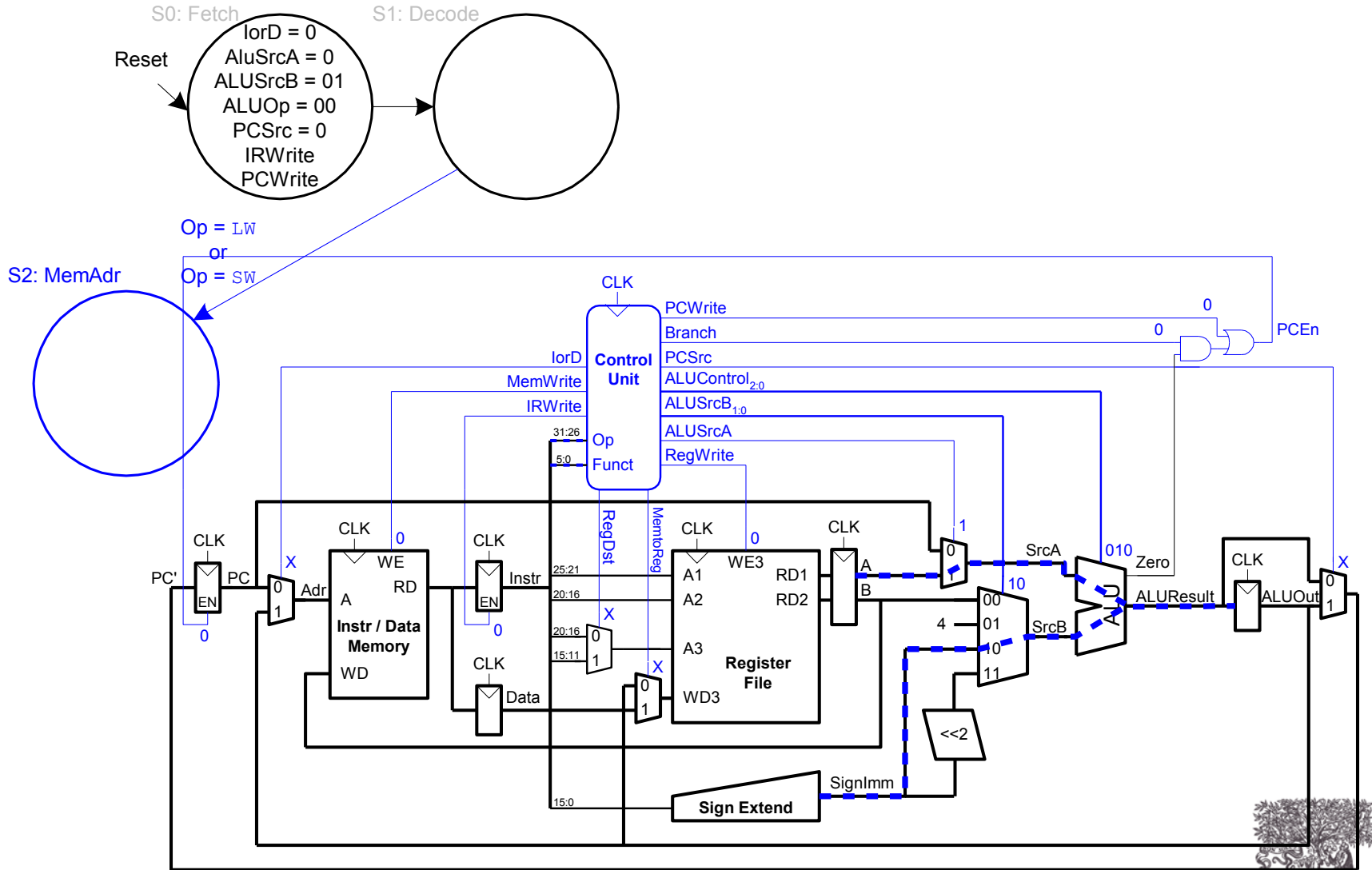


Main Controller FSM: Address

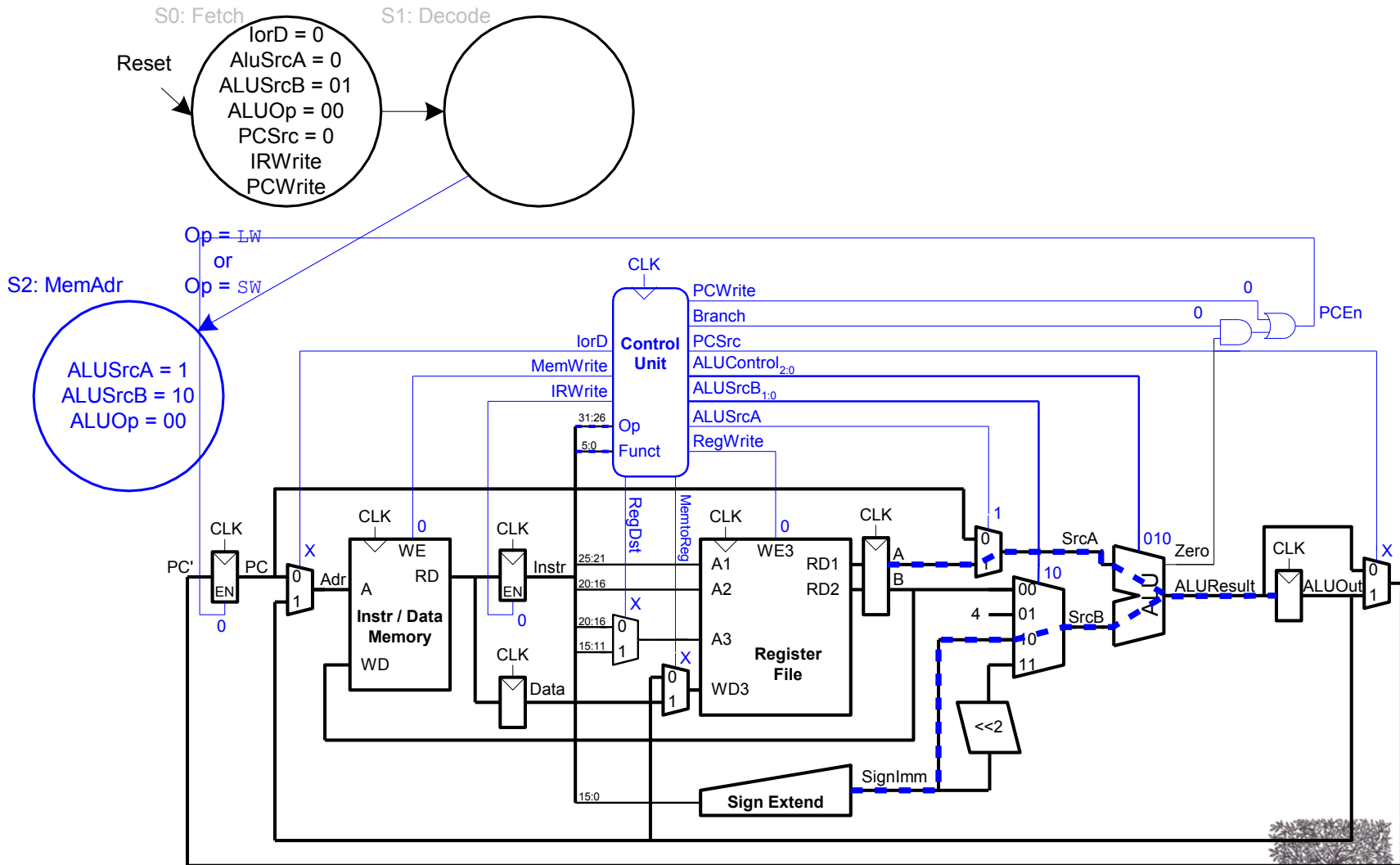


Main Controller FSM: $\perp W$

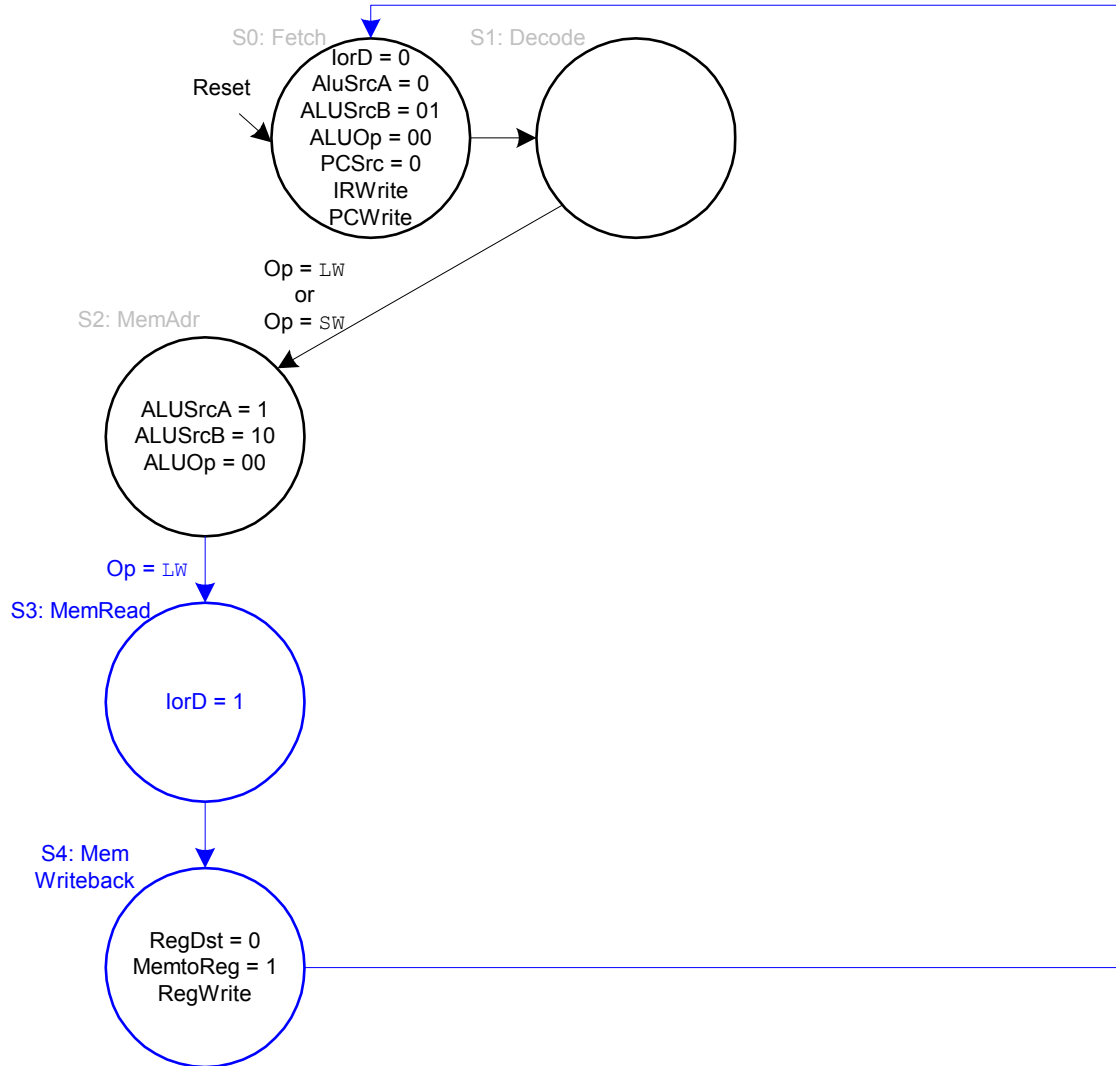


Main Controller FSM: SW

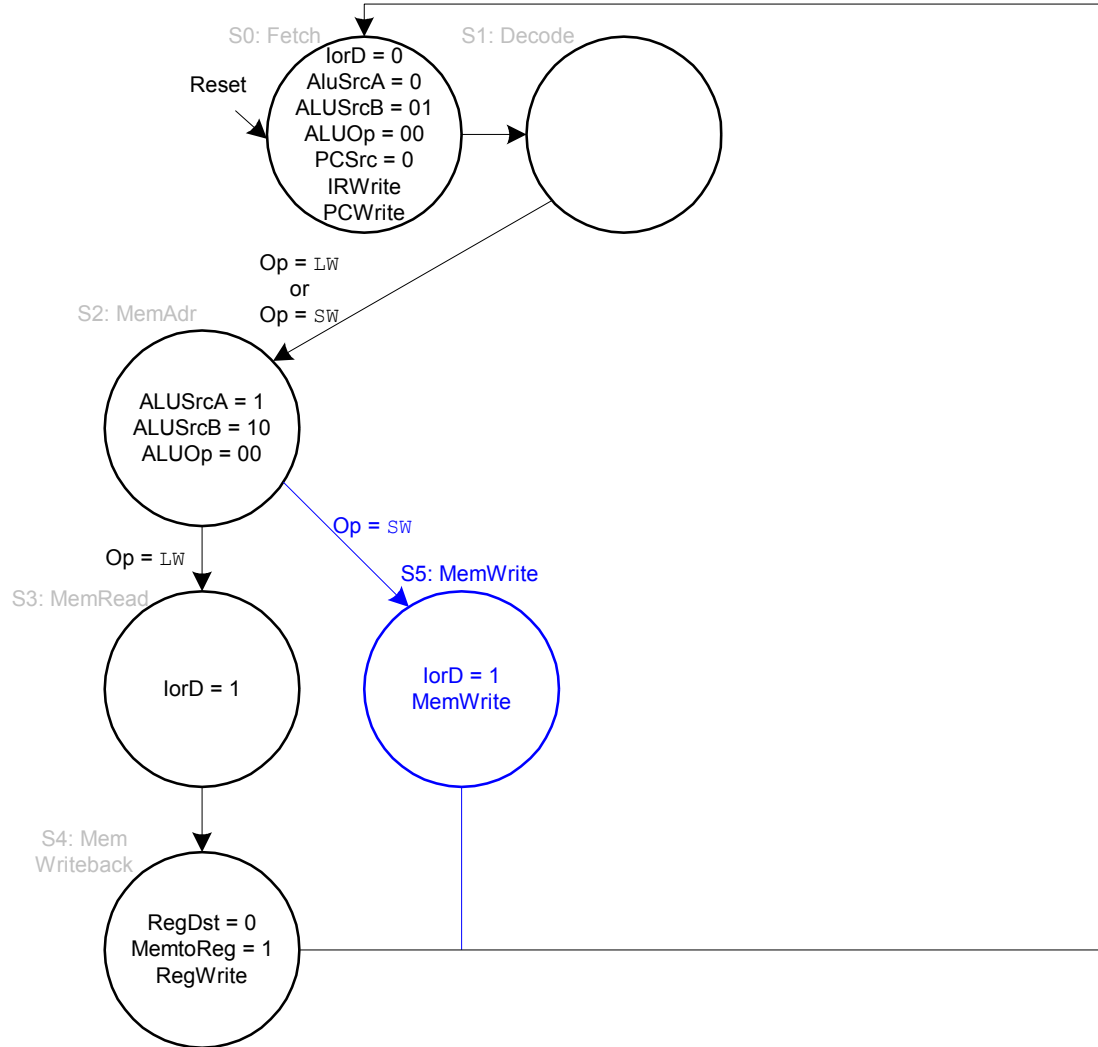


Main Controller FSM: R-Type

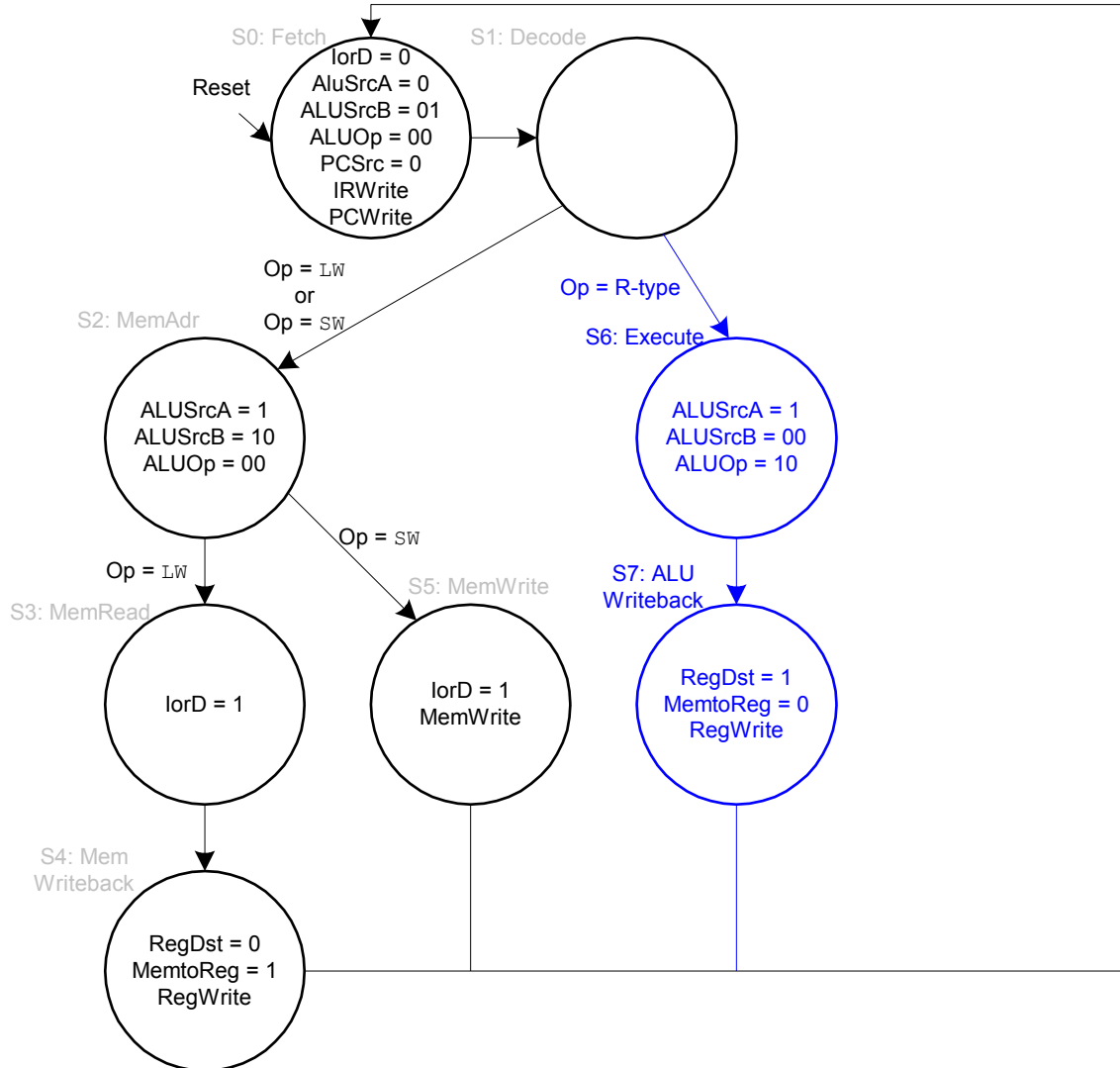


Main Controller FSM: beq

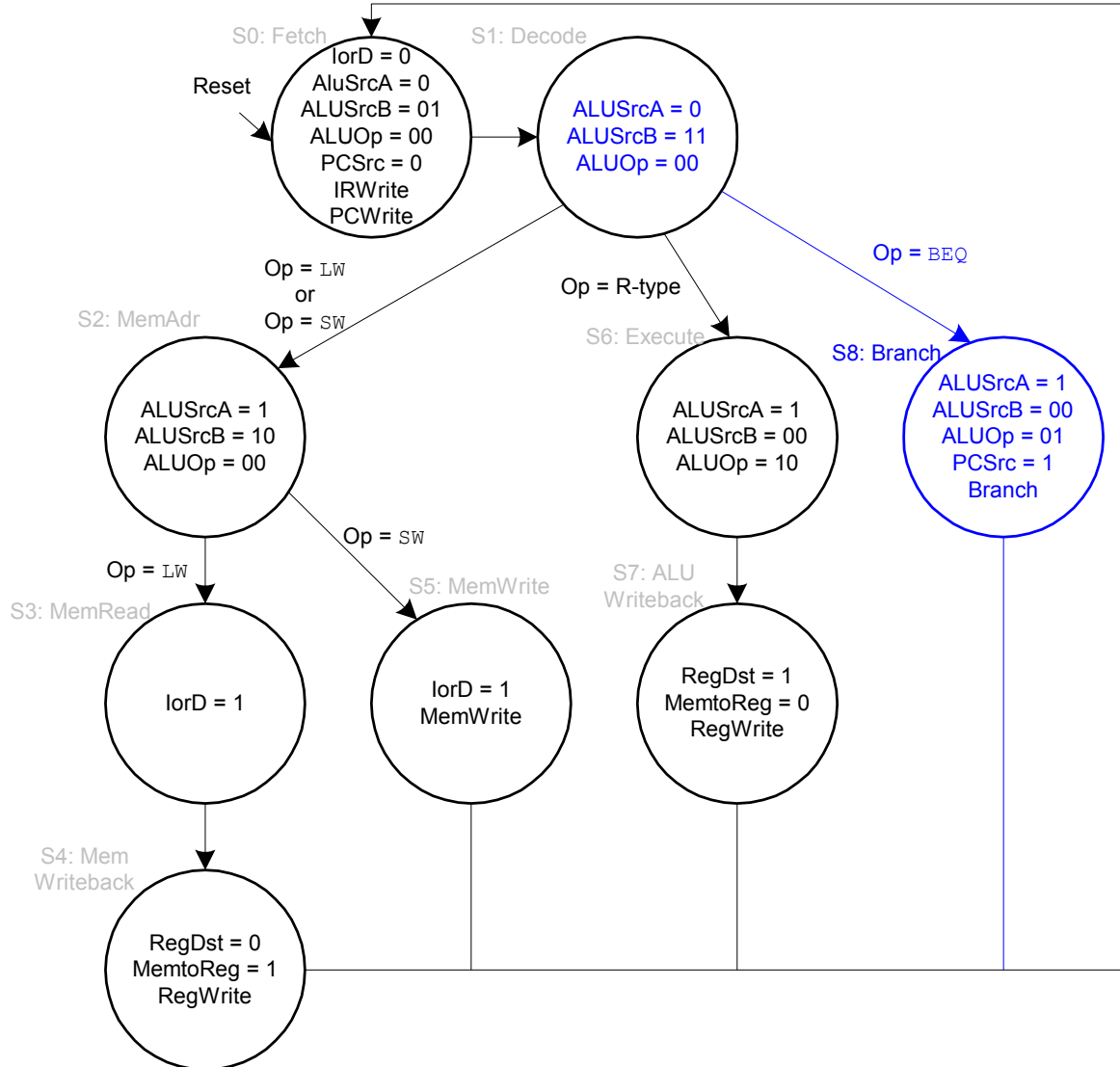


Multicycle Controller FSM

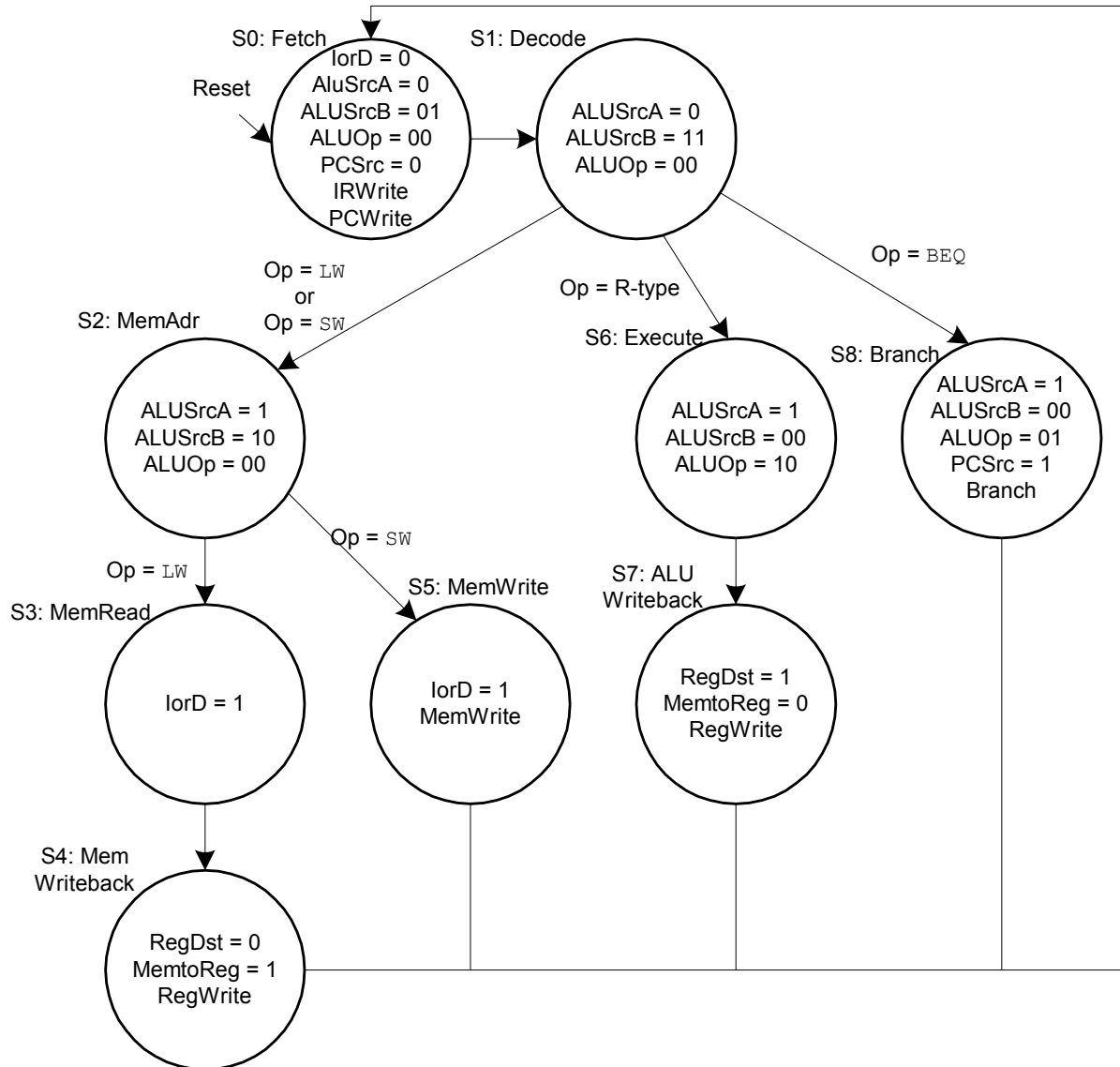


Extended Functionality: addi

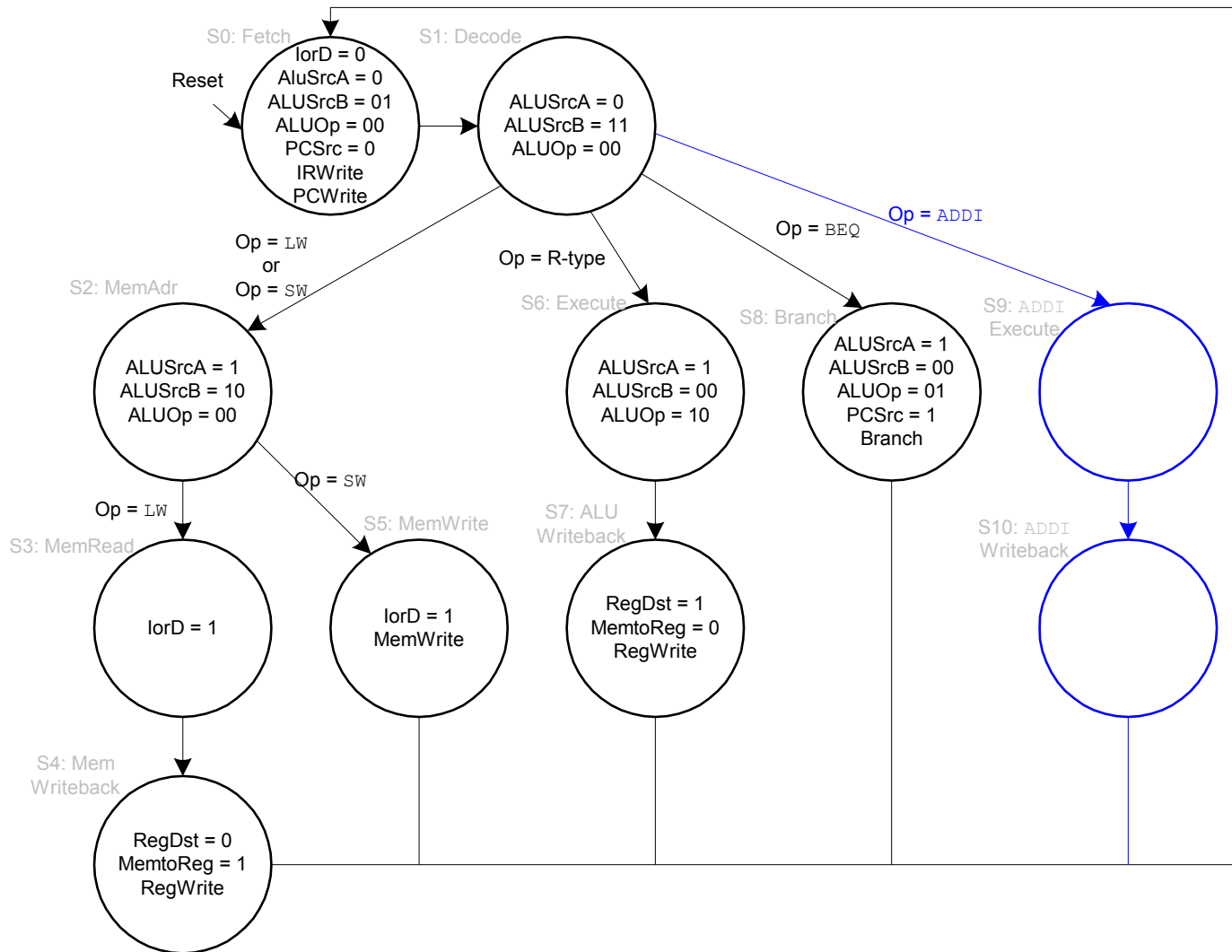


Main Controller FSM: addi

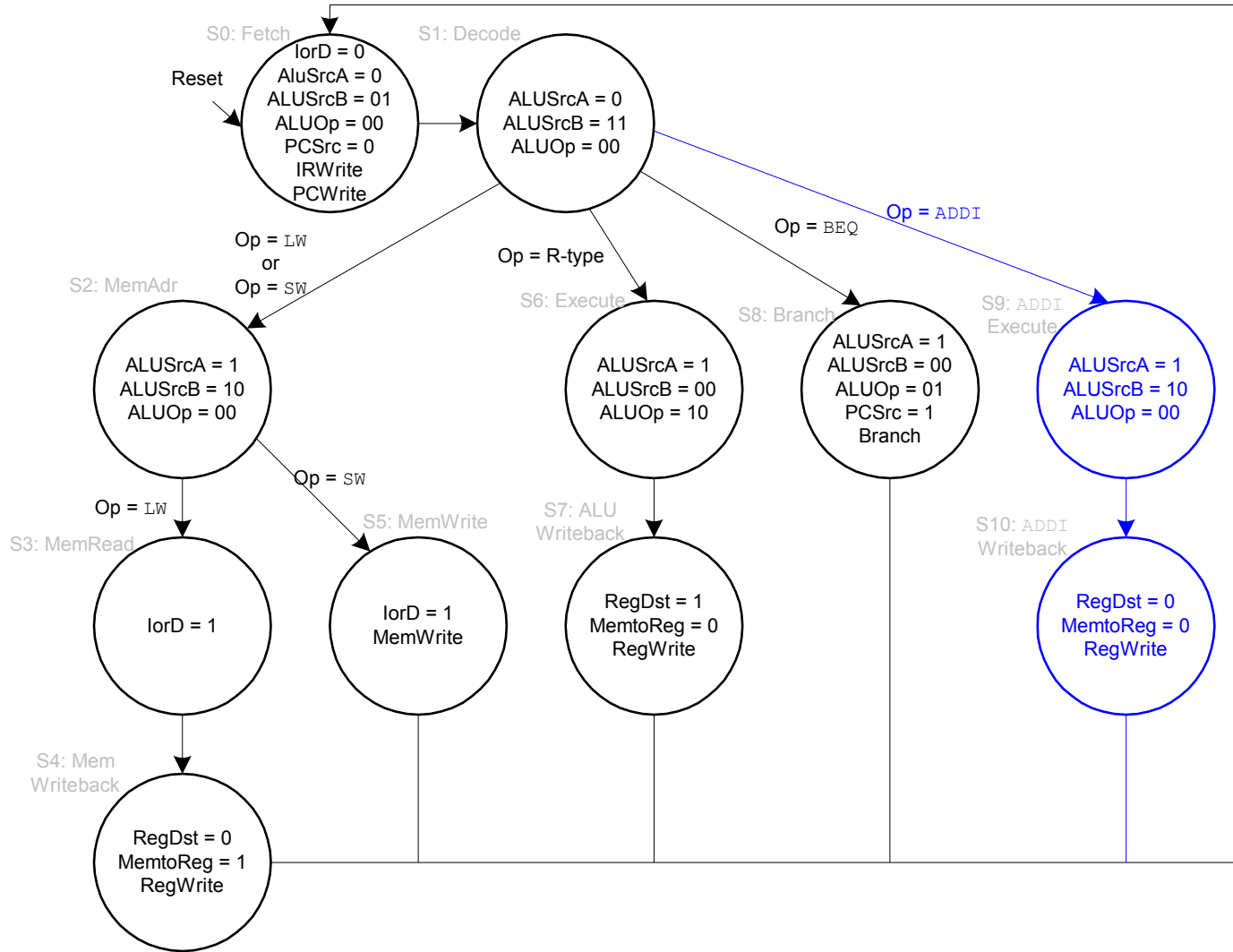


Extended Functionality: j

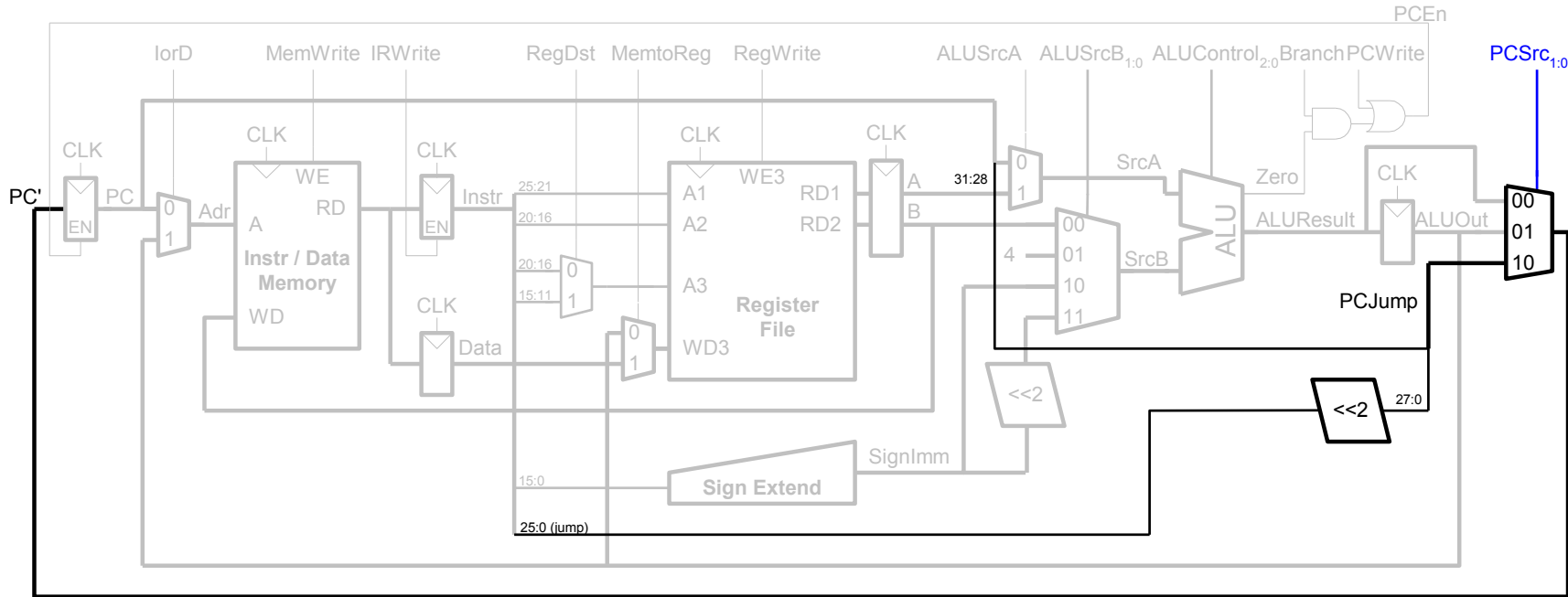

Main Controller FSM: j

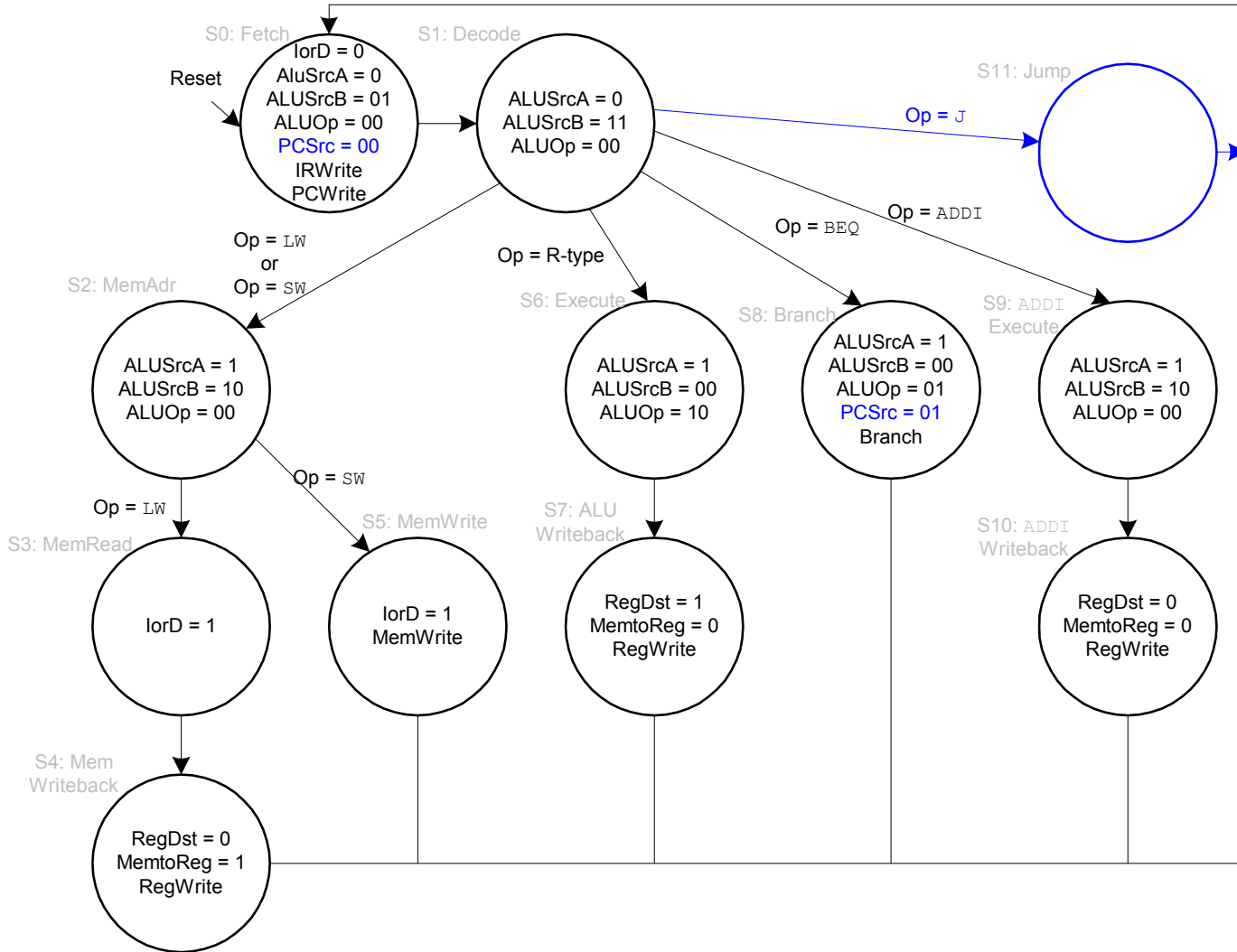

Main Controller FSM: j

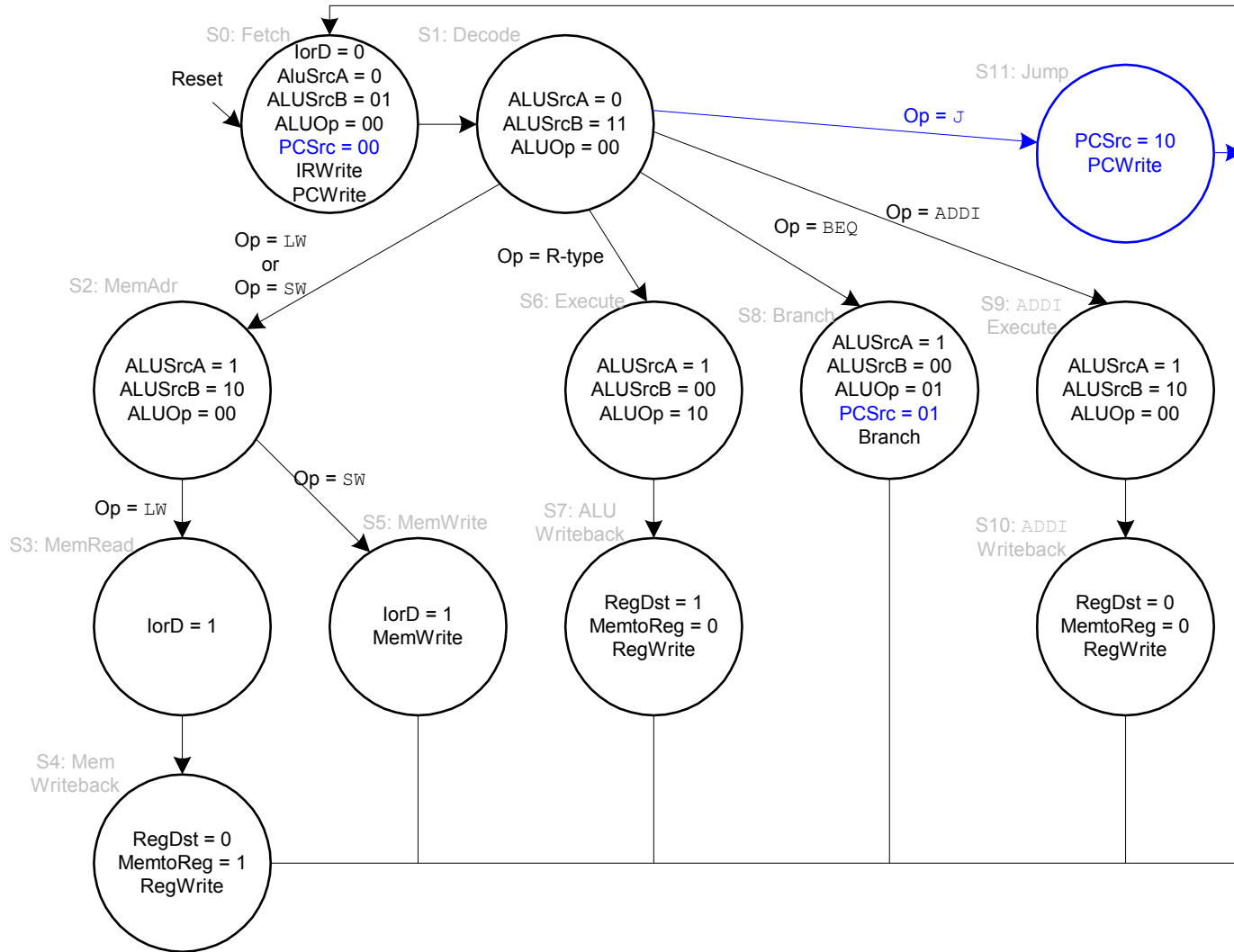

Multicycle Processor


- Instructions take different number of cycles:
 - 3 cycles: beq, j
 - 4 cycles: R-Type, sw, addi
 - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type

Average CPI = $(0.11 + 0.02)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$

Multicycle Processor

Multicycle critical path:
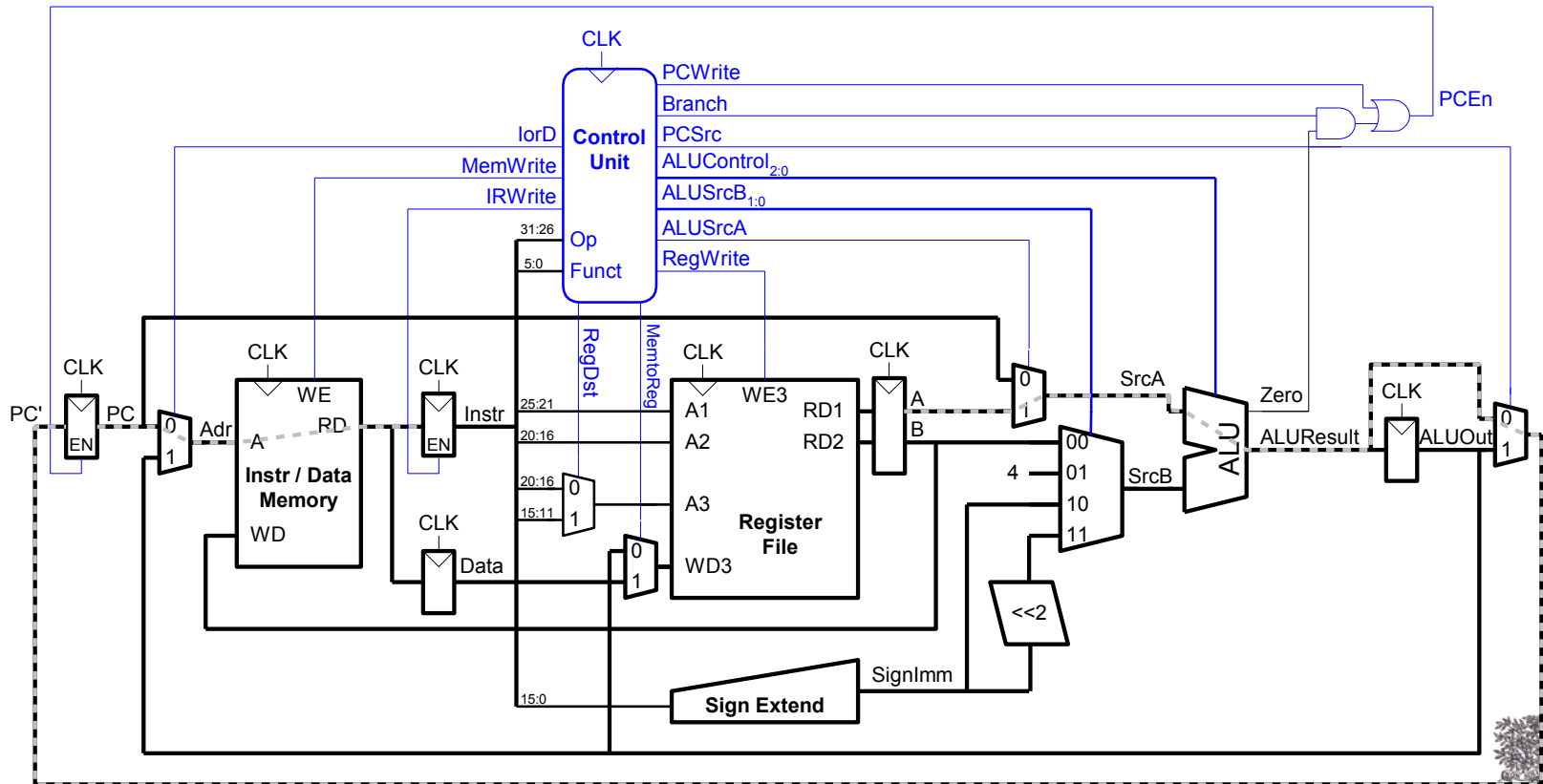
$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c = ?$$

Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}
 T_c &= t_{pcq_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\
 &= t_{pcq_PC} + t_{mux} + t_{mem} + t_{setup} \\
 &= [30 + 25 + 250 + 20] \text{ ps} \\
 &= \mathbf{325 \text{ ps}}
 \end{aligned}$$

Multicycle Performance Example


Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= \mathbf{133.9 \text{ seconds}}\end{aligned}$$


This is **slower** than the single-cycle processor (92.5 seconds). Why?

- Not all steps same length
- Sequencing overhead for each step ($t_{pcq} + t_{\text{setup}} = 50 \text{ ps}$)

Review: Single-Cycle Processor

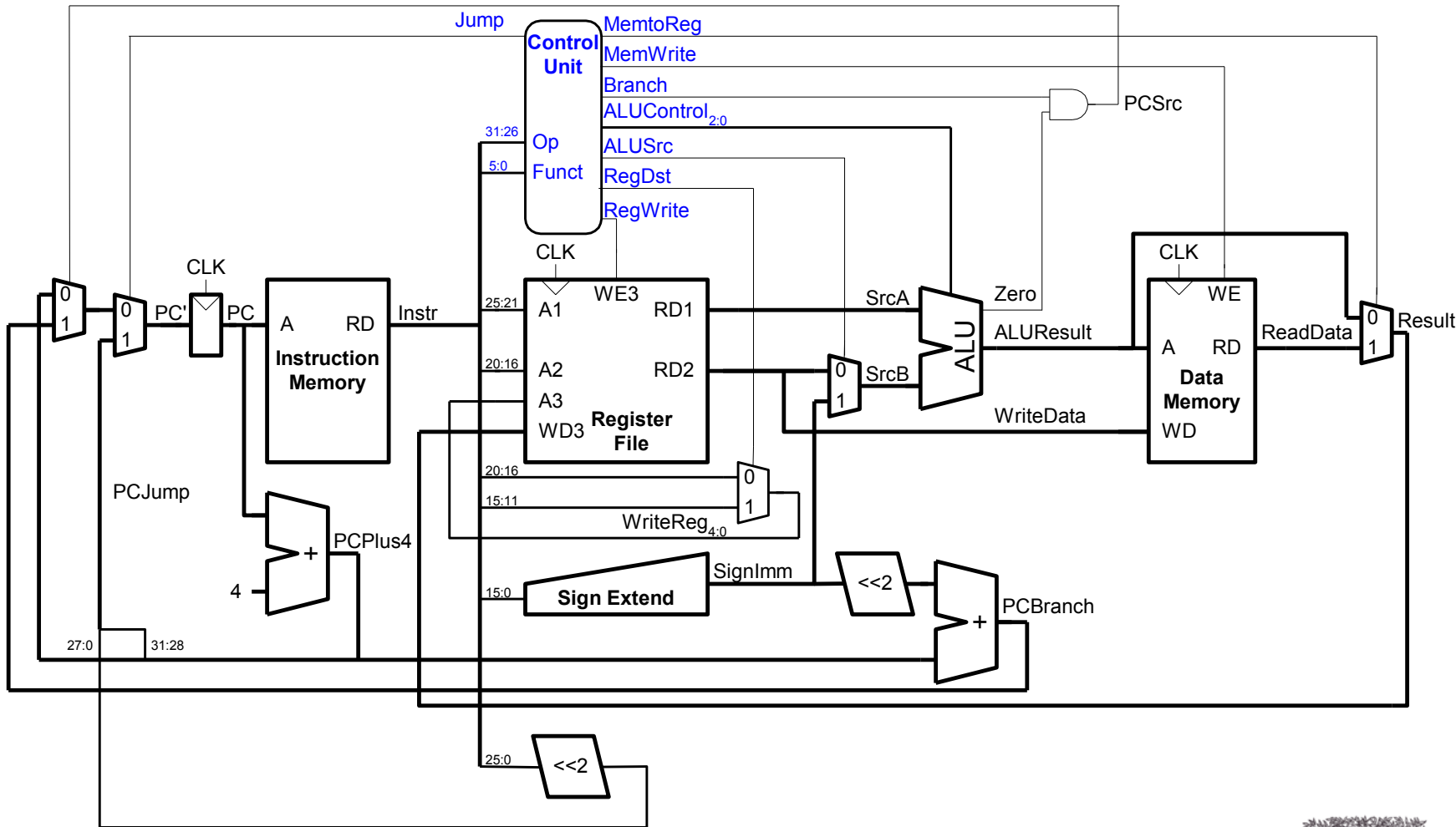

Review: Multicycle Processor

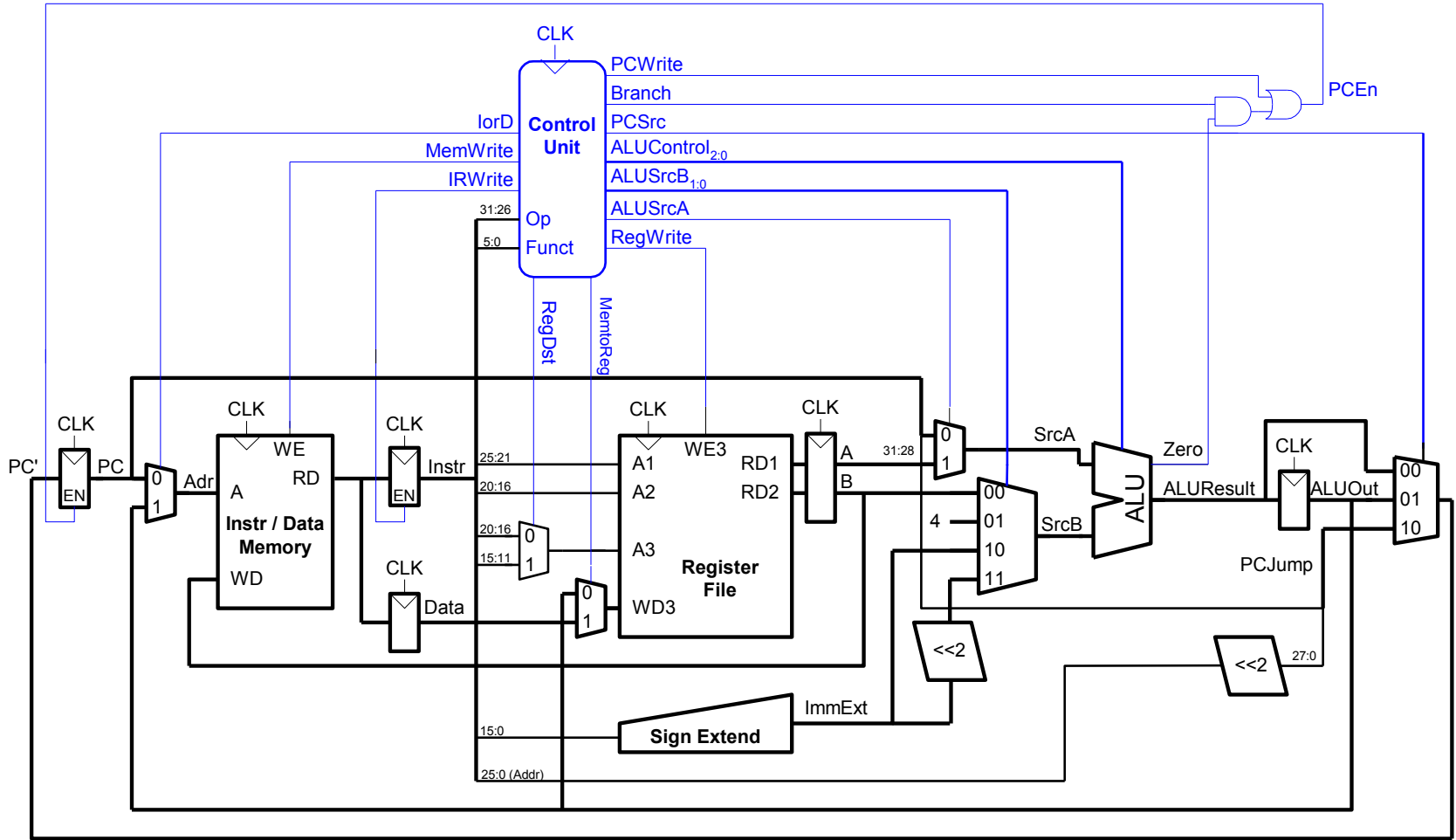


Pipelined MIPS Processor


- Temporal parallelism
- Divide single-cycle processor into 5 stages:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add pipeline registers between stages

Single-Cycle vs. Pipelined


Single-Cycle

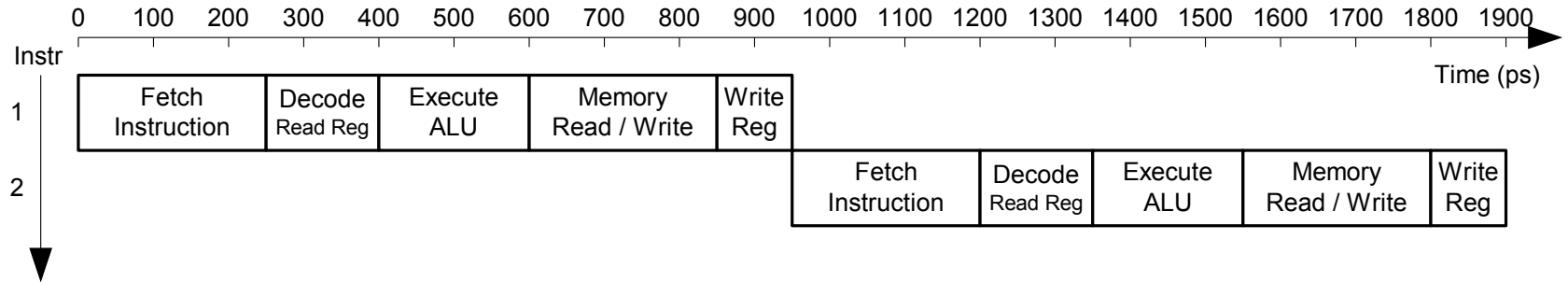



Pipelined

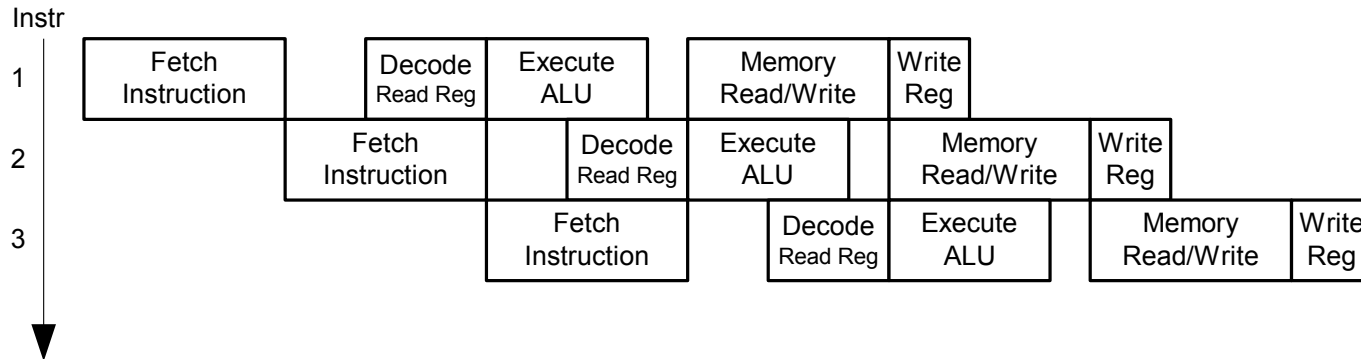


Pipelined Processor Abstraction

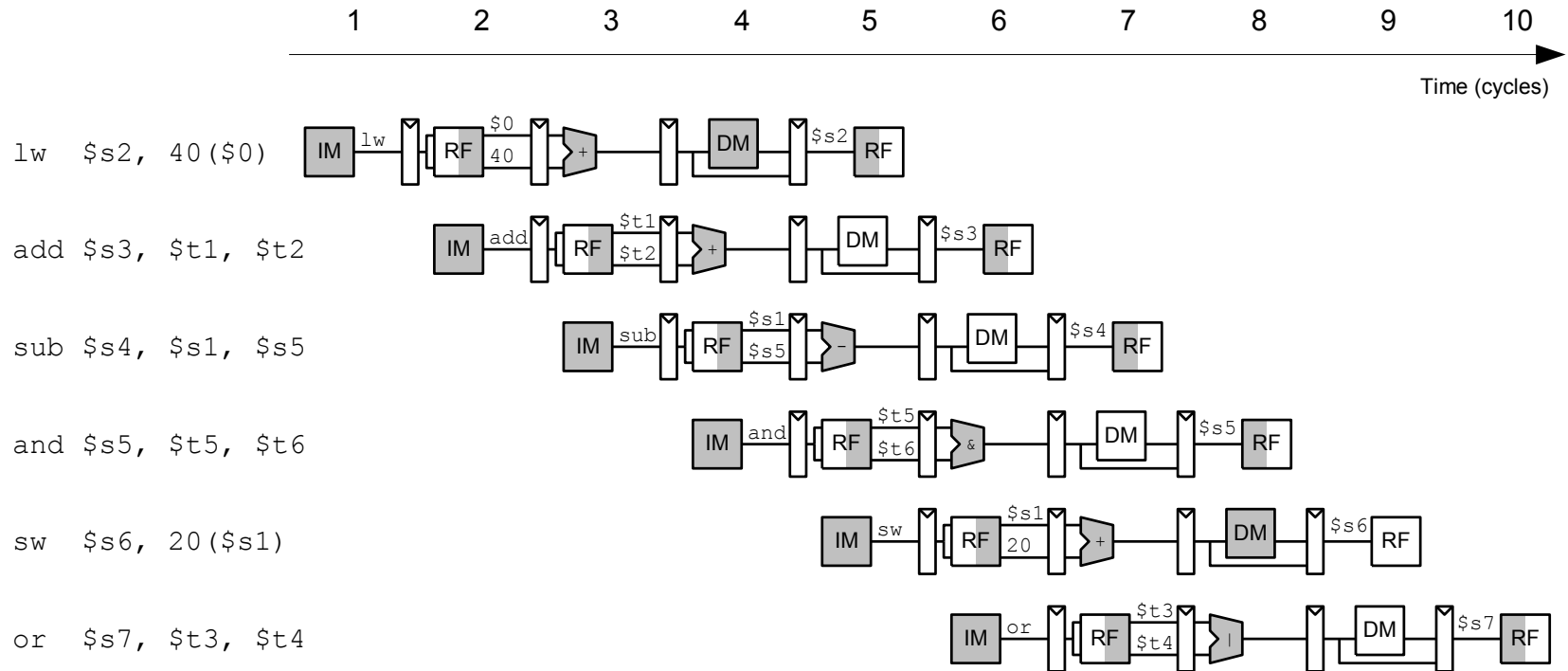

Single-Cycle & Pipelined Datapath

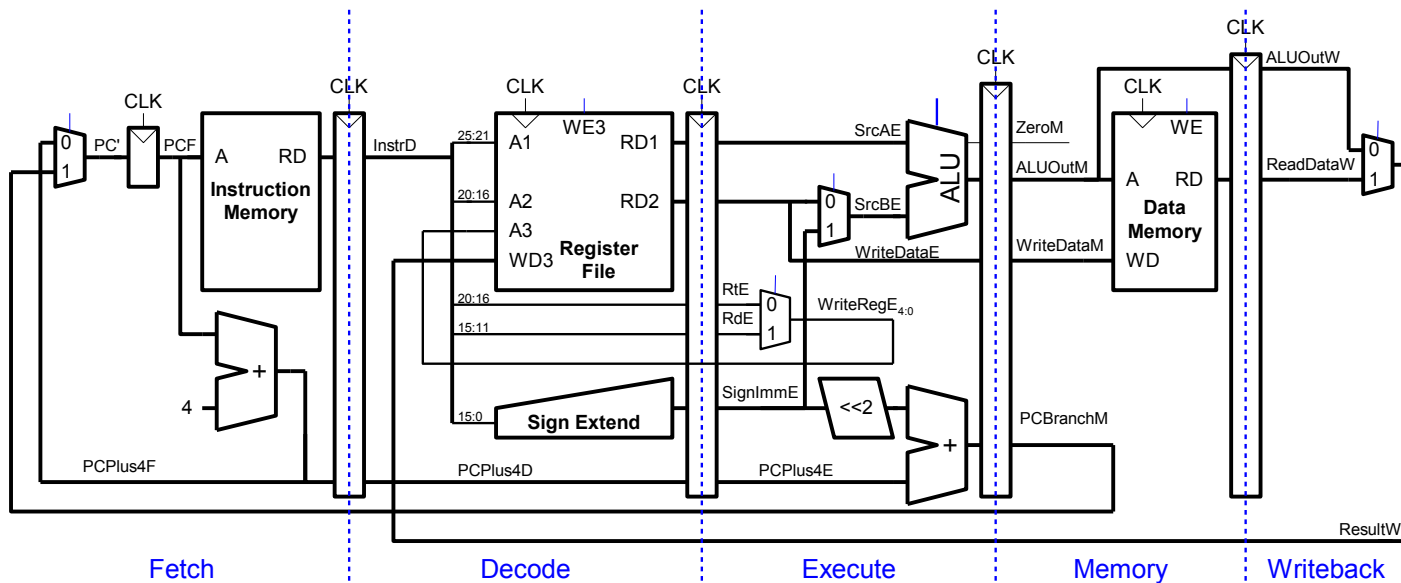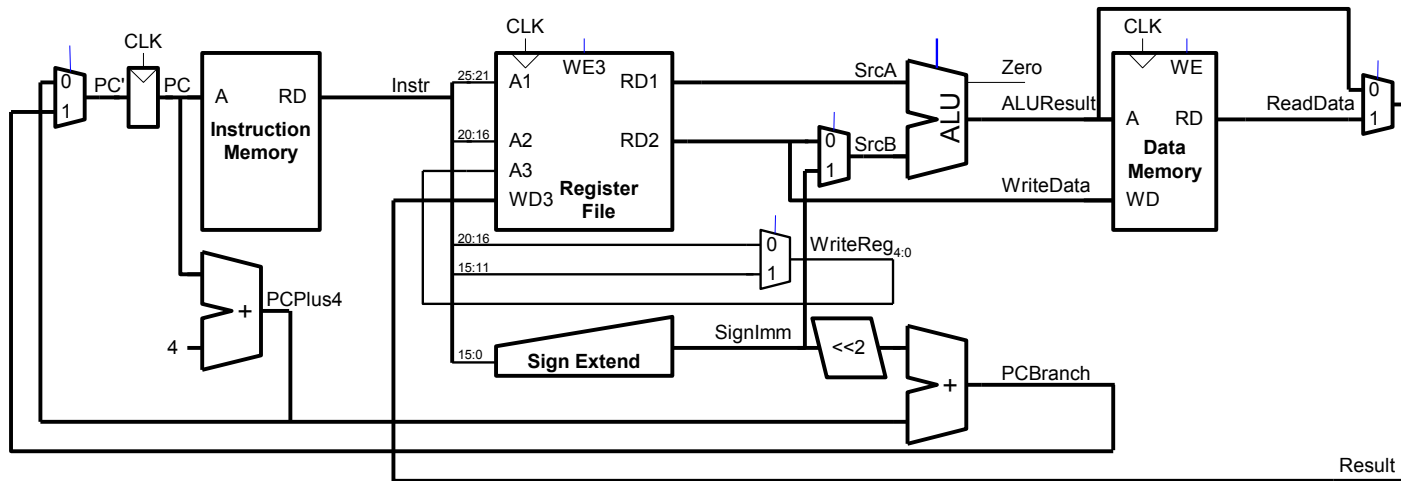


Corrected Pipelined Datapath

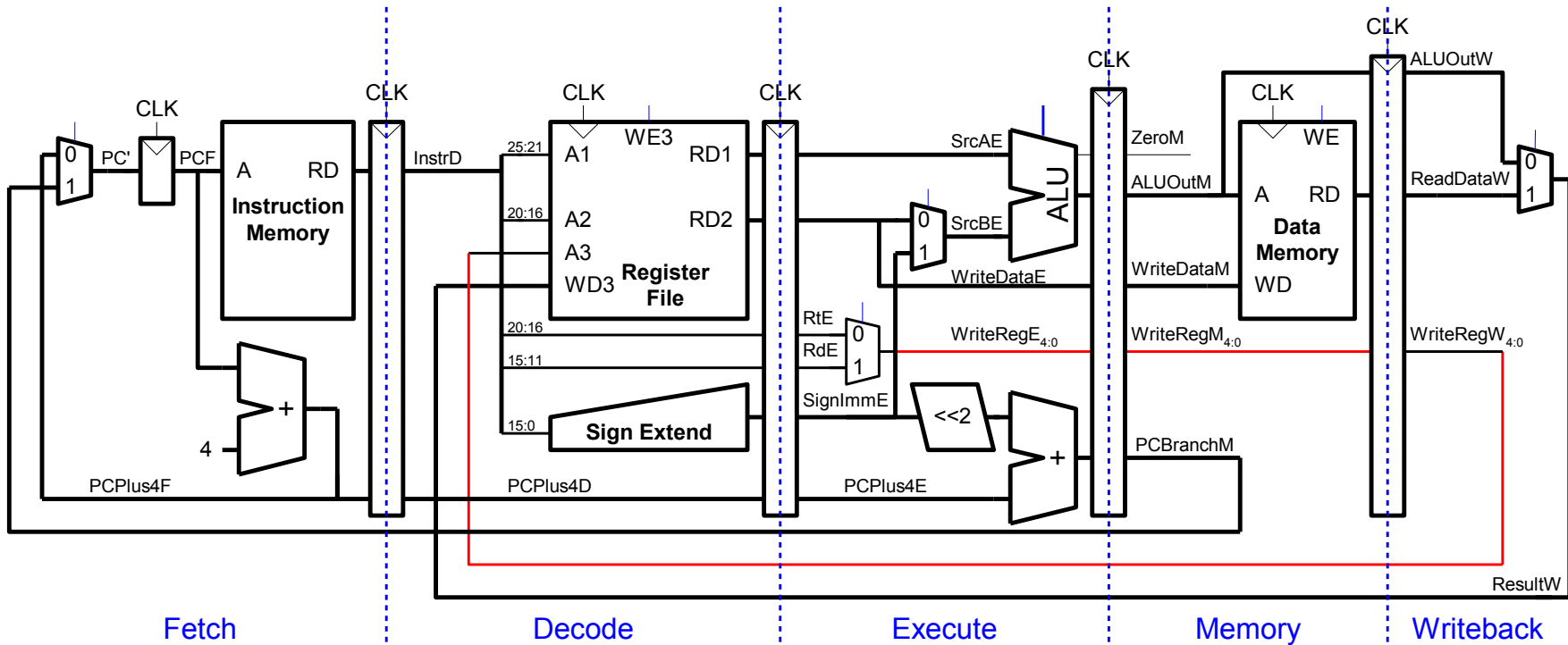

WriteReg* must arrive at same time as *Result



Pipelined Processor Control

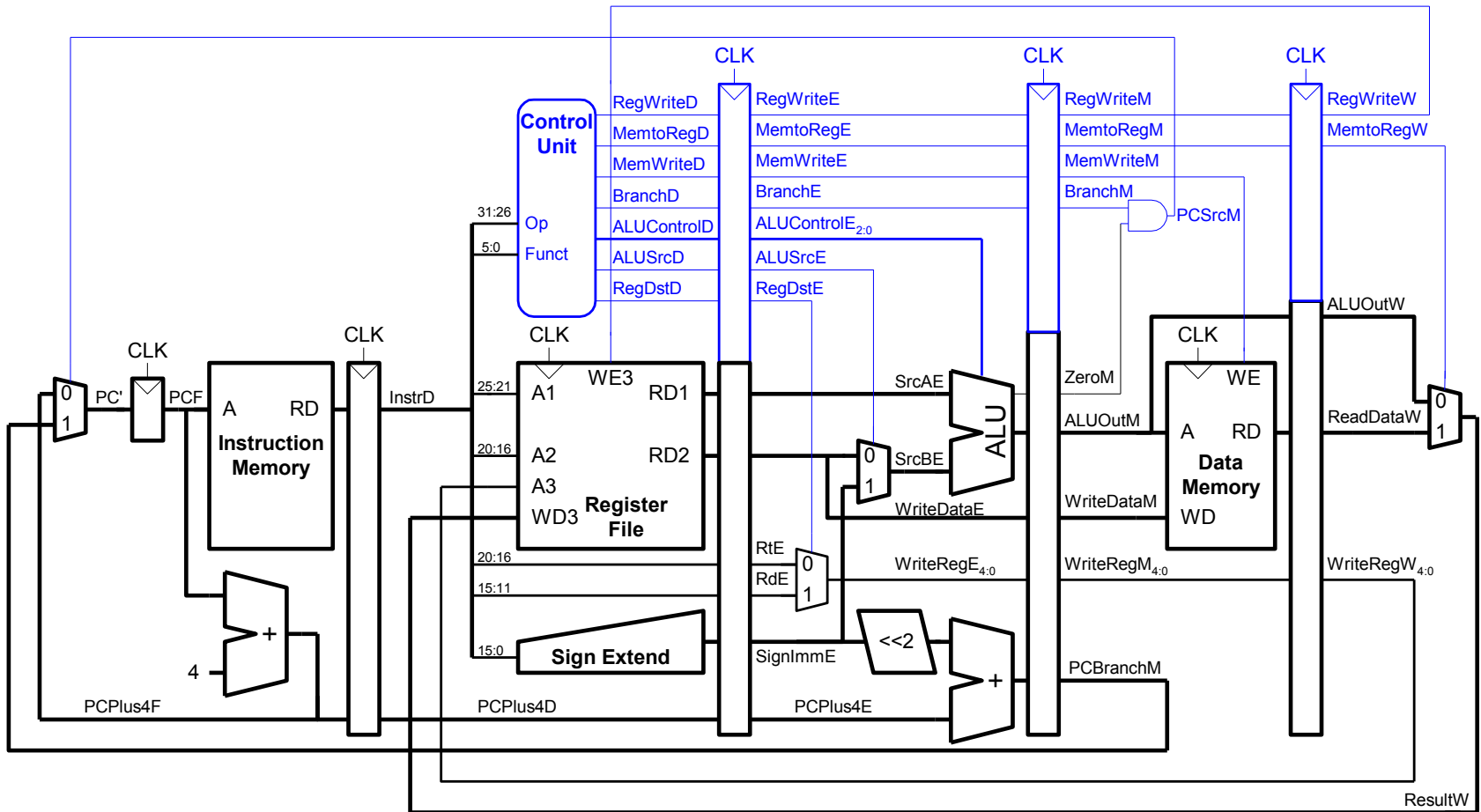


- Same control unit as single-cycle processor
- Control delayed to proper pipeline stage



Pipeline Hazards

- When an instruction depends on result from instruction that hasn't completed
- Types:
 - **Data hazard:** register value not yet written back to register file
 - **Control hazard:** next instruction not decided yet (caused by branches)

Data Hazard

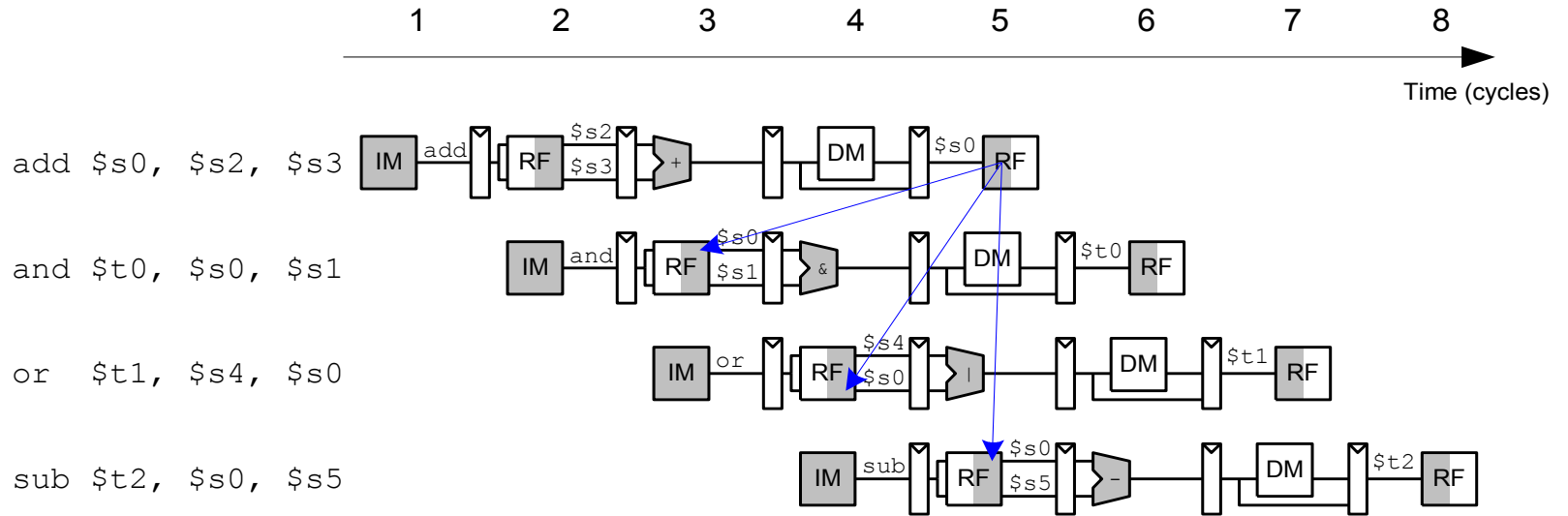


Handling Data Hazards


- Insert `nops` in code at compile time
- Rearrange code at compile time
- Forward data at run time
- Stall the processor at run time

Compile-Time Hazard Elimination

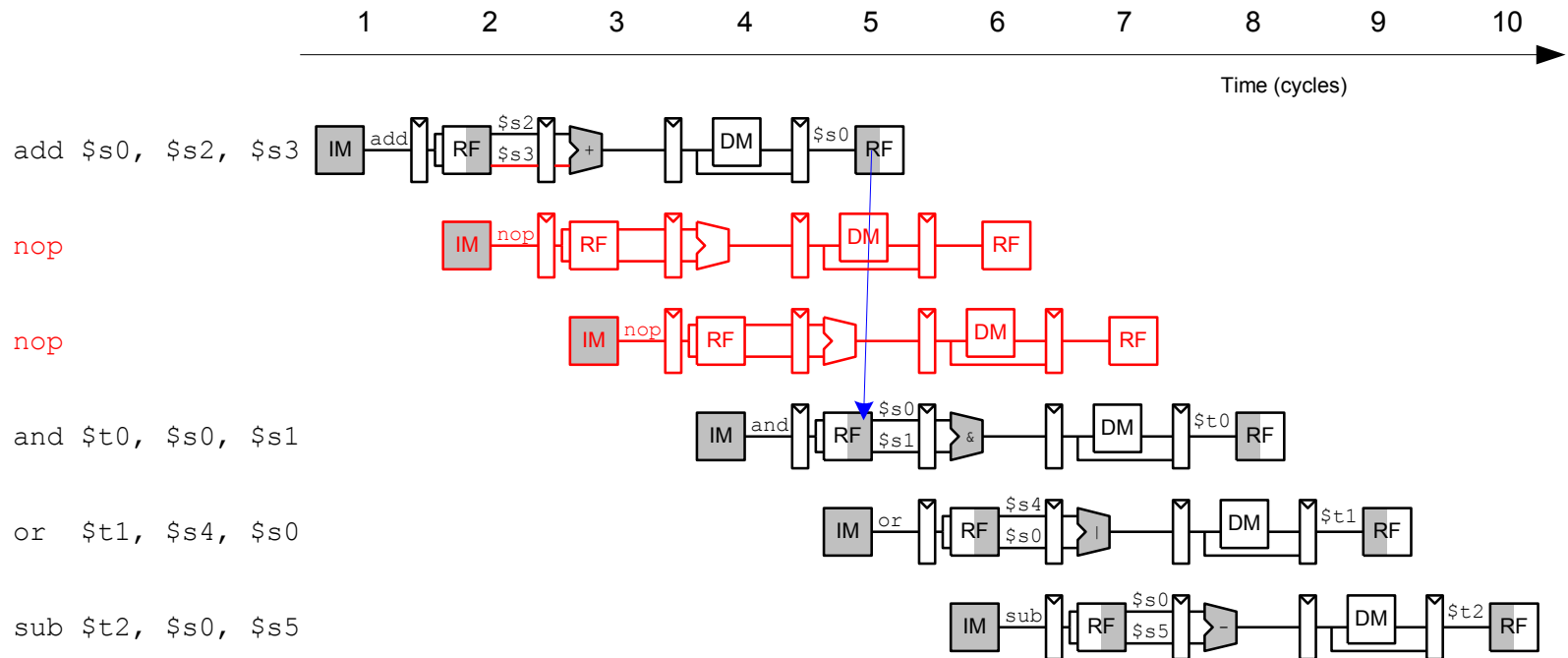
- Insert enough nops for result to be ready
- Or move independent useful instructions forward



Data Forwarding

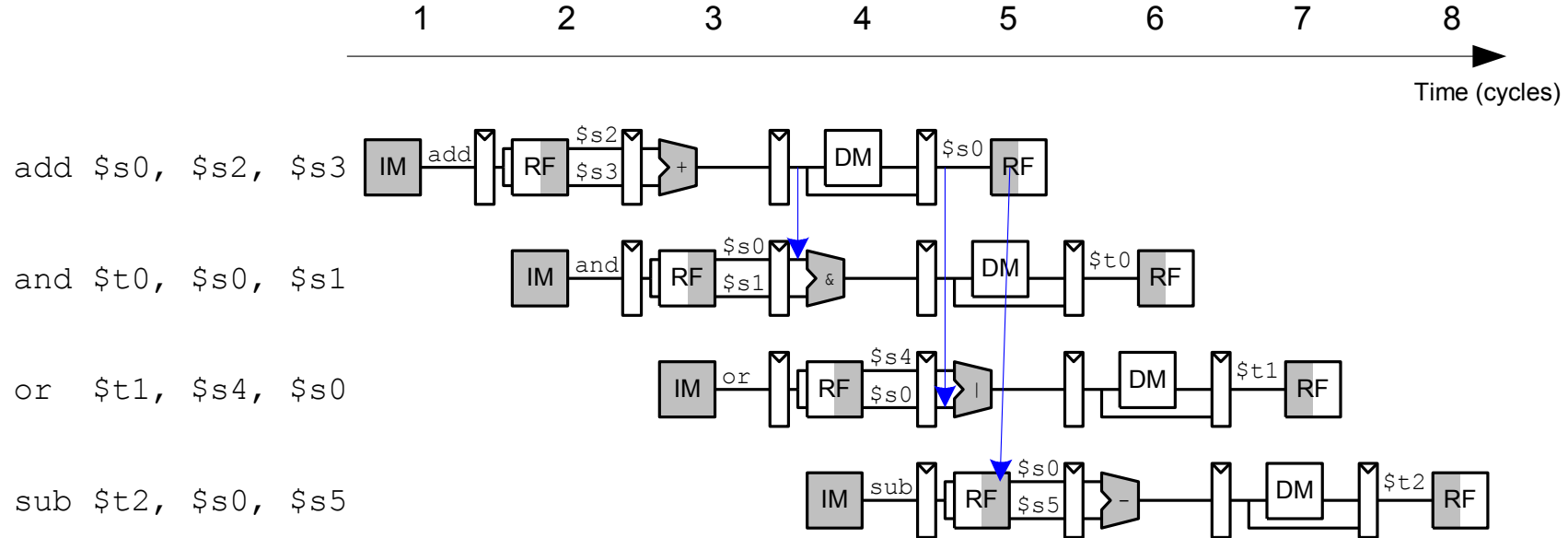

Data Forwarding

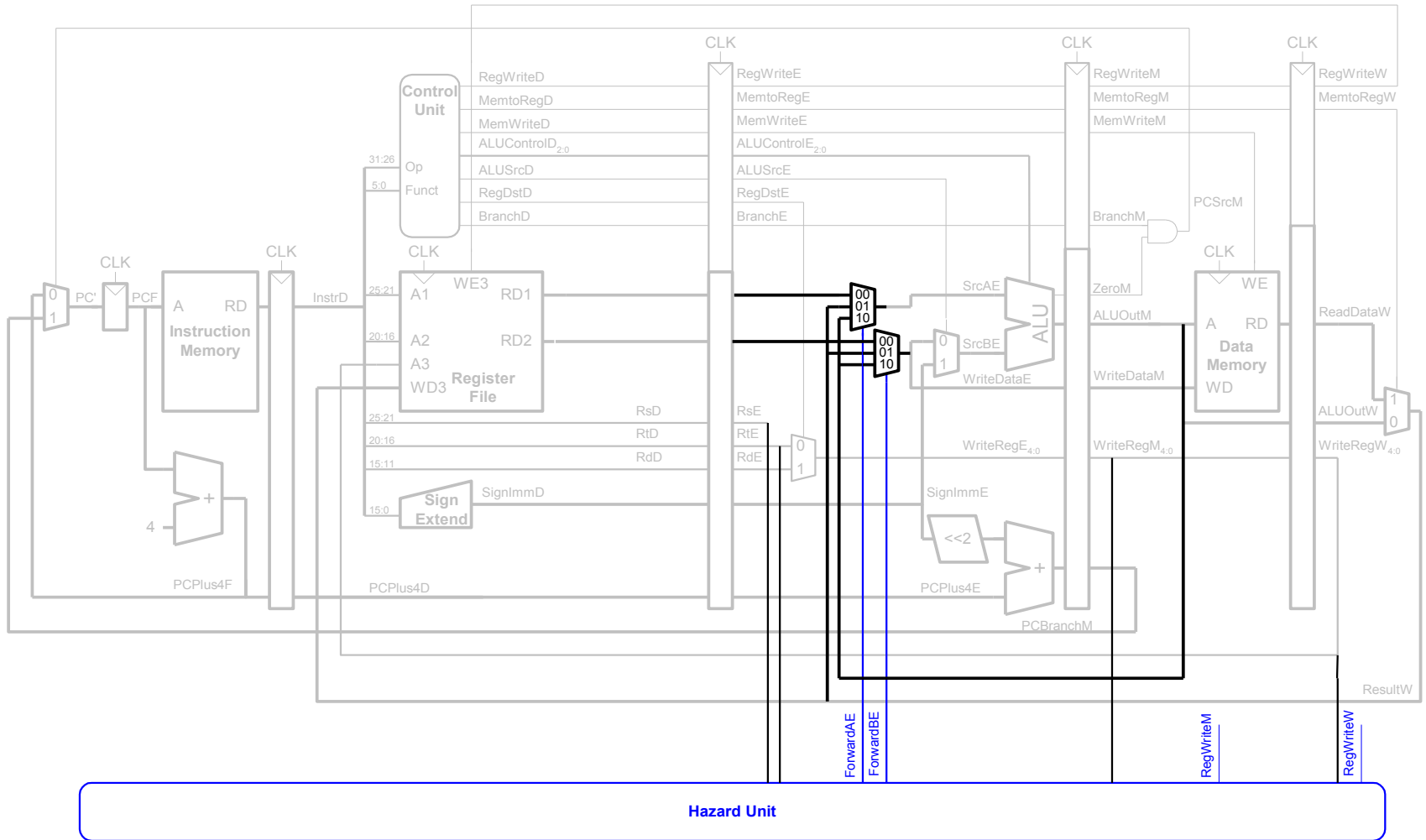

Data Forwarding


- Forward to Execute stage from either:
 - Memory stage or
 - Writeback stage
- Forwarding logic for *ForwardAE*:

```
if      ((rsE != 0) AND (rsE == WriteRegM) AND RegWriteM)
  then  ForwardAE = 10
else if ((rsE != 0) AND (rsE == WriteRegW) AND RegWriteW)
  then  ForwardAE = 01


else    ForwardAE = 00
```

Forwarding logic for *ForwardBE* same, but replace *rsE* with *rtE*


Stalling

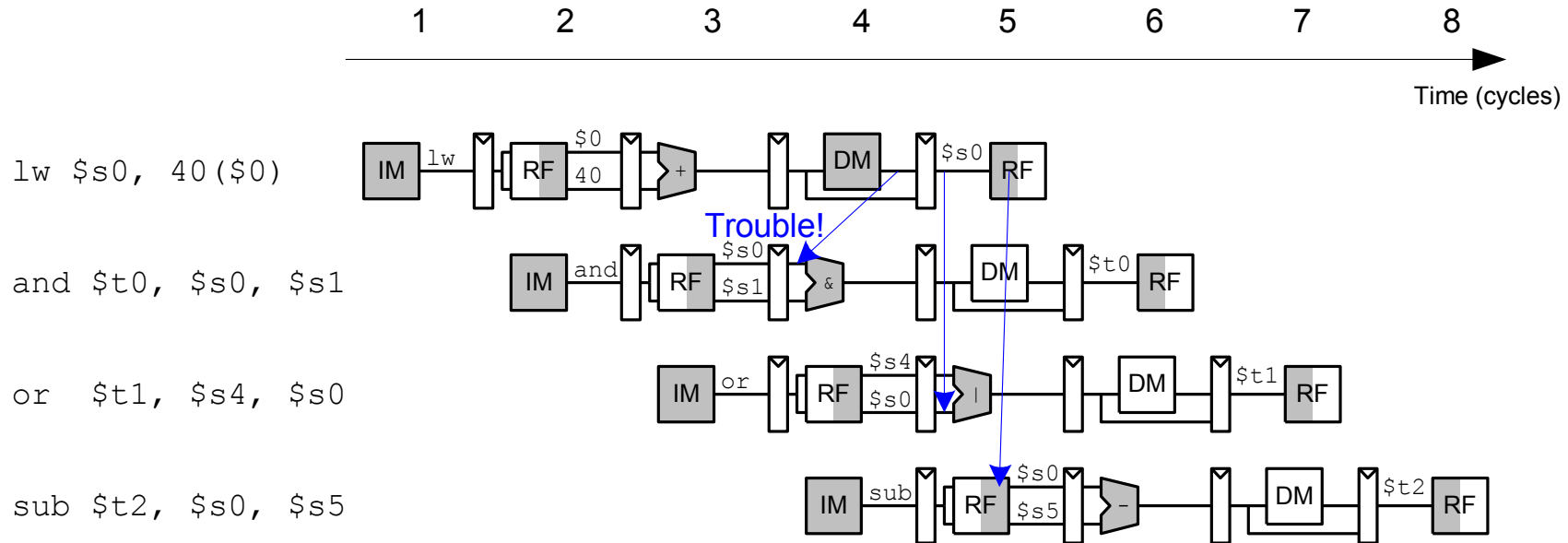

Stalling

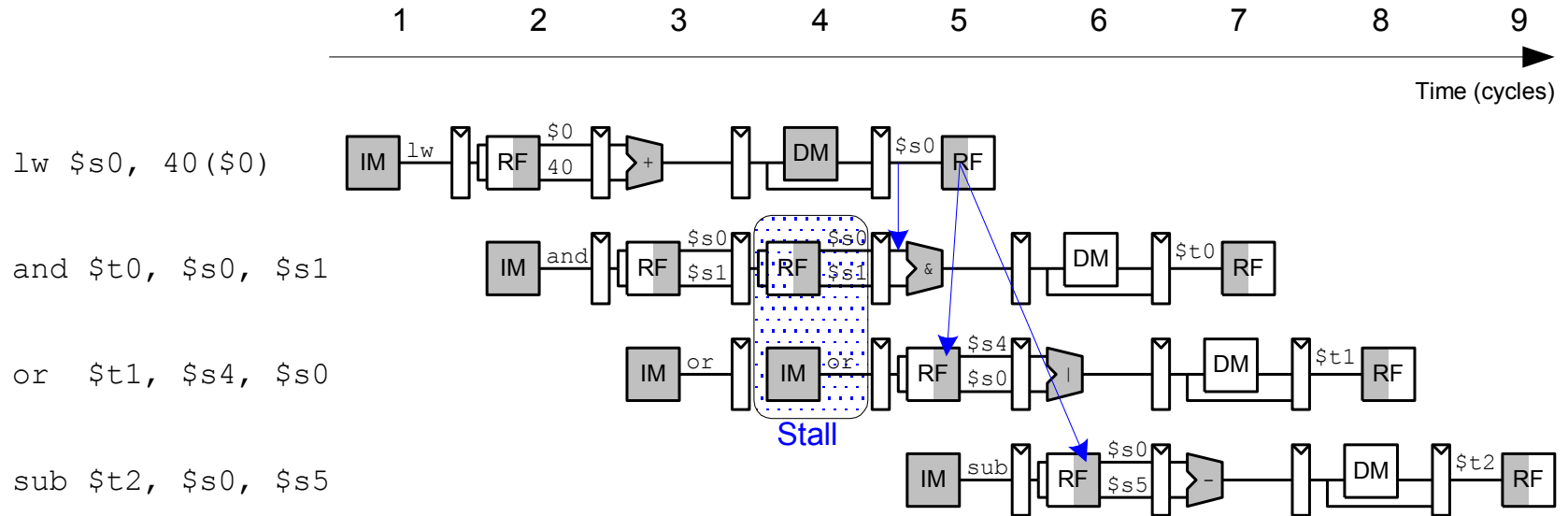

Stalling Hardware

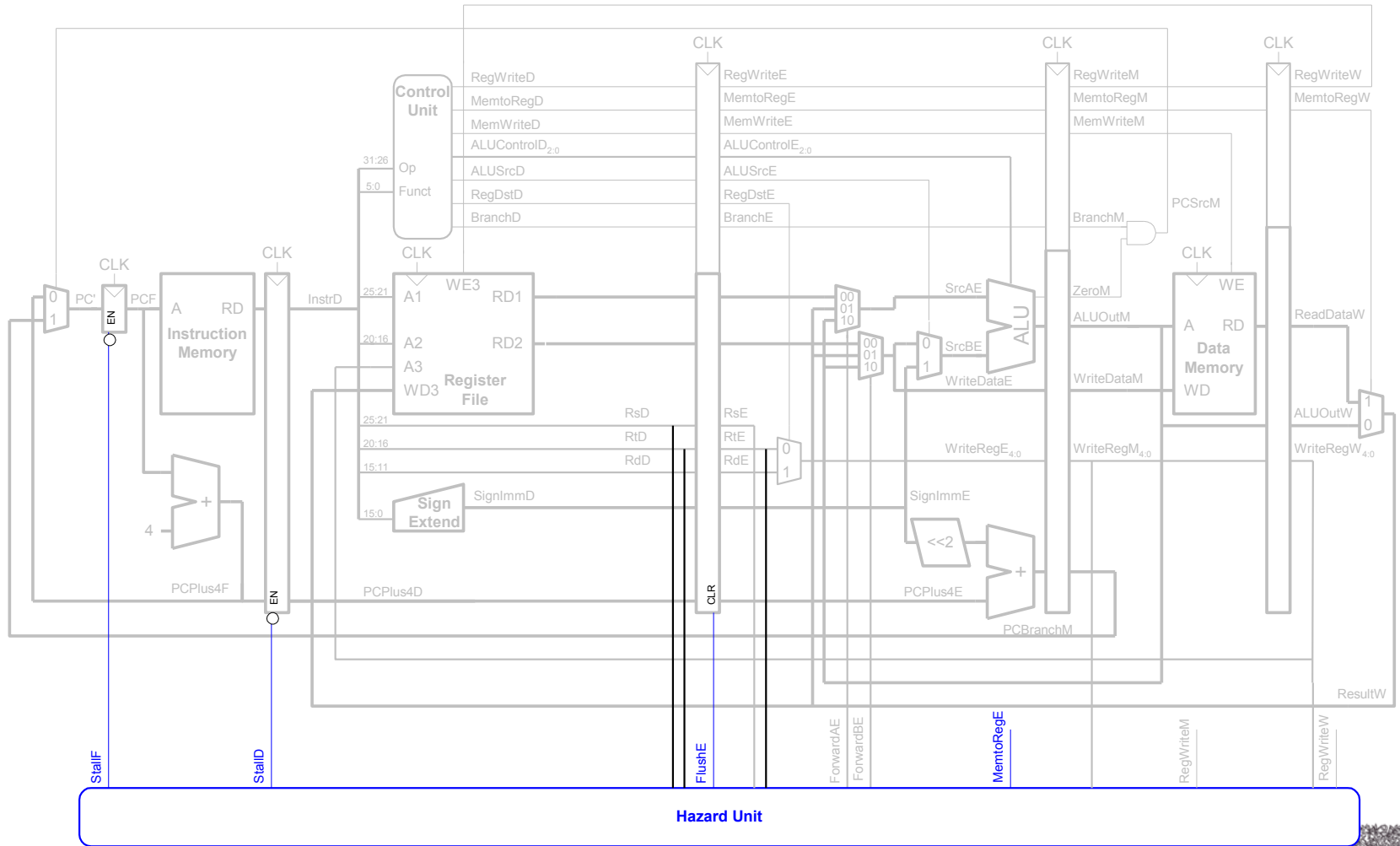

Stalling Logic

lwstall =


$((rsD == rtE) \text{ OR } (rtD == rtE)) \text{ AND MemtoRegE}$

StallF = *StallD* = *FlushE* = *lwstall*


Control Hazards

- **beq:**
 - branch not determined until 4th stage of pipeline
 - Instructions after branch fetched before branch occurs
 - These instructions must be flushed if branch happens
- **Branch misprediction penalty**
 - number of instruction flushed when branch is taken
 - May be reduced by determining branch earlier


Control Hazards: Original Pipeline

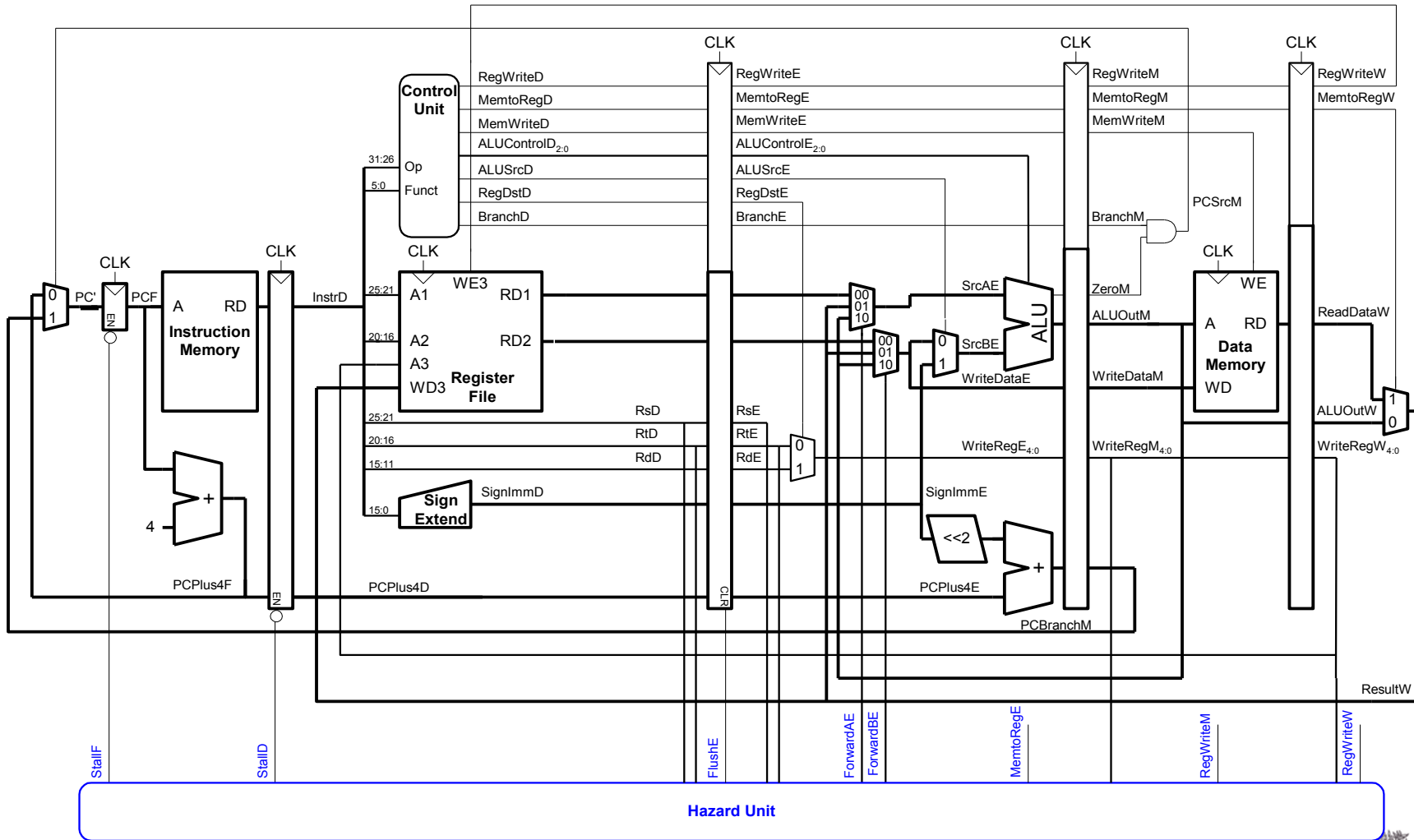

Control Hazards

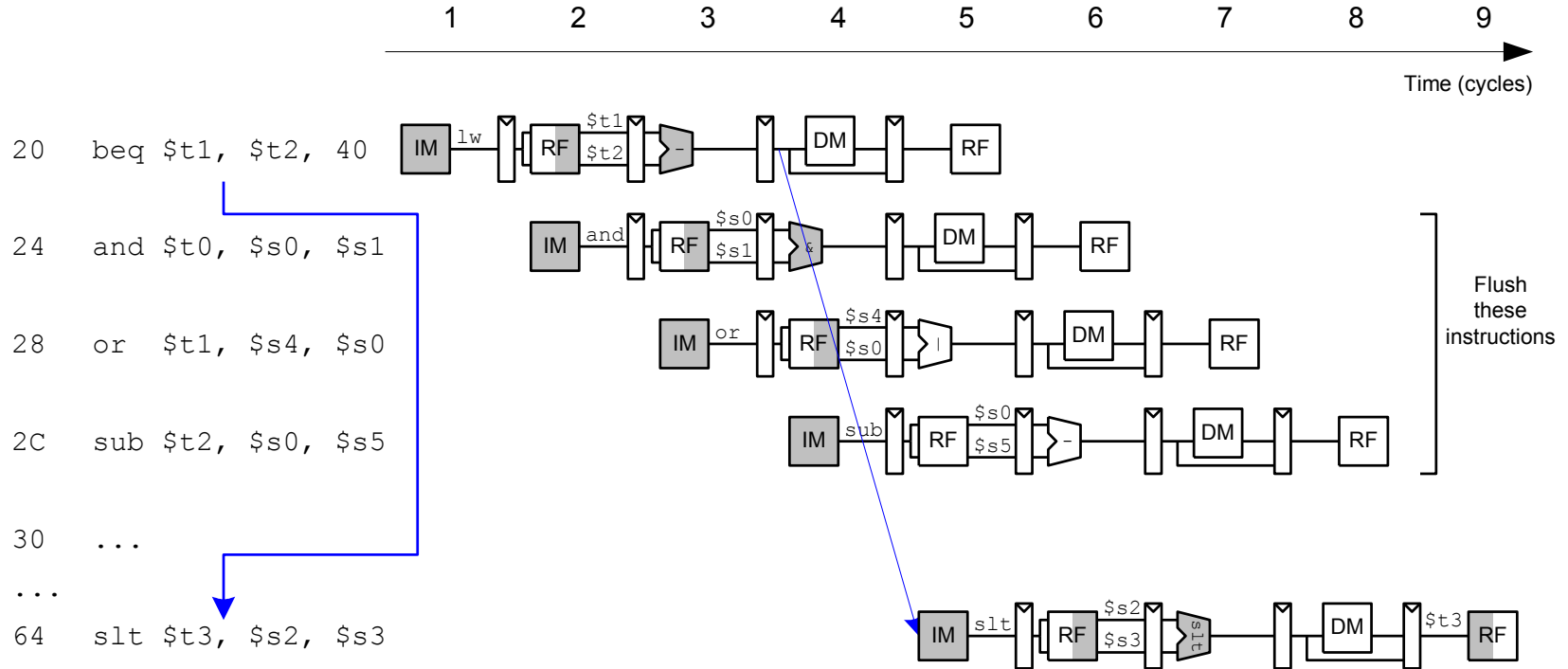


Early Branch Resolution

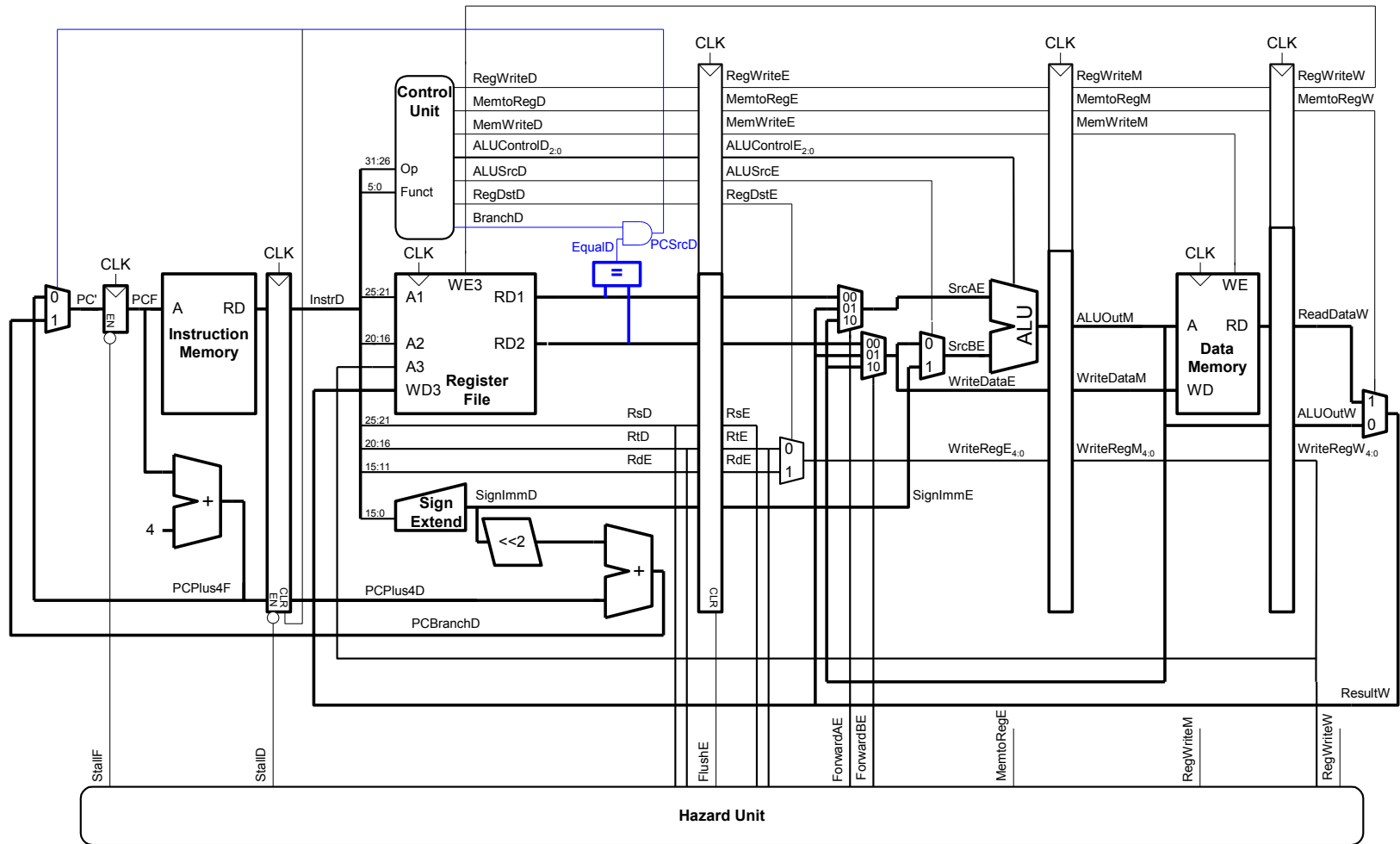


Introduced another data hazard in Decode stage



Early Branch Resolution

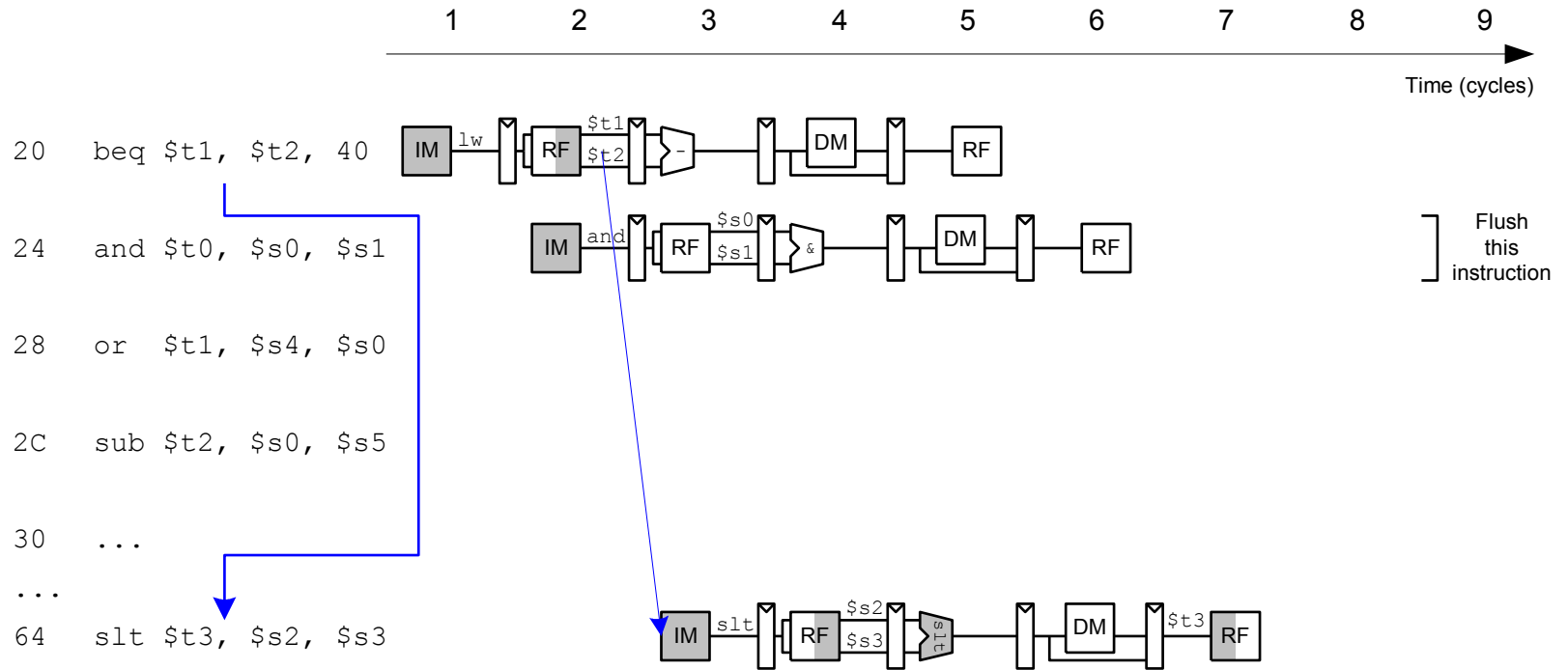

Handling Data & Control Hazards

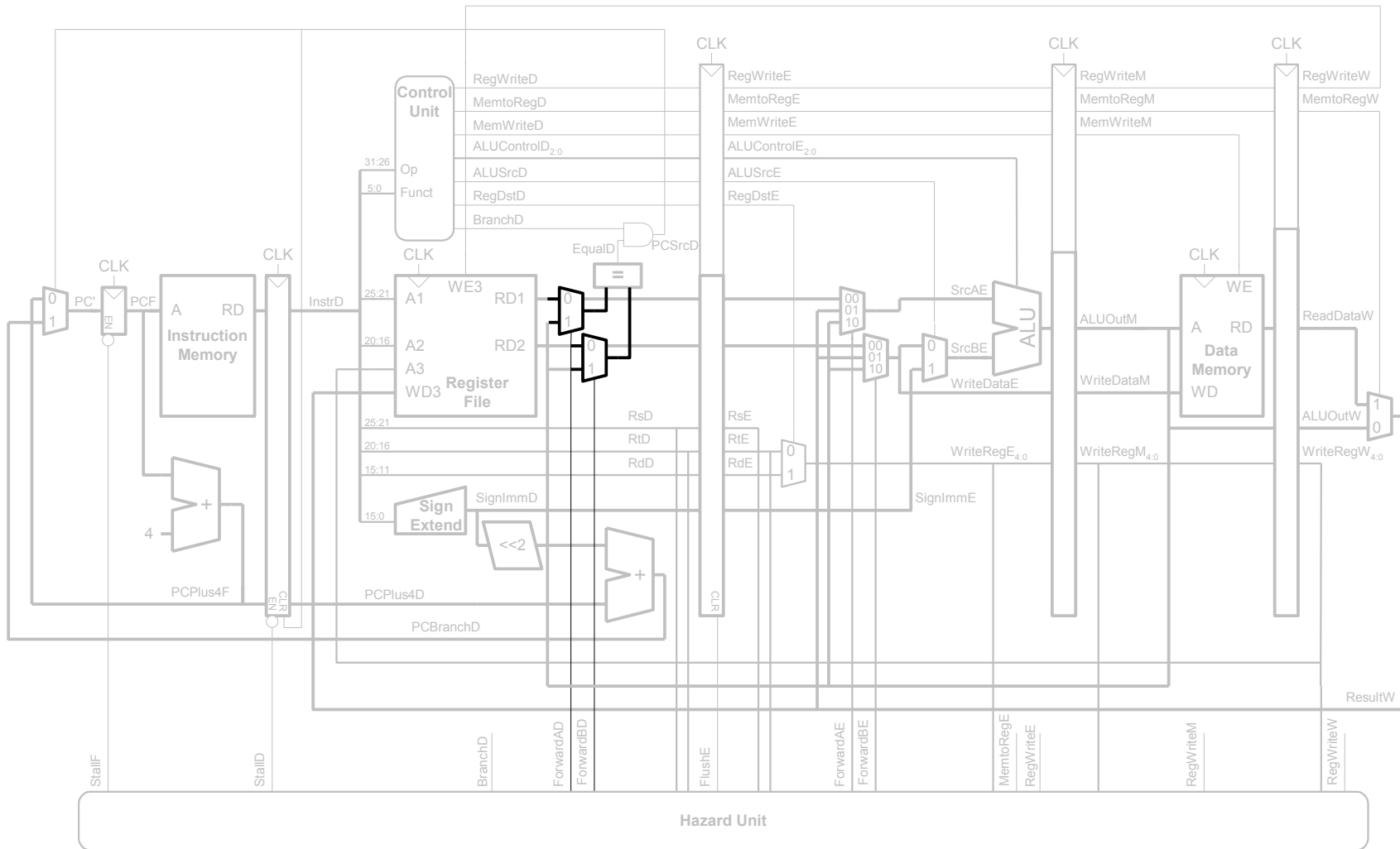

Branch Prediction

- Guess whether branch will be taken
 - Backward branches are usually taken (loops)
 - Consider history to improve guess
- Good prediction reduces fraction of branches requiring a flush

Pipelined Performance Example

- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type
- Suppose:
 - 40% of loads used by next instruction
 - 25% of branches mispredicted
 - All jumps flush next instruction
- **What is the average CPI?**

Pipelined Performance Example

- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type
- Suppose:
 - 40% of loads used by next instruction
 - 25% of branches mispredicted
 - All jumps flush next instruction
- **What is the average CPI?**
 - Load/Branch CPI = 1 when no stalling, 2 when stalling
 - $CPI_{lw} = 1(0.6) + 2(0.4) = 1.4$
 - $CPI_{beq} = 1(0.75) + 2(0.25) = 1.25$

$$\begin{aligned}\text{Average CPI} &= (0.25)(1.4) + (0.1)(1) + (0.11)(1.25) + (0.02)(2) + (0.52)(1) \\ &= \mathbf{1.15}\end{aligned}$$

Pipelined Performance

- Pipelined processor critical path:

$$T_c = \max \left\{ \begin{array}{l} t_{pcq} + t_{mem} + t_{setup} \\ 2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup}) \\ t_{pcq} + t_{mux} + t_{mux} + t_{ALU} + t_{setup} \\ t_{pcq} + t_{memwrite} + t_{setup} \\ 2(t_{pcq} + t_{mux} + t_{RFwrite}) \end{array} \right\}$$

Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20
Equality comparator	t_{eq}	40
AND gate	t_{AND}	15
Memory write	$T_{memwrite}$	220
Register file write	$t_{RFwrite}$	100 ps

$$\begin{aligned}
 T_c &= 2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup}) \\
 &= 2[150 + 25 + 40 + 15 + 25 + 20] \text{ ps} = \mathbf{550 \text{ ps}}
 \end{aligned}$$

Pipelined Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1.15)(550 \times 10^{-12}) \\ &= \mathbf{63 \text{ seconds}}\end{aligned}$$

Processor Performance Comparison

Processor	Execution Time (seconds)	Speedup (single-cycle as baseline)
Single-cycle	92.5	1
Multicycle	133	0.70
Pipelined	63	1.47